 


ENGR-354  
HW # 13

- 1) A Set-Reset flip-flop has set and reset inputs like a gated SR latch. Design a rising edge Set-Reset flip-flop using a rising edge D flip-flop and other logic gates. Draw the circuit.

Note that clock connects only to the clock input of the D flip-flop. We say that the flip-flop that is being designed inherits clock behavior (i.e. rising or fall edge triggering) from the D flip-flop.

The state diagram and SR operation table show how the assertion of S and R affect the output Q (the state diagram is a graphical way to show the operation table). The D-F/F excitation table defines how the D input needs to be asserted to make transitions state to state.




**State Diagram**

S	R	Action	$Q_{n+1}$
0	0	hold	$Q_n$
0	1	reset	0
1	0	set	1
1	1	set	1

**Operation Table**

$Q_n \rightarrow Q_{n+1}$	D
0 → 0	0
0 → 1	1
1 → 0	0
1 → 1	1

**D-F/F excitation table**

 

Block diagram of the SR flip flop you are designing.

- 2) Repeat problem one but use the operation table shown below. Draw the circuit. Also draw the state diagram.

S	R	Action	$Q_{n+1}$
0	0	hold	$Q_n$
0	1	reset	0
1	0	set	1
1	1	reset	0

**Operation Table**