


# Flip-Flops

# Terminology

- Latches are often called *Transparent* because the output will follow the input as long as the clock signal is high.
- Flip-flops are *edge-triggered*
  - Positive-edge triggered (PET) is when action occurs on the rising edge of the clock signal;
  - Negative-edge triggered (NET) is when action occurs on the falling edge of the clock signal.
- Types of Flip-flops
  - SR (rarely used);
  - D (very, very common, 74HC74);
  - JK (hardly ever used, 74HC109);
  - Toggle (occasionally used by CAD programs).

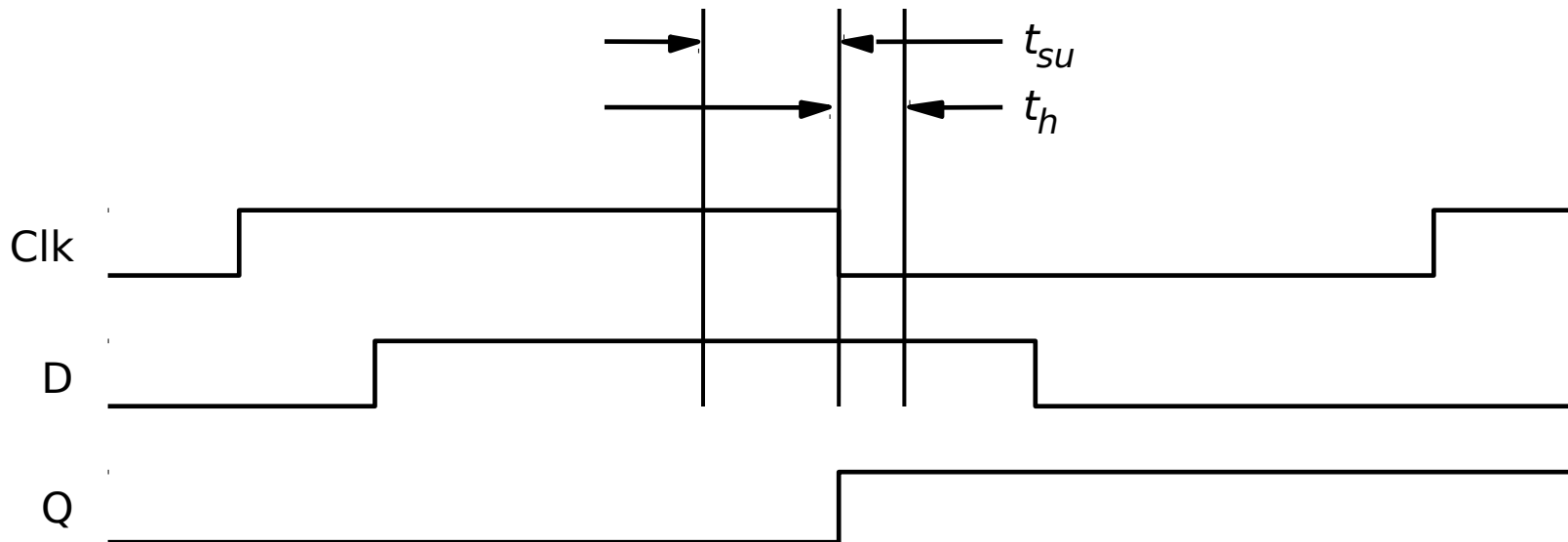
# Setup and Hold Times

- Setup time ( $t_{SU}$ ) is the time interval preceding the active transition point of the CLK during which all data inputs must remain stable.
- Hold time ( $t_H$ ) is the time interval following the active transition point of the CLK during which all data inputs must remain stable.
- See data sheet for [74HC74](#)


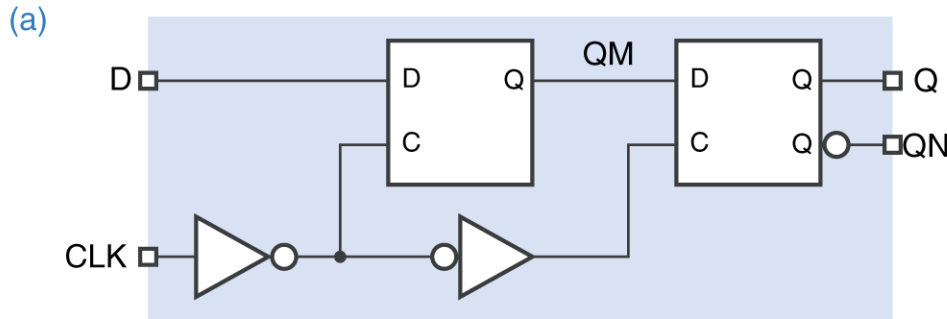
# PET Master-Slave D Flip-Flop (Positive Edge Triggered)

- QM follows the D input whenever CLK is low.
- When CLK goes high, QM is transferred to the output.



(b)

D	CLK	Q	QN
0		0	1
1		1	0
x	0	last Q	last QN
x	1	last Q	last QN


 


Figure 7-16

 
Functional behavior of a positive-edge-triggered D flip-flop.





 
# Level-Sensitive vs. Edge-Triggered

- Level-sensitive = latch
- Edge-triggered = flip-flop




(a) Circuit

 

(b) Timing diagram
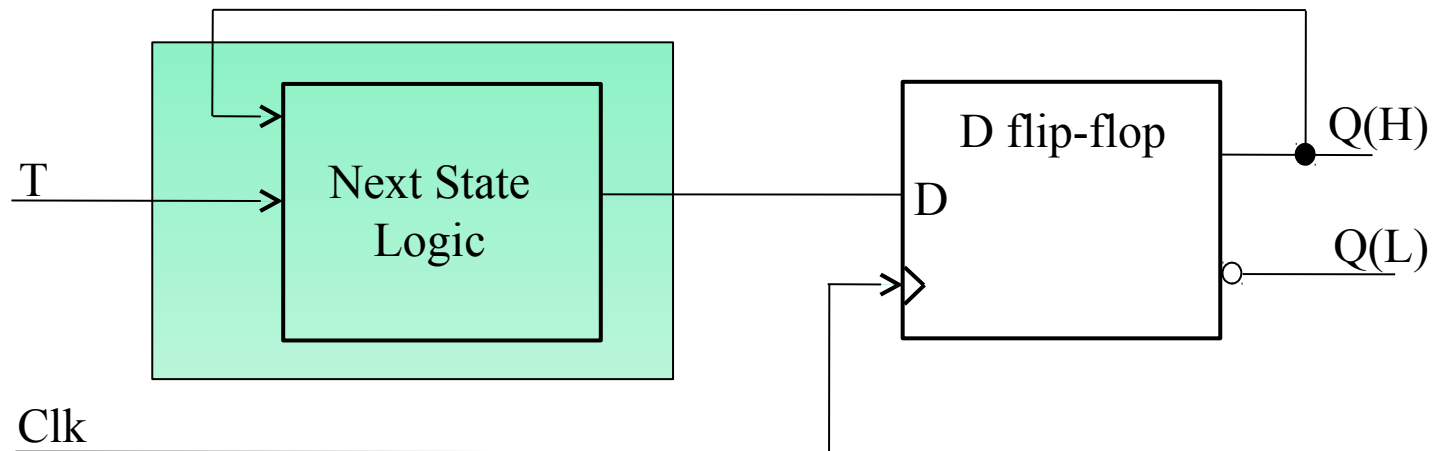
# Design a T Flip-Flop from a D Flip-Flop

- The memory element is now *edge-triggered* meaning the Clk signal is no longer part of the *next-state logic*.



T	Q(n+1)
0	Q(n)
1	$\bar{Q}(n)$

**Function Table**

Q <sub>n</sub> → Q <sub>n+1</sub>	D
0 → 0	0
0 → 1	1
1 → 0	0
1 → 1	1


**Excitation Table**

T	Q <sub>n</sub>	Q <sub>n+1</sub>	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0


**Truth Table**


 
# Design a T Flip-Flop from a D Flip-Flop




(a) Circuit

 

(c) Graphical symbol

 
# Design a JK Flip-Flop from a D Flip-Flop



**Circuit**

J	K	$Q(n+1)$
0	0	$Q(n)$
0	1	0
1	0	1
1	1	$\bar{Q}(n)$

**Function Table**

 

**Graphical symbol**

# Summary of Terminology

- Basic cell – cross-coupled NAND/NOR.
- Gated latch – output changes only while *Clk* is asserted
  - Gated SR latch;
  - Gated D latch;
  - Gated JK latch.
- Flip-flop – output changes only on *Clk* edge
  - Master-slave;
  - Edge-triggered;
  - Three main types
    - D (very, very common, 74HC74);
    - JK (hardly ever used, 74HC109);
    - Toggle (occasionally used by CAD programs).