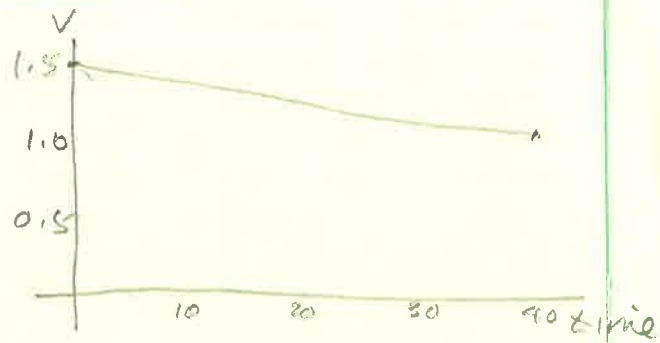


a 1.5V Battery will deliver 9mA for 40 hours. During that time the voltage drops from 1.5V to 1.0V linearly. How much energy does the Battery deliver in this 40 hour interval?





$$V = -\frac{0.5}{40h}t + 1.5$$

$$W = \int P dt = \int V I dt = \int_0^{40 \text{ hours}} \left(-\frac{0.5}{40}t + 1.5\right) (9 \text{ mA}) dt$$

$$W = 1620 \text{ J}$$

Voltage and current are shown below.

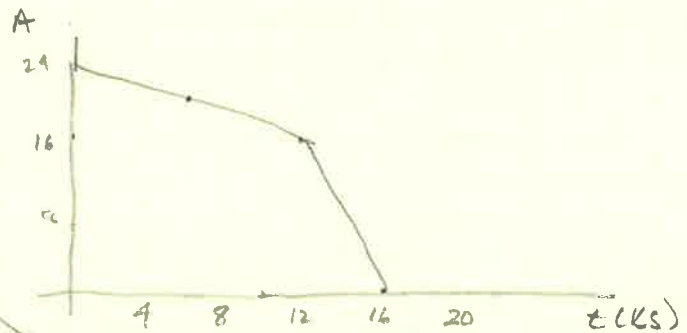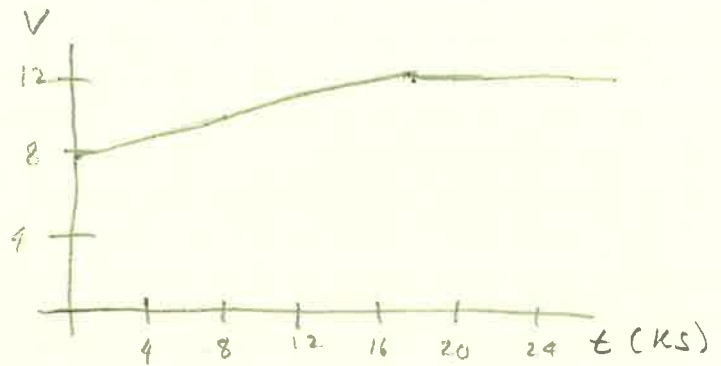- a) Find total charge transferred to battery
 b) " " energy



$$a) Q = \int i dt$$

$$= \int_0^{12K} \left(-\frac{8}{12}t + 24\right) dt$$

$$+ \int_{12K}^{16K} \left(-\frac{16}{4}t + 64\right) dt$$

(area under the curve)

$$= \frac{1}{2}(8)(12K) + 16(12) + \frac{1}{2}(4K)16$$

$$= 48K + 192K + 32K$$

$$Q = 272K C$$

b) energy = $\int \text{power } dt = \int v i dt$


$$= \int_0^{12K} \left(\frac{8}{12}t + 8\right) \left(-\frac{8}{12}t + 24\right) dt + \int_{12K}^{16K} \left(\frac{8}{12}t + 8\right) \left(-\frac{16}{4}t + 64\right) dt$$

$$= 2610.7 KJ$$

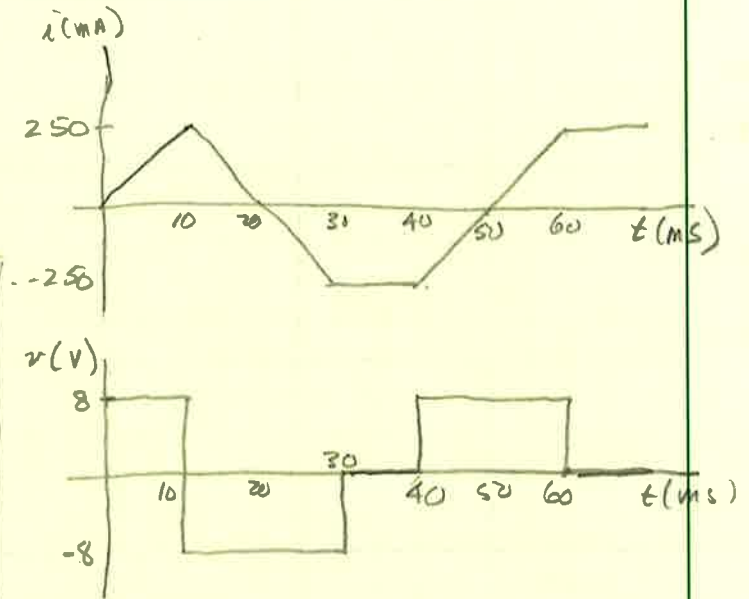1.27

nilsson 10th

- with V and I as shown:
- Sketch power vs. t
 - Calculate energy delivered to the circuit element at $t = 10, 30,$ and 80 ms.



$$a) \text{ Power} = VI$$


$$0 \leq t \leq 10 \quad P = 8\left(\frac{250}{10}t\right) \text{ mW}$$

$$10 \leq t \leq 30 \quad P = -8\left(-\frac{250}{10}t + 500\right) \text{ mW}$$

$$30 \leq t \leq 40 \quad P = 0$$

$$40 \leq t \leq 60 \quad P = 8\left(\frac{250}{10}t - 1250\right) \text{ mW}$$

$$t < 60 \quad P = 0$$

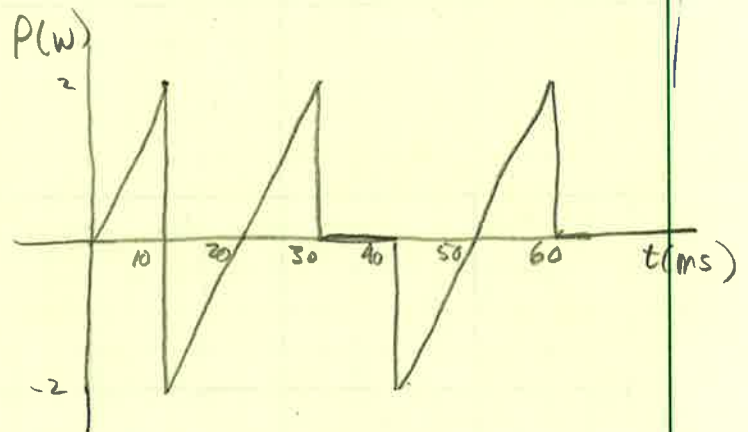

$$b) \text{ energy} = \int \text{power}$$


$$= \text{area under curve}$$

$$\text{energy}(0.01) = \frac{1}{2}(10)(2) = \underline{10 \text{ mJ}}$$

$$(0.03) = 10 - \frac{1}{2}(2)(10) + \frac{1}{2}(2)(10) = \underline{10 \text{ mJ}}$$

$$(0.80) = 10 - \frac{1}{2}(2)(10) + \frac{1}{2}(2)(10) = \underline{10 \text{ mJ}}$$

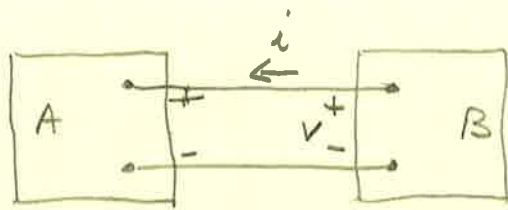Find the Power and state whether it is flowing from A-B or B-A



a) $i = 10A$ $V = 125V$

$$P_A = iV = 1250W$$

Power is flowing from B-A

b) $i = 5A$ $V = -240V$

$$P_A = -1200W \text{ from B-A or } 1200W \text{ from A-B}$$


c) $i = -12A$ $V = 480V$

$$P_A = (-12)(480) = -5760W \text{ from B-A or } 5760W \text{ from A-B}$$

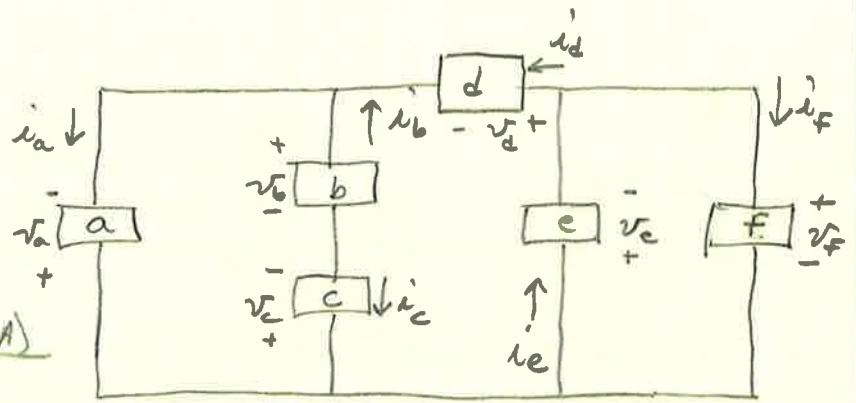d) $i = -25A$ $V = -660V$

$$P = (-25)(-660) = 16,500W \text{ from B-A}$$

Using the table below, does the circuit satisfy the power check?



Element	Volt (kV)	Curr (mA)
A	-3	-250
B	4	-400
C	1	400
D	1	150
E	-4	200
F	4	50

$$P_a = -(i_a)(v_a) = -(-250)(-3) = -750 \text{ mW}$$

$$P_b = -(i_b)(v_b) = -(-400)(4) = 1600 \text{ mW}$$

$$P_c = -(i_c)(v_c) = -(400)(1) = -400 \text{ mW}$$

$$P_d = (i_d)(v_d) = (150)(1) = 150 \text{ mW}$$

$$P_e = (i_e)(v_e) = (200)(-4) = -800 \text{ mW}$$

$$P_f = (i_f)(v_f) = (50)(4) = 200 \text{ mW}$$

$$\Sigma P_{\text{abs}} = 1600 + 150 + 200 = 1950 \text{ mW} = 1.95 \text{ W} \quad \checkmark$$

$$\Sigma P_{\text{del}} = 750 + 400 + 800 = 1950 \text{ mW} = 1.95 \text{ W} \quad \checkmark$$

Yes