

$v_o = 4V$ Before R_L
is attached.
When R_L is attached,
 $v_o = 3V$

Find R_L

Before R_L is attached,
using Voltage Divider Law,

$$4 = \frac{20(R_2)}{40 + R_2}$$

$$R_2 = 10 \Omega$$




Now the circuit becomes:

To find R_L :

$$3 = \frac{20(10 \parallel R_L)}{40 + (10 \parallel R_L)}$$

$$10 \parallel R_L = \frac{120}{17}$$

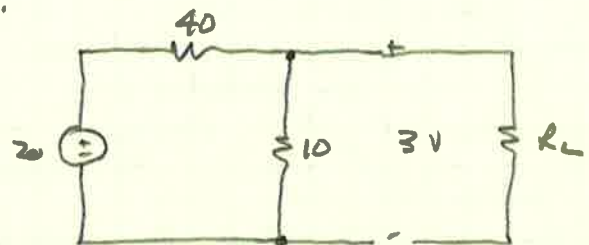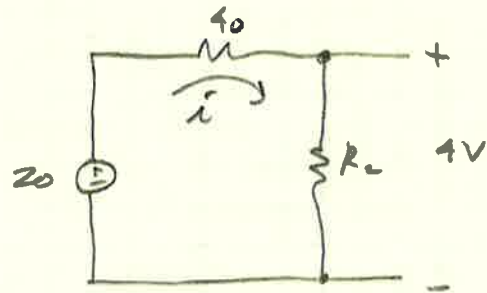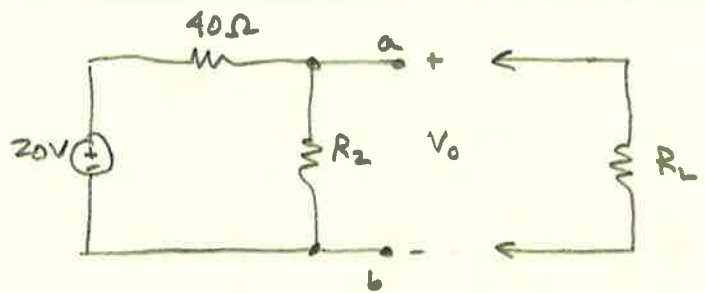
$$\frac{10(R_L)}{10 + R_L} = \frac{120}{17} \Rightarrow \boxed{R_L = 24 \Omega}$$



a) Calculate V_0

$$V_0 = \frac{75(500)}{500+2000}$$

$$V_0 = 15V$$

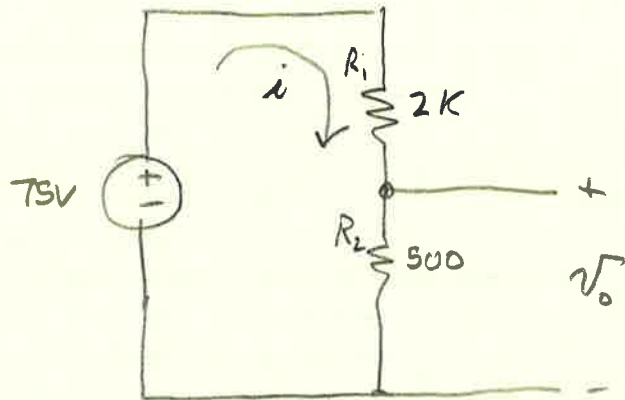

b) Calculate Power in the resistors

$$P_{500} = \frac{V^2}{R} = \frac{(15)^2}{500} = 0.45W = P_{500}$$

$$P_{2000} = \frac{V^2}{R} = \frac{(75-15)^2}{2000} = 1.80W = P_{2000}$$

c) For $V_0 = 15V$ and 1W maximum Resistor, find the smallest $R_1 + R_2$ can be


The ratio of R_1, R_2 has to remain the same

$$P_{R_1} = \frac{V^2}{R_1} \text{ or } \frac{(60)^2}{R_1} \leq 1W$$


$$R_1 \geq 3600\Omega$$

$$\text{For } R_1 = 3600, R_2 = \frac{3600}{4} = 900\Omega = R_2$$

3.16

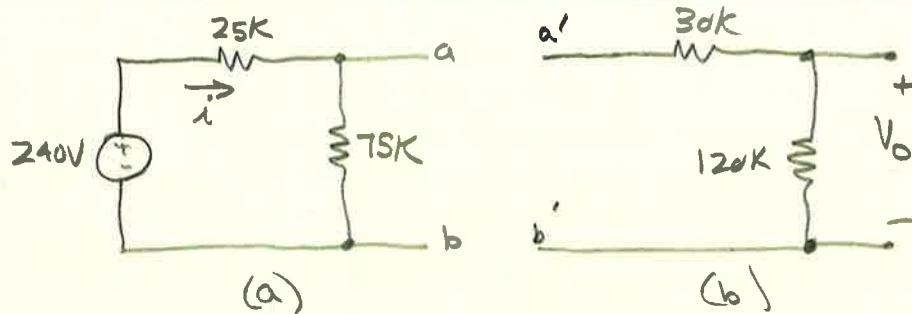Nilsson 11th

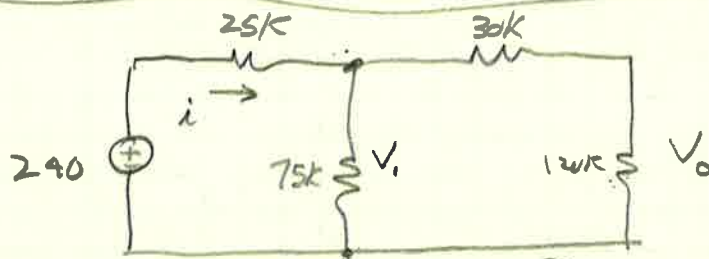The voltage divider in (a) is loaded with (b).
Find V_0 .



First find V_1 , then use a voltage divider to find V_0 .


$$30k + 120k = 150k$$

$$75k \parallel 150k = \frac{(75)(150)}{75+150} = 50k$$

The circuit now becomes:
using a voltage divider,

$$V_1 = \frac{240(50k)}{25k + 50k}$$


$$= 160V$$

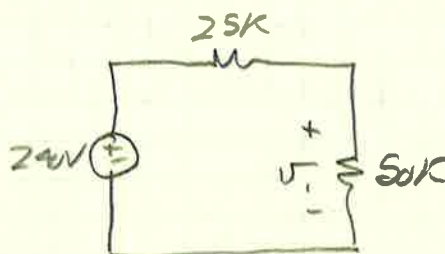


now calculate V_0 :

$$V_0 = \frac{160(120k)}{30k + 120k}$$

$$V_0 = 128V$$

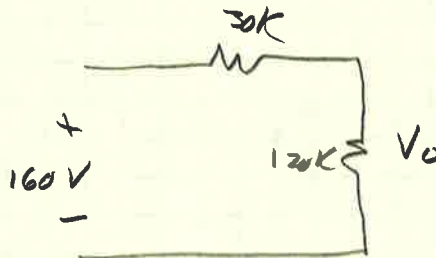

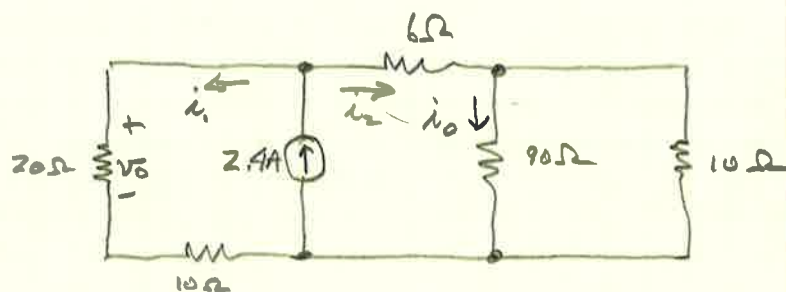

a) find $v_0 + i_0$

the $90\Omega + 10\Omega$ in parallel = $\frac{10(90)}{10+90} = 9\Omega$
using a current divider,

$$i_2 = \frac{2.4(20+10)}{(20+10)+(6+9)} = 1.6A$$

again using a current divider,

$$i_1 = \frac{2.4(6+9)}{(6+9)+(20+10)} = 0.8A$$

find i_0 using a current divider from i_2 :

$$i_0 = \frac{1.6(10)}{10+90} = \frac{16}{100} = \boxed{0.16A = i_0}$$

$$v_0 = i_1(20) = \boxed{16V = v_0}$$

b) find power dissipated in the 6Ω resistor

$$P_{6\Omega} = i_2^2 R = (1.6)^2 6 = \boxed{15.36W}$$

c) find the power developed by the source

$$V_{\text{source}} = i_1(20+10) = (0.8)(30) = 24V$$

$$P_{\text{source}} = 24(2.4) = \boxed{57.6W \text{ generated } \Delta}$$


a) FIND V_0

- assume reference
at bottom of circuit

using Voltage divider,

$$V_0 = \frac{160(R_2)}{R_1 + R_2}$$

$$V_0 = 66V$$

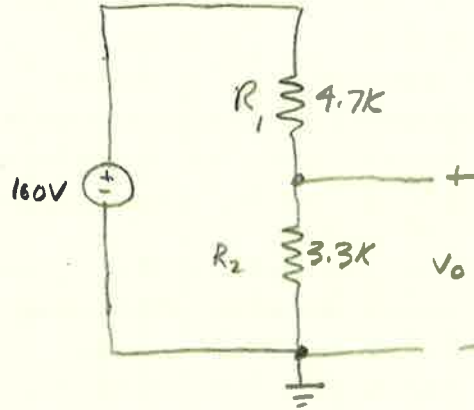

b) $P_{R_1} = \frac{V^2}{R} = \frac{(160-66)^2}{4.7k} = 1.88W$

$$P_{R_2} = \frac{(66)^2}{3.3k} = 1.32W$$

c) assume only .5W resistors available + V_0 is the same as part a. Find the smallest values of R_1 + R_2

For R_2 , $P_{R_2} = \frac{V^2}{R_2} \Rightarrow 0.5 = \frac{(66)^2}{R_2} \Rightarrow R_2 = 8.71k\Omega$

For R_1 , $P_{R_1} = \frac{(160-66)^2}{R_1} \Rightarrow 0.5 = \frac{(94)^2}{R_1} \Rightarrow R_1 = 17.67k\Omega$


a) find v_x

For left branch:

$$V_{x+} = \frac{18(6k)}{6k+2k} = 13.5V$$

$$V_{x-} = \frac{18(3k)}{9k+3k} = 4.5V$$
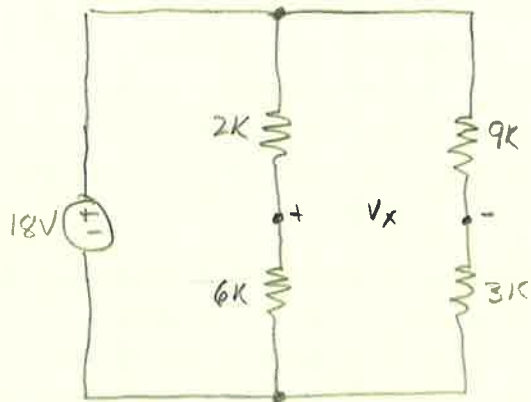
$$v_x = V_{x+} - (V_{x-}) = \boxed{9.0V}$$



b) Replace the 18V source with a general source V_s . Find v_x in terms of V_s .

$$V_{x+} = \frac{V_s(6k)}{6k+2k} = \frac{3}{4} V_s$$

$$V_{x-} = \frac{V_s(3k)}{9k+3k} = \frac{1}{4} V_s$$

$$v_x = V_{x+} - V_{x-} = \boxed{\frac{1}{2} V_s}$$