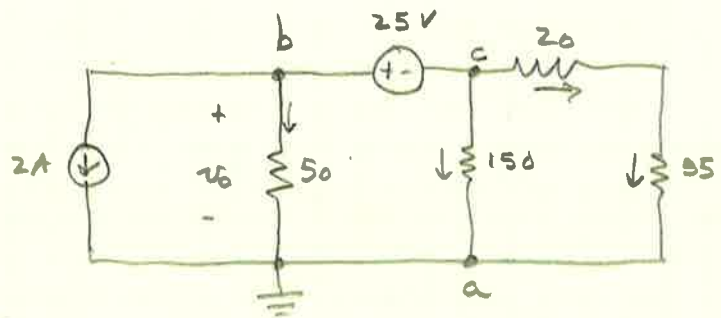


- a) FIND V_o +
 P_{2A} . Use node
 a as the reference



with node a as the
 reference, this becomes
 a super-node problem.

$$\textcircled{1} V_b = V_c + 25$$

$$\textcircled{2} \sum i_{in} = \sum i_{out} \text{ (Super node)}$$

$$0 = 2 + \frac{V_b}{50} + \frac{V_c}{150} + \frac{V_c}{75}$$

Solving:

$$V_b = V_o = -37.5V$$

$$V_c = -62.5V$$

$$P_{2A} = (-37.5)(2) = -75W$$

- b) Solve using node b as the reference.

Not a Super-node problem

$$V_b = 0V$$

$$V_c = -25V$$


Node a; $\sum i_{in} = \sum i_{out}$

$$2 + \frac{0 - V_A}{50} + \frac{(-25 - V_A)}{150} + \frac{(-25 - V_A)}{75} = 0$$

$$V_A = 37.5V$$


$$V_o = -V_A = -37.5V$$

$$P_{2A} = (-37.5)(2) = -75W$$

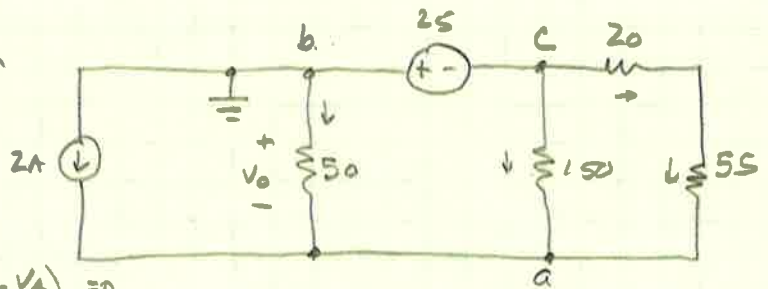

- c) which is better? - b, because it only requires 1 equation.

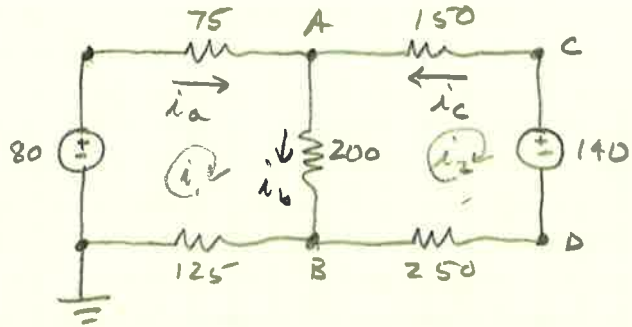a) use node-voltage method to find i_a, i_b, i_c



1) assign reference node
2) Super node problem

Node A : $i_a + i_c = i_b$

$$\frac{80 - V_A}{75} + \frac{V_C - V_A}{150} = \frac{V_A - V_B}{200} \quad (1)$$

Node V_B : $i_b = i_a + i_c$

$$\frac{V_A - V_B}{200} = \frac{V_B}{125} + \frac{V_B - V_D}{250} \quad (2)$$

Super node : $i_c = i_c$

$$\frac{V_B - V_D}{250} = \frac{V_C - V_A}{150} \quad (3)$$

Super node equation : $V_C = V_D + 140 \quad (4)$

Solving,

$$\begin{aligned} V_A &= 72.5V \\ V_B &= 12.5V \\ V_C &= 102.5V \\ V_D &= -37.5V \end{aligned}$$

b) Solve using mesh currents

mesh i_1 : $-80 + 75i_1 + 200(i_1 - i_2) + 125i_1 = 0$
 $140 + 250(i_2) + 200(i_2 - i_1) + 150i_2 = 0$


$$\begin{aligned} 400i_1 - 200i_2 &= 80 \\ -200i_1 + 600i_2 &= -140 \end{aligned}$$

$$\begin{aligned} i_1 &= 0.1A \\ i_2 &= -0.2A \end{aligned}$$

So,

$$\begin{aligned} V_A &= 80 - 75i_1 = 72.5V \\ V_B &= 0 + 125(i_1) = 12.5V \\ V_C &= V_A + (-i_2)(150) = 102.5V \\ V_D &= V_C - 140 = -37.5V \\ \text{also, } V_D &= V_B + (i_2)(250) = -37.5V \end{aligned}$$

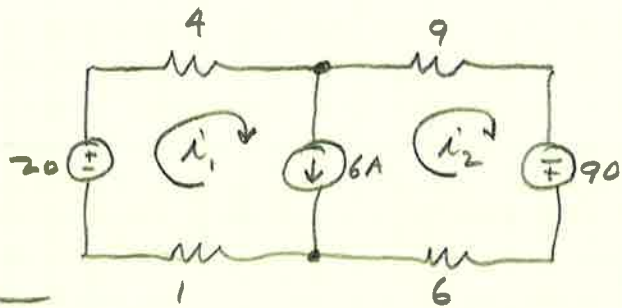use the mesh
current method to
solve for total
power dissipated.



Super-mesh problem

$$i_1 - i_2 = 6$$

$$-20 + 4i_1 + 9i_2 - 90 + 6i_2 + 1i_1 = 0$$

$$i_1 - i_2 = 6$$

$$5i_1 + 15i_2 = 110$$

Solving : $i_1 = 10A$
 $i_2 = 4A$

$$P_{20V} = -(20)(10) = -200W$$

$$P_{90V} = -(90)(4) = -360W$$

$$P_{6A} = (-i_1 + 20 - i_2)(6) = -180W$$

} 740 W generated

$$P_4 = i_1^2 R = (10)^2 \cdot 4 = 400W$$

$$P_1 = (10)^2 \cdot 1 = 100W$$

$$P_9 = (4)^2 \cdot 9 = 144W$$


$$P_6 = (4)^2 \cdot 6 = 96W$$

} 740 W dissipated

4.58

$N_1 / 5 \text{ ssm}$ $11 \frac{4h}{m}$
 0.003 V_Δ

Find P_{20V} source

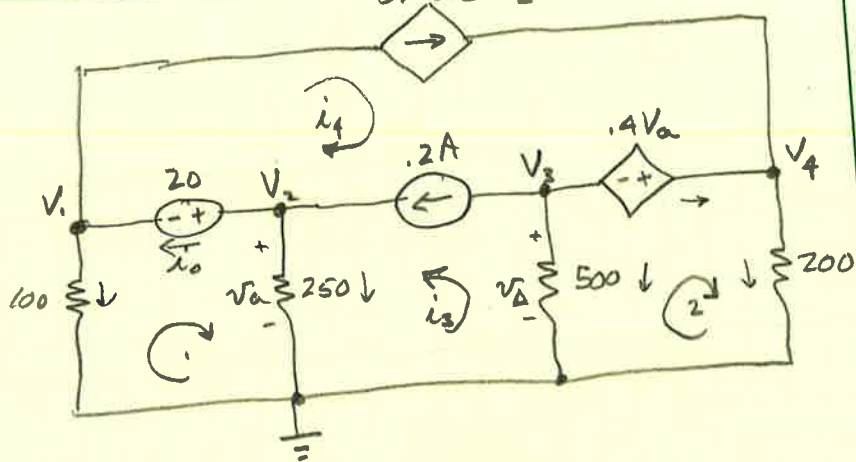

NODAL ANALYSIS

Note: Both voltage sources are Super nodes

Nodes $V_1 + V_2$: $\sum i_{in} = \sum i_{out}$
 $.2 = \frac{V_2}{250} + \frac{V_1}{100} + 0.003V_\Delta$

Super node $V_1 + V_2$: $V_2 = V_1 + 20$
 also: $V_\Delta = V_3$

Nodes $V_3 + V_4$: $\sum i_{in} = \sum i_{out}$
 $0.003V_\Delta = .2 + \frac{V_3}{500} + \frac{V_4}{200}$

also $V_4 = V_3 + 4V_a$

$V_a = V_2$

Solving: $V_1 = 24V$
 $V_2 = 44V = V_a$
 $V_3 = -72V = V_\Delta$
 $V_4 = -54V$

$i_1 = -240 \text{ mA} \checkmark$
 $i_2 = -272 \text{ mA} \checkmark$
 $i_3 = 416 \text{ mA} \checkmark$
 $i_4 = -216 \text{ mA} \checkmark$

$i_o = .2 - \frac{V_2}{250} = 24 \text{ mA}$

$\therefore P_{20V} = (20)(24 \text{ mA}) = \boxed{480 \text{ mW absorbed}}$

Mesh technique

mesh 1: $100i_1 - 20 + 250(i_1 + i_3) = 0$
 mesh 2: $-4V_a + 200i_2 + 500(i_2 + i_3) = 0$
 mesh 3: $i_3 + i_4 = .2$
 mesh 4: $V_a = 250(i_1 + i_3)$
 $i_4 = 0.003V_\Delta = 0.003(500(i_3 + i_2))$

Solving: $i_1 = -240 \text{ mA}$
 $i_2 = -272 \text{ mA}$
 $i_3 = 416 \text{ mA}$
 $i_4 = -216 \text{ mA}$