

Find the Norton equivalent at a-b.





$$R_{Norton} = \frac{(3K)(6K)}{3K+6K}$$

$$= \underline{2K\Omega}$$


$$I_N = \frac{75mA(4K)}{4K+2K}$$

$$= 50mA$$

The Norton equivalent is shown below.

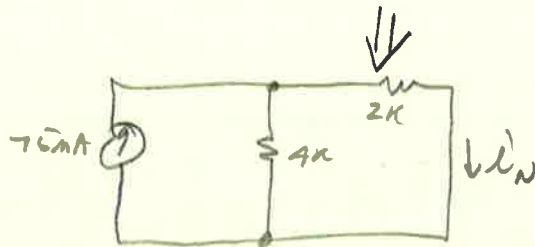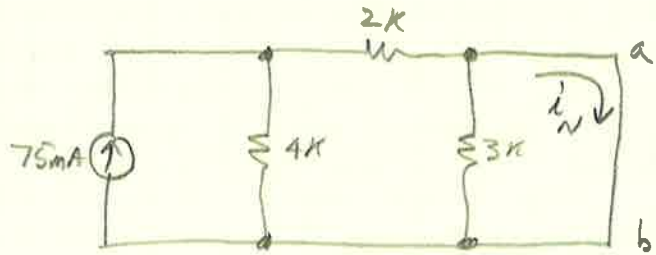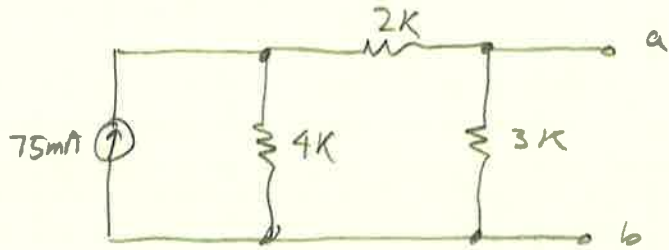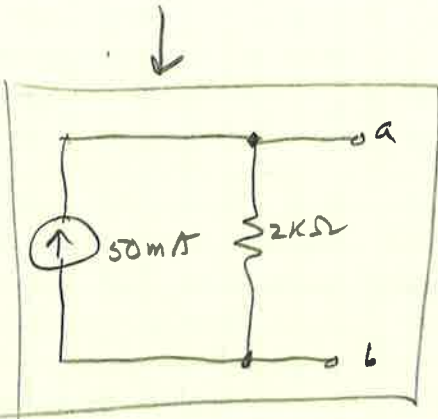


Find the Thevenin equivalent at a-b.

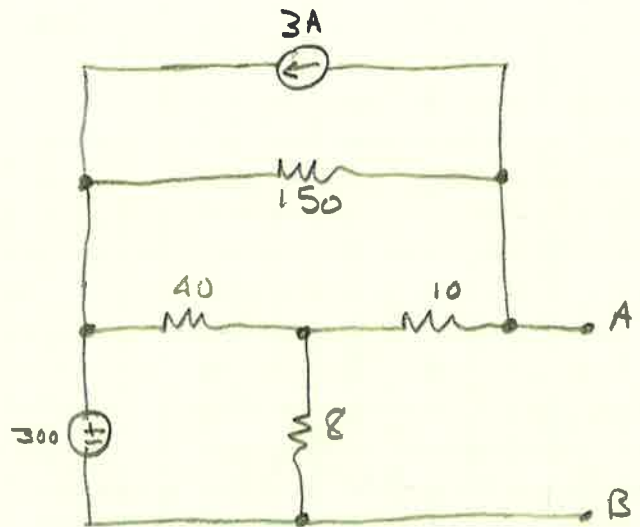

1) Find R_{th}

$$R_{th} = (40 \parallel 8 + 10) \parallel 150$$

$$R_{th} = 15 \Omega$$

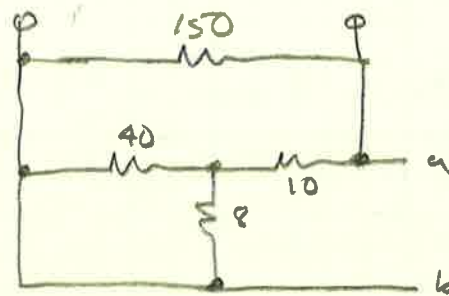

2) Find V_{th}

Do a source transformation
write mesh equations

mesh i_1

$$-300 + 40(i_1 - i_2) + 8i_1 = 0$$

mesh i_2

$$450 + 150i_2 + 10i_2 + 40(i_2 - i_1) = 300$$


Solving

$$i_1 = 5.25 \text{ A}$$


$$i_2 = -1.2 \text{ A}$$

$$V_A = V_{th} = 300 - 450 + i_2(150)$$

$$V_{th} = 30 \text{ V}$$

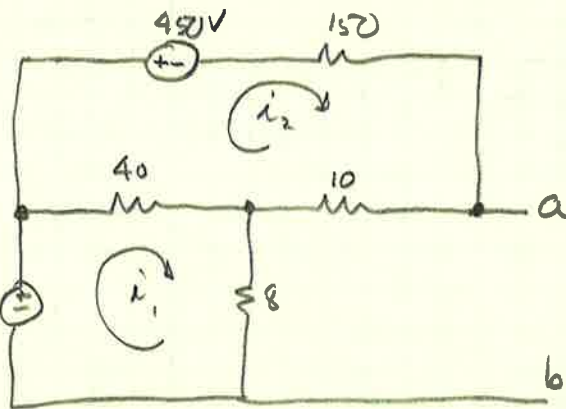

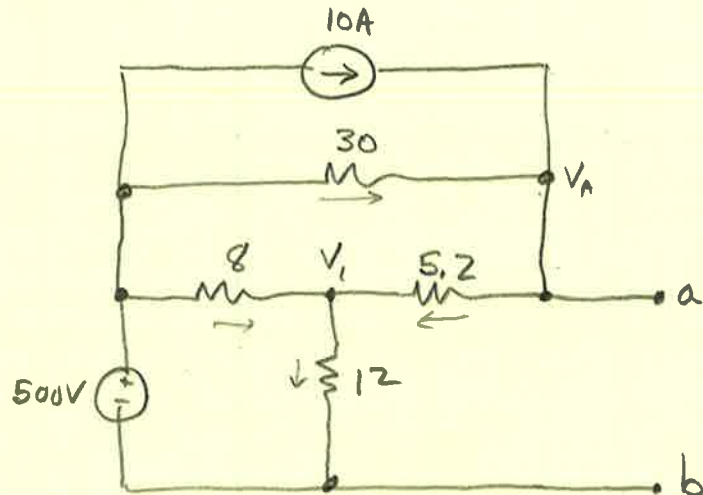
Find thevenin equivalent at terminals a-b.



Find R_{th} : $i \rightarrow$ open
 $v \rightarrow$ short

$$R_{th} = [(8 \parallel 12) + 5.2] \parallel 30$$

$$= \boxed{7.5 \Omega}$$

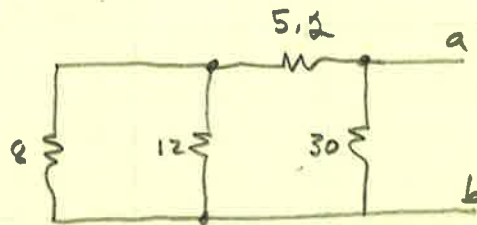

Find V_{th} :

node V_A : $\sum i_{in} = \sum i_{out}$

$$10 + \frac{500 - V_A}{30} = \frac{V_A - V_1}{5.2}$$

node V_1 : $\frac{500 - V_1}{8} + \frac{V_A - V_1}{5.2} = \frac{V_1}{12}$

$$\boxed{V_A = V_{th} = 425V}$$

$$V_1 = 360V$$