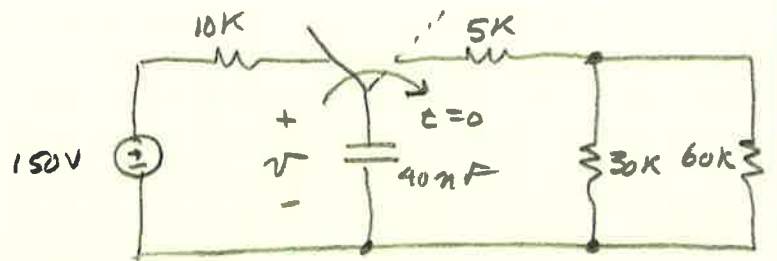


The switch moves to the right at $t=0$.



- a) Find the initial voltage drop across the capacitor.

$$v_c(0^-) = 150\text{V} = v_c(0^+)$$

- b) Find the initial energy stored in the capacitor.

$$E = \frac{1}{2} C V^2 = 0.45\text{mJ}$$

- c) Find τ for $t > 0$.


$$\tau = R_{eq} C = (5k + 30k \parallel 60k) C = 1\text{ms} = \tau$$

- d) Find $v_c(t)$ for $t \geq 0$

$$v_c(t) = v_0(t) e^{-t/\tau}$$


$$v_c(t) = 150 e^{-1000t} \text{ V} \quad t \geq 0$$

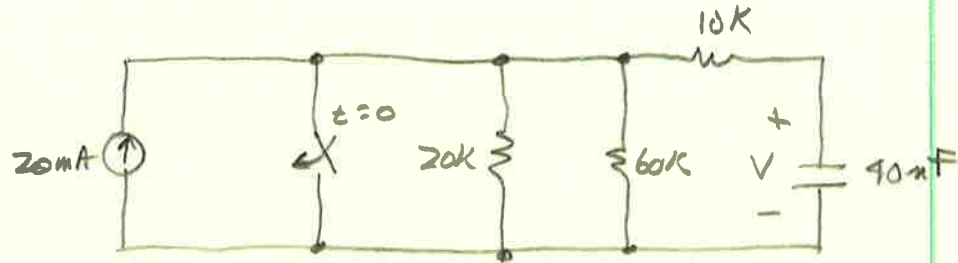switch has
been open for
a long time.
find $v(t)$.



Find $v_c(0)$

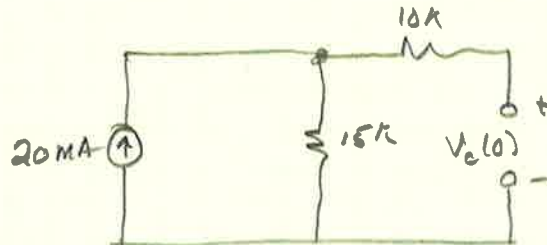
$$v_c(0) = 20\text{mA}(15\text{k}) \\ = 300\text{V}$$





after switch closes,

$$R_{eq} = 25\text{k}$$

$$v_c(t) = v_0 e^{-t/\tau}$$

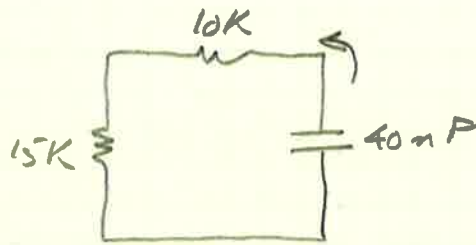


$$v_c(t) = 300 e^{-10000t} \text{ V}$$

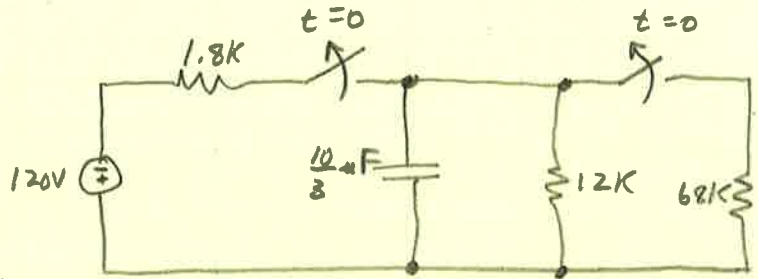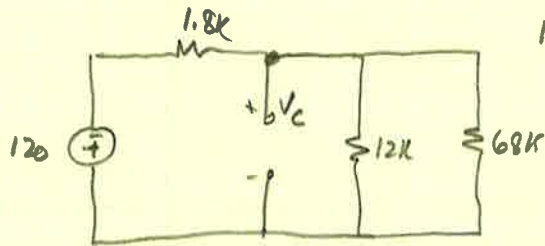For $t < 0$:

$$V_c(0^-) = \frac{-120(12 \parallel 68)}{(12 \parallel 68) + 1.8} = -102V$$

for $t > 0$:

$$V_c(t) = -102e^{-25t}$$

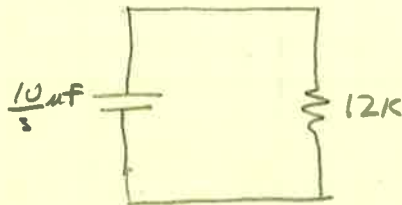

$$\text{Power} = \frac{V^2}{R} = .867e^{-50t}$$

- a) Find How many μ Joules have been dissipated in R 12 ms after the switch open.

$$W = \int_0^{0.012} .867e^{-50t} dt$$

$$= \frac{.867}{-50} \left(e^{-50t} \Big|_0^{0.012} \right) = \frac{.867}{-50} (.5498 - 1)$$

$$W = 7.824 \mu J$$

- b) How long does it take to dissipate 75% of the initial stored energy?


$$W(0) = \frac{1}{2} CV^2 = \frac{1}{2} \left(\frac{10}{3} \times 10^{-6} \right) (-102)^2 = 17.34 \text{ mJ}$$

$$75\% (W(0)) = 13 \text{ mJ}$$

$$\int_0^{t_0} .867e^{-50t} dt = .013 \Rightarrow t = 27.73 \text{ ms}$$

$$v = 48e^{-25t} \text{ V} \quad t \geq 0^+$$
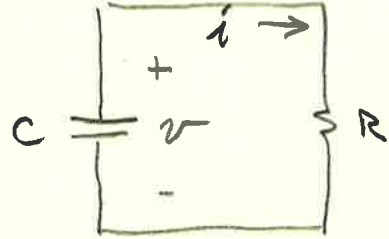
$$i = 12e^{-25t} \text{ mA} \quad t \geq 0^+$$



find:

A) $R = \frac{v}{i} = \boxed{4 \text{ k}\Omega = R}$

B) $C \quad \frac{L}{R_C} = 25 \Rightarrow \boxed{C = 10 \mu\text{F}}$

C) $\tau = RC = \boxed{40 \text{ ms}}$

D) initial energy in capacitor

$$E = \frac{1}{2} CV^2 = \boxed{11.52 \text{ mJ}}$$

E) the amount of energy dissipated by the resistor after 60 ms

$$E_{60\text{ms}} = \int_0^{0.06} \frac{v^2}{R} dt = \int_0^{0.06} \frac{(48e^{-25t})^2}{4\text{k}} dt$$

$$= \frac{48^2}{4000} \left(\frac{e^{-50t}}{-50} \right) \Big|_0^{0.06}$$

$$= 0.576 \left[\frac{e^{-50(0.06)}}{-50} - \left(-\frac{1}{50} \right) \right]$$

$$\boxed{E = 10.95 \text{ mJ}}$$

Switch moves @ $t=0$
 Find $i_o(t)$ for $t \geq 0^+$

Before $t=0$,

$$i_c = 0 \text{ so } V_c(0) = 15V$$

after,

writing KVL,

$$15i_o + 5i_o + \frac{1}{C} \int i_o dt = 0$$

$$20 \frac{di_o}{dt} + \frac{i_o}{C} = 0$$



$$\Rightarrow i_o = i_o(0) e^{-\frac{t}{20C}} = i_o(0) e^{-25,000t}$$


$$V_c = \frac{1}{C} \int i_c(t) dt = \frac{1}{C} \int i_o(0) e^{-25,000t} dt$$

$$V_c = \frac{i_o(0)}{-25,000C} e^{-25,000t}$$

$$V_c(0) = 15 = \frac{i_o(0)}{-25,000C} e^0 \Rightarrow i_o(0) = -0.75A$$

$$i_o(t) = -0.75 e^{-25,000t} A$$

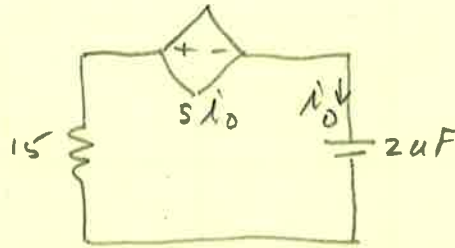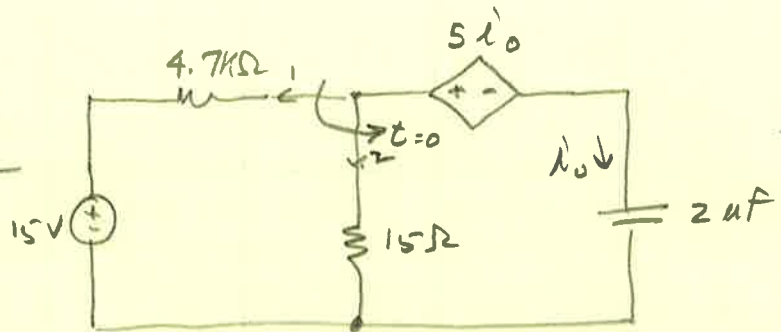

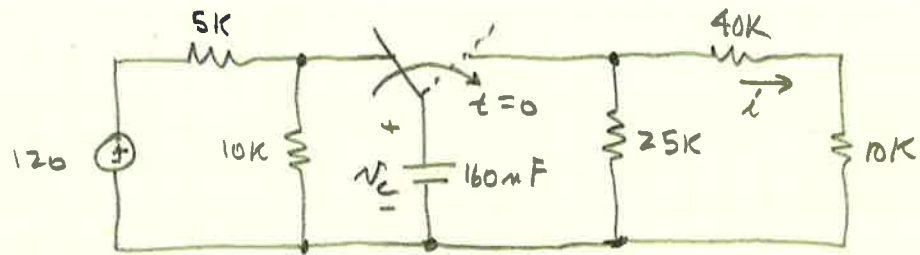


The switch has been in the left position for a long time, at $t=0$ it moves to the right position.

a) Find $v_c(t)$ for $t \geq 0$


$$v_c(t) = v_c(0) e^{-t/\tau} \text{ V}$$

The capacitor is an open circuit.
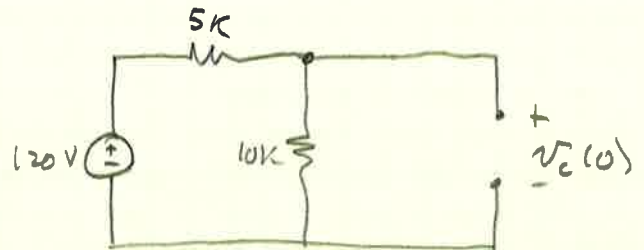
$$v_c(0) = \frac{120(10k)}{10k + 5k} = 80 \text{ V}$$



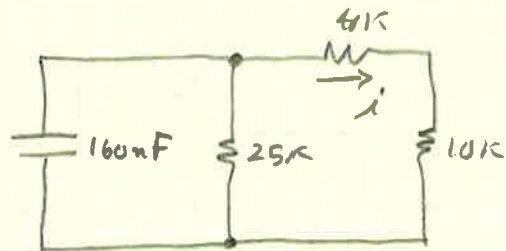For $t > 0$, the capacitor discharges through the circuit shown at the right.



$$R_{eq} = (40k + 10k) \parallel 25k = 16.667k\Omega$$

$$\tau = RC = (160 \times 10^{-9})(16.667k) = 2.667 \text{ ms}$$

$$v_c(t) = 80 e^{-375t} \text{ V}$$

b) Find $i(t)$ for $t \geq 0$

$$\text{Since } v_c(t) = 80 e^{-375t}$$

$$i = \frac{v_c(t)}{40k + 10k} = 1.6 e^{-375t} \text{ mA} = i(t)$$