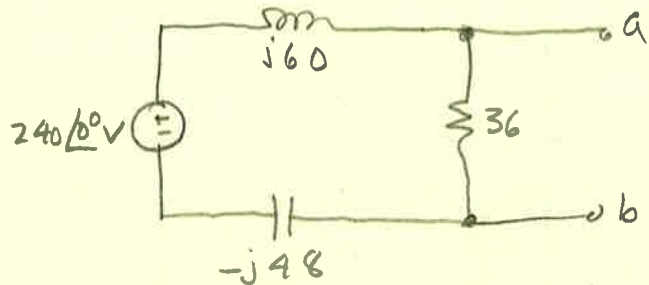


Use source transformation to find thevenin equiv. at ab.



$$Z = j60 - j48 = j12$$

$$I = \frac{V}{Z} = \frac{240 \angle 0^\circ}{12 \angle 90^\circ} = 20 \angle -90^\circ$$

$$Z \parallel 36 = \frac{(12j)(36)}{12j + 36}$$

$$= \frac{432 \angle 90^\circ}{37.95 \angle 18.43^\circ}$$

$$= 11.384 \angle 71.565^\circ$$

$$= Z_{th}$$

$$V_{th} = I_{th} Z_{th}$$

$$= 20 \angle -90^\circ (11.384 \angle 71.565^\circ)$$



$$= 227.7 \angle -18.435^\circ \text{ V}$$


$$V_{th} = 227.7 \angle -18.435^\circ \text{ V}$$

$$= 216 - 72j \text{ V}$$

$$Z_{th} = 11.384 \angle 71.565^\circ \Omega$$

$$= 3.6 + 10.8j \Omega$$

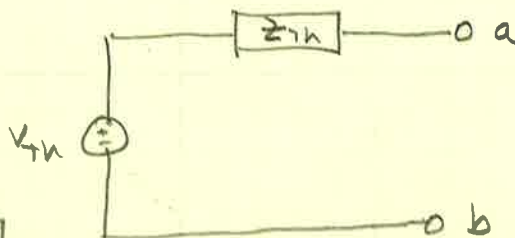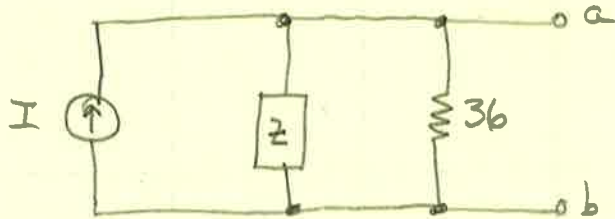

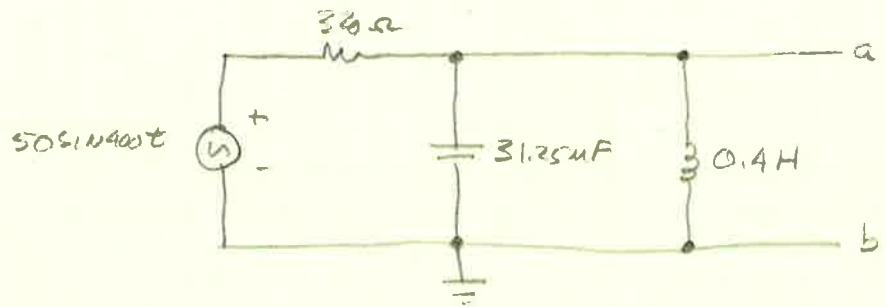


Find the Thevenin equivalent at terminals a-b.

- Convert circuit to frequency domain.

$$Z_C = \frac{1}{j\omega C} = -80j$$

$$Z_L = j\omega L = 160j$$

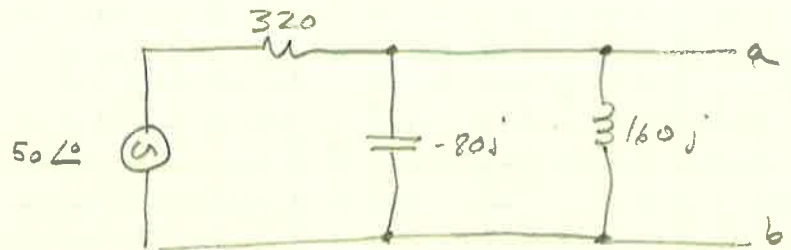

$$Z_{Th} = 160j \parallel (-80j \parallel 320)$$

$$= 64 - j128 \Omega$$


$$= 143 \angle -63.43^\circ$$

$$\text{use cosine: } 50 \angle 0^\circ = 50 \angle -90^\circ$$

$$V_{Th} = \frac{(50 \angle -90^\circ)(-80j \parallel 160j)}{320 + (-80j \parallel 160j)} = \frac{-20 - j10 \text{ V}}{22.36 \angle -153.46^\circ \text{ V}}$$

Use the node-voltage method to find

V_g .

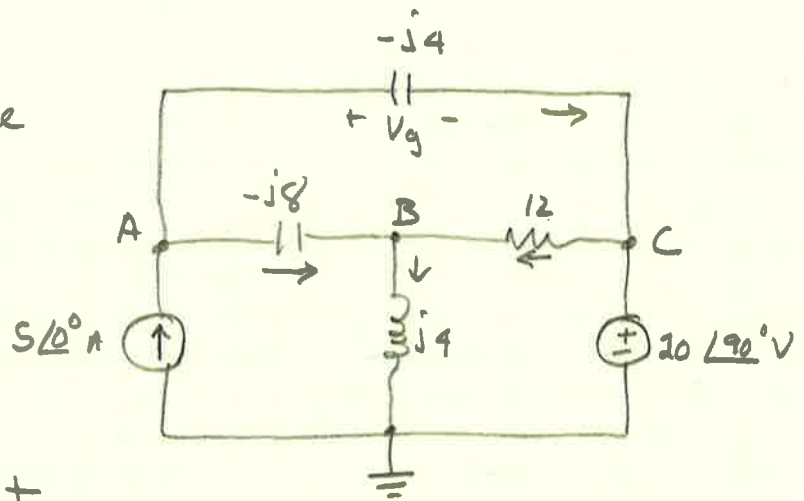

1) Place reference at bottom of circuit

2) $V_C = 20 \angle 90^\circ$

$$\text{Node A: } \sum i_{in} = \sum i_{out}$$

$$5 \angle 0^\circ = \frac{V_A - 20 \angle 90^\circ}{-j4} + \frac{V_A - V_B}{-j8}$$

$$\text{Node B: } \sum i_{in} = \sum i_{out}$$


$$\frac{V_A - V_B}{-j8} + \frac{20 \angle 90^\circ - V_B}{12} = \frac{V_B}{j4}$$

$$\text{Solving: } V_A = -\frac{8}{3} + \frac{4}{3}j$$

$$V_B = -8 + j4$$

$$V_g = V_A - V_C = -\frac{8}{3} - j\frac{56}{3} \text{ V}$$

Find i_0 using the mesh-current method.

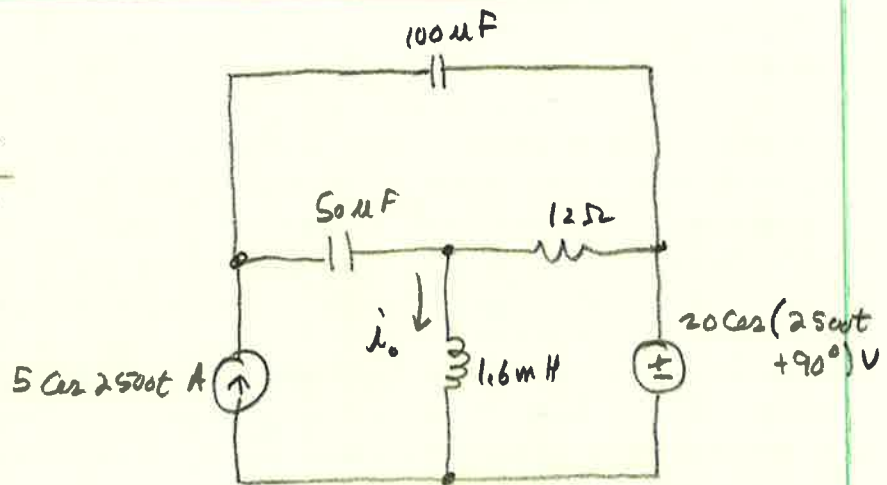

convert to frequency domain

$$\omega = 2500 \text{ rad/s}$$

$$Z_{100\mu\text{F}} = \frac{1}{j\omega C} = -4j$$

$$Z_{50\mu\text{F}} = -8j$$

$$Z_L = j\omega L = 4j$$

mesh i_1

$$i_1 = 5 \angle 0^\circ$$

mesh i_2

$$-4j(i_2) + 12(i_2 - i_3) - 8j(i_2 - i_1) = 0$$

mesh i_3

$$20 \angle 90^\circ + 4j(i_3 - i_1) + 12(i_3 - i_2) = 0$$


solving:

$$\begin{aligned} i_1 &= 5 \angle 0^\circ \text{ A} = 5 + j0 \text{ A} \\ i_2 &= -0.667j + 4.667 \text{ A} \\ i_3 &= 4 - j2 = 4.47 \angle -26.57^\circ \text{ A} \end{aligned}$$

$$i_0 = i_1 - i_3$$


$$i_0 = 1 + j2 = 2.24 \angle 63.43^\circ \text{ A}$$
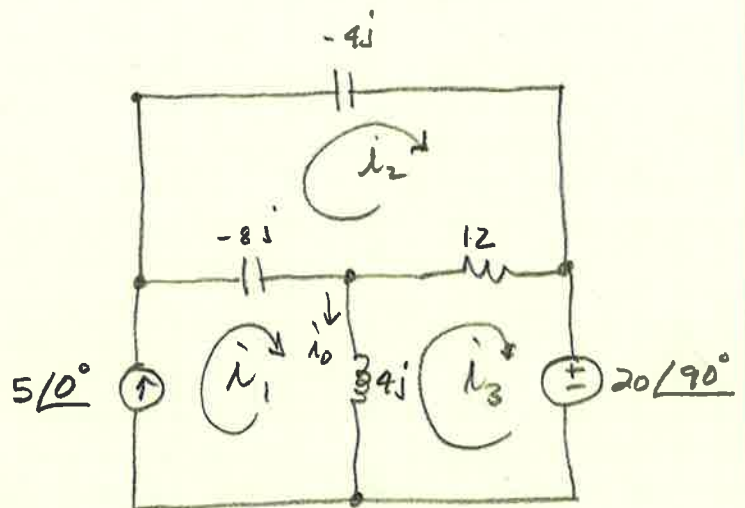
$$= 2.24 \cos(2500t + 63.43^\circ) \text{ A}$$



Find V_o using mesh analysis.

400cos 5000t

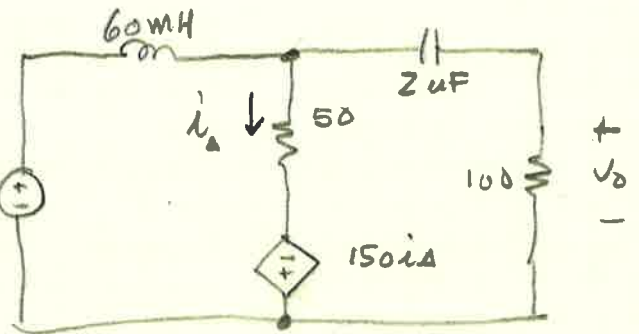


$$\omega = 5000$$

$$Z = j\omega L = 300j$$

$$Z_C = \frac{1}{j\omega C} = -100j$$

Redraw:

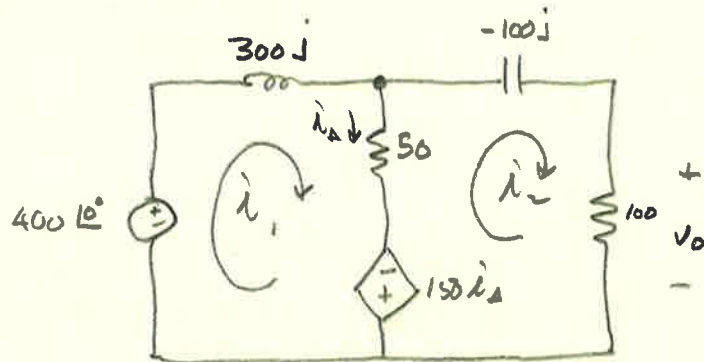

mesh i_1

$$\textcircled{1} -400\angle 0 + i_1(300j + 50(i_1 - i_2)) - 150i_A = 0$$

Mesh i_2

$$\textcircled{2} -100ji_2 + 100i_2 + 150i_A + 50(i_2 - i_1) = 0$$

$$\textcircled{3} i_A = i_1 - i_2$$

$$\text{Solving: } \begin{aligned} i_1 &= -1.8 - 1.6j \text{ A} \\ i_2 &= -1.6 + 0.8j \text{ A} \\ i_A &= 0.8 - 2.4j \text{ A} \end{aligned}$$

$$V_o = 100i_2 = -160 + 80j = 178.89 \angle 153.43^\circ \text{ V}$$

$$V_o = 178.89 \cos(5000t + 153.43^\circ) \text{ V}$$

$$i = 125 \cos(800t + 36.87^\circ) \text{ mA}$$

a) Find F

$$800 = \omega = 2\pi f \Rightarrow f = \frac{800}{2\pi} = \boxed{127.32 \text{ Hz}}$$

b) Find T in milliseconds

$$T = \frac{1}{f} = \frac{1}{127.32} = \boxed{7.854 \text{ ms}}$$

c) Find I_m

$$I_m = \boxed{125 \text{ mA}}$$

d) Find $i(0)$

$$i(0) = 125 \cos(36.87^\circ) = \boxed{100 \text{ mA}}$$

e) Find ϕ in degrees + radians

$$\boxed{\phi = 36.87^\circ} = \frac{36.87(2\pi)}{360^\circ} = \boxed{0.644 \text{ radians} = \phi}$$

f) Smallest positive value of t for which $i = 0$.

$$0 = 125 \cos(800t + 36.87^\circ)$$

$$800 \frac{\text{rad}}{\text{sec}} t = 53.13^\circ = 53.13 \left(\frac{2\pi \text{ rad}}{360^\circ} \right) = 0.9273 \text{ rad}$$

$$t = \frac{0.9273}{800} = \boxed{1.159 \text{ ms}}$$


g) Smallest positive value of t at which $\frac{di}{dt} = 0$

$$\frac{di}{dt} = 125(-800 \sin(800t + 36.87^\circ))$$

$$\frac{di}{dt} = 0 \text{ when } 800t + 36.87^\circ = 180^\circ$$

$$t = \frac{(180^\circ - 36.87^\circ) \left(\frac{2\pi}{360} \right)}{800} = \boxed{3.12 \text{ ms}}$$
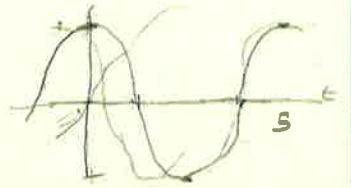
$$v(t) = 25 \cos(400\pi t + 60^\circ) \text{ V}$$



a) what is the maximum amplitude of v ?

$$\boxed{V_{\max} = 25 \text{ V}}$$

b) Find freq. in Hz

$$\omega = 2\pi f = 400\pi \Rightarrow f = \frac{400\pi}{2\pi} = \boxed{200 \text{ Hz}}$$

c) Find freq in rad/sec $\Rightarrow \omega = 400\pi = \boxed{1257 \text{ rad/sec}}$

d) Find phase angle in radians

$$\theta = 60^\circ = 60 \left(\frac{\pi}{180} \right) = \frac{\pi}{3} = \boxed{1.047 \text{ rad}}$$

e) find θ in degrees

$$\boxed{\theta = 60^\circ}$$

f) find period

$$P = \frac{1}{f} = \frac{1}{200} = \boxed{5 \text{ ms}}$$

g) what is the first time after $t=0$ that $v=0$ V?

for $\cos v=0$ after $\frac{1}{4}$ period

$$\text{But } 60^\circ = \frac{1}{6} \text{ period so crosses } 0 \text{ after } \left(\frac{1}{4} - \frac{1}{6} \right) 5 \text{ ms} = \frac{1}{12} (5 \text{ ms}) = \boxed{416.7 \mu\text{s}}$$


h) v is shifted $\frac{5}{6}$ ms to the right. what is the new $v(t)$?

$$\frac{5}{6} \text{ ms is } \frac{1}{6} \text{ of a period} = 60^\circ \text{ so } \boxed{v = 25 \cos 400\pi t \text{ V}}$$

i) what is the minimum number of ms that the function must be shifted to the left for $v(t) = 25 \sin 400\pi t$ V?

$$\text{must be shifted } \frac{3}{4}T - \frac{1}{6}T = \frac{7}{12}T = \boxed{2.917 \text{ ms}}$$


use mesh-current method to find v_o .

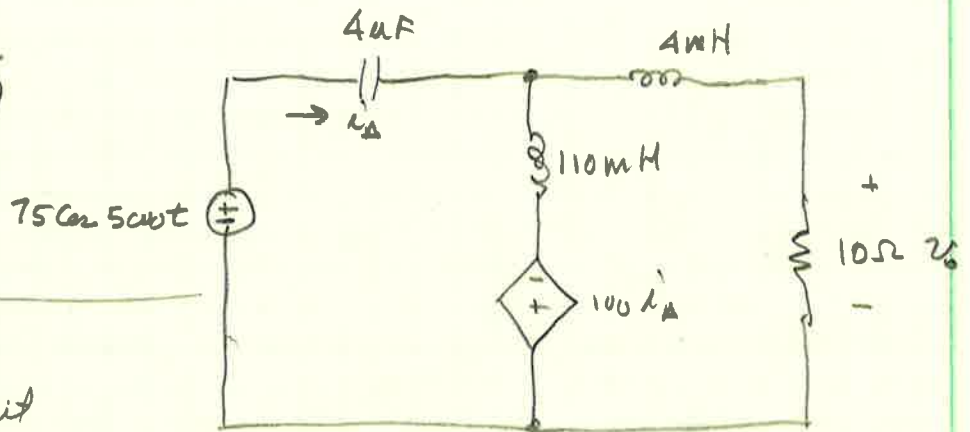

1) transform circuit

$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$

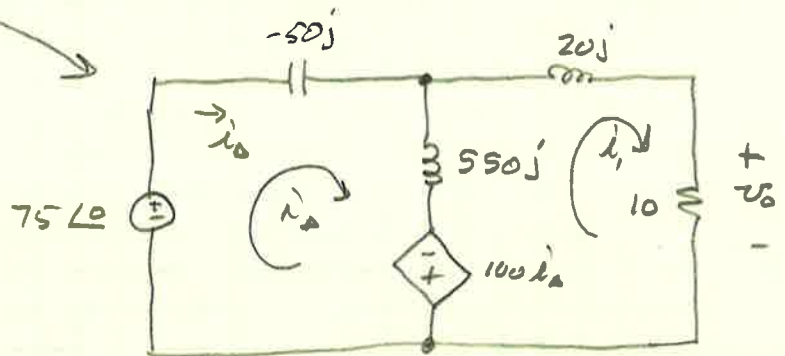

2) write mesh equations:

$$i_\Delta: -75 \angle 0 - 50j(i_\Delta) + 550j(i_\Delta - i_1) - 100i_\Delta = 0$$

$$i_1: 20j(i_1) + 10(i_1) + 100i_\Delta + 550j(i_1 - i_\Delta) = 0$$

$$i_\Delta: i_\Delta(400j) + i_1(-550j) = 75 \angle 0$$


$$i_1: i_\Delta(100 - 550j) + i_1(10 + 570j) = 0$$

$$\text{Solving: } i_\Delta = 3.25j \text{ A}$$

$$i_1 = 2.5j \text{ A}$$

$$v_o = 10(i_1) = 25j = 25 \angle 90^\circ = 25 \cos(5000t + 90^\circ) \text{ V.}$$

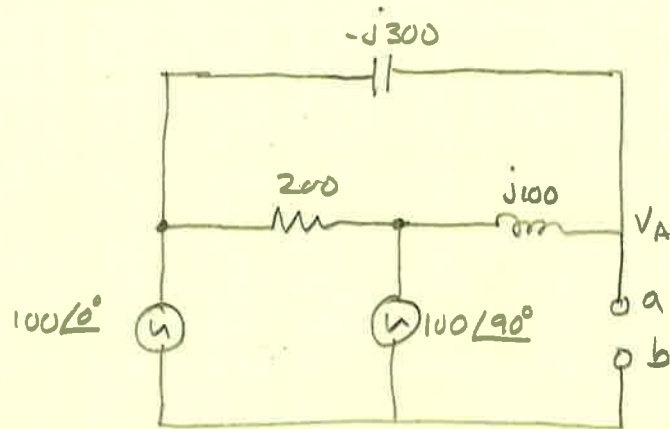
Find the Thevenin equivalent @ terminals a,b.



Z_{th}

$$\begin{aligned} Z_{in} &= j100 \parallel -j300 \\ &= \frac{(j100)(-j300)}{j100 - j300} \\ &= 30000 / -200j \end{aligned}$$

$$Z_{in} = 150j \Omega$$

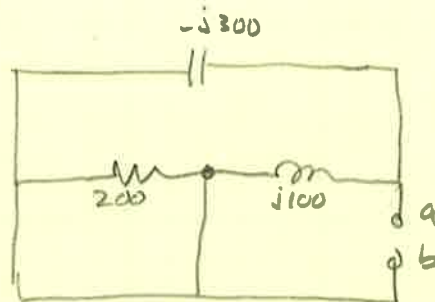

V_{th}

$$\text{NODE A: } \frac{100 \angle 0^\circ - V_A}{-j300} = \frac{V_A - 100 \angle 90^\circ}{j100}$$

$$V_A = 158.11 \angle 108.43^\circ \text{ V}$$