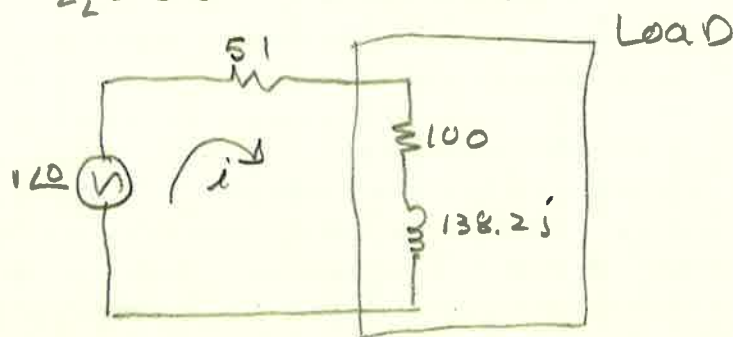


$$f = 1 \text{ MHz} \Rightarrow \omega = 2\pi f$$


$$Z_L = j\omega L = j138.2 \Omega$$



$$i = \frac{170}{51 + 138.2j} = 4.885 \angle -42.47 \text{ mA}$$

$$V_{R_L} = i(100) = 0.4885 \angle -42.47 \text{ V}$$
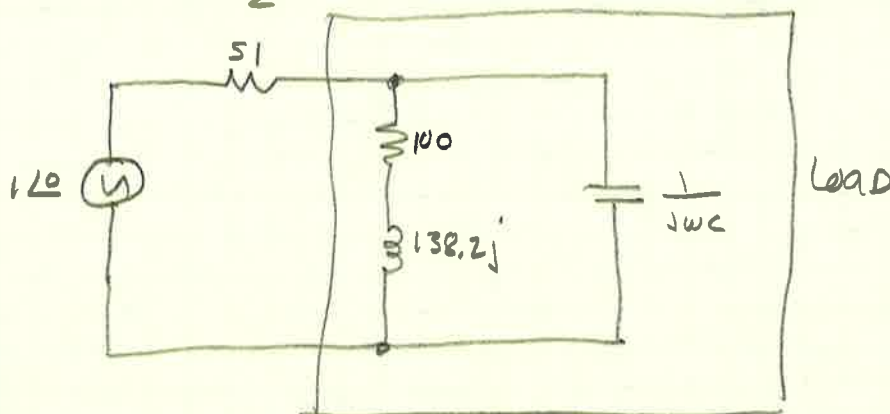
$$P_L = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \underline{\underline{1.1932 \text{ mW}}}$$



$$Z_L = (100 + 138.2j) \parallel \frac{1}{j\omega C} = \frac{(170.59 \angle 54.11) (\frac{1}{\omega C} \angle -90^\circ)}{170.59 \angle 54.11 + \frac{1}{\omega C} \angle -90^\circ}$$

$$= \frac{170.59 \angle -35.889^\circ}{\omega C} = \frac{170.59 \angle -35.889^\circ}{100 + j(138.2 - \frac{1}{\omega C})}$$

$$\theta(z_L) = \left(-35.889 - \tan^{-1} \left[\frac{138.2 - \frac{1}{\omega c}}{100} \right] \right)$$

$$-35.889 = \tan^{-1} [\quad]$$

$$-.7236 = \frac{138.2 - \frac{1}{\omega c}}{100}$$

$$\frac{1}{\omega c} = 210.559 \Rightarrow C = \frac{1}{\omega(210.559)} = \boxed{756 \text{ pF}}$$

$$C = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{RMS}}^2}$$