

The book cover for ENGR 228: Circuit Analysis features an orange background with a circular diagram of electrical formulas. The formulas include V^2/R , $R \times I$, P/I , $R \times I^2$, $V \times I$, P , V , I , and R . The text on the cover includes "ENGR 228: Circuit Analysis", "Multiple instructors", and "SPRING 2020".

Chapter 3.2
Analysis Techniques
Node Voltage Method


Engr228 - Circuit Analysis
Spring 2020

Dr Curtis Nelson

Section 3.2 Objective

- Learn to apply the node-voltage method to analyze an electric circuit of any configuration, so long as it is linear and planar.

Resistors in Series

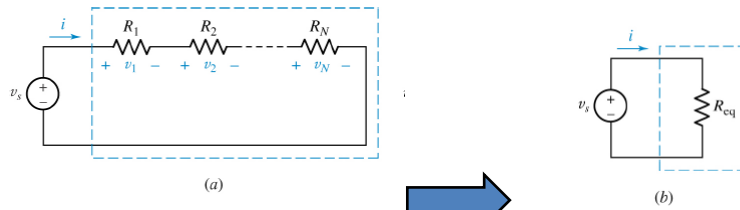

$$v_s = v_1 + v_2 + \dots + v_N$$

$$v_s = R_1 i + R_2 i + \dots + R_N i$$


$$= (R_1 + R_2 + \dots + R_N) i$$

$$v_s = R_{eq} i$$

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

Voltage Division

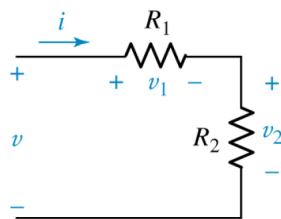Resistors in series “share” the voltage applied to them.



$$v = v_1 + v_2$$

$$= i(R_1 + R_2)$$


$$i = \frac{v}{R_1 + R_2}$$

$$v_2 = i R_2 = \left(\frac{v}{R_1 + R_2} \right) R_2$$



$$v_2 = \frac{R_2}{R_1 + R_2} v$$

Parallel Connections

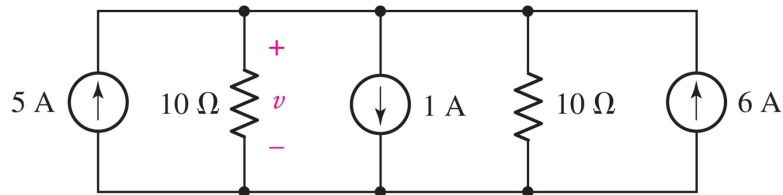- Elements in a circuit connected head-to-head and tail-to-tail have a common voltage across them and are said to be connected in *parallel*.



Resistors in Parallel

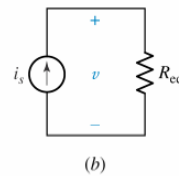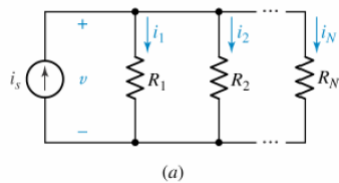


$$i_s = i_1 + i_2 + \cdots + i_N$$

$$i_s = \frac{v}{R_1} + \frac{v}{R_2} + \cdots + \frac{v}{R_N} = \frac{v}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}$$

Two Resistors in Parallel
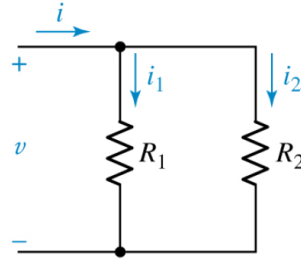
$$\begin{aligned} R_{\text{eq}} &= R_1 \parallel R_2 \\ &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \end{aligned}$$




$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

Connecting resistors in parallel makes the equivalent resistance *smaller. Always.*


Current Division

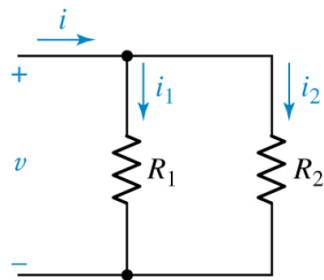Resistors in parallel “share” the current through them.



$$\begin{aligned} i_2 &= \frac{v}{R_2} \\ &= \frac{i(R_1 \parallel R_2)}{R_2} \\ &= \frac{i}{R_2} \frac{R_1 R_2}{R_1 + R_2} \end{aligned}$$


$$i_2 = i \frac{R_1}{R_1 + R_2}$$

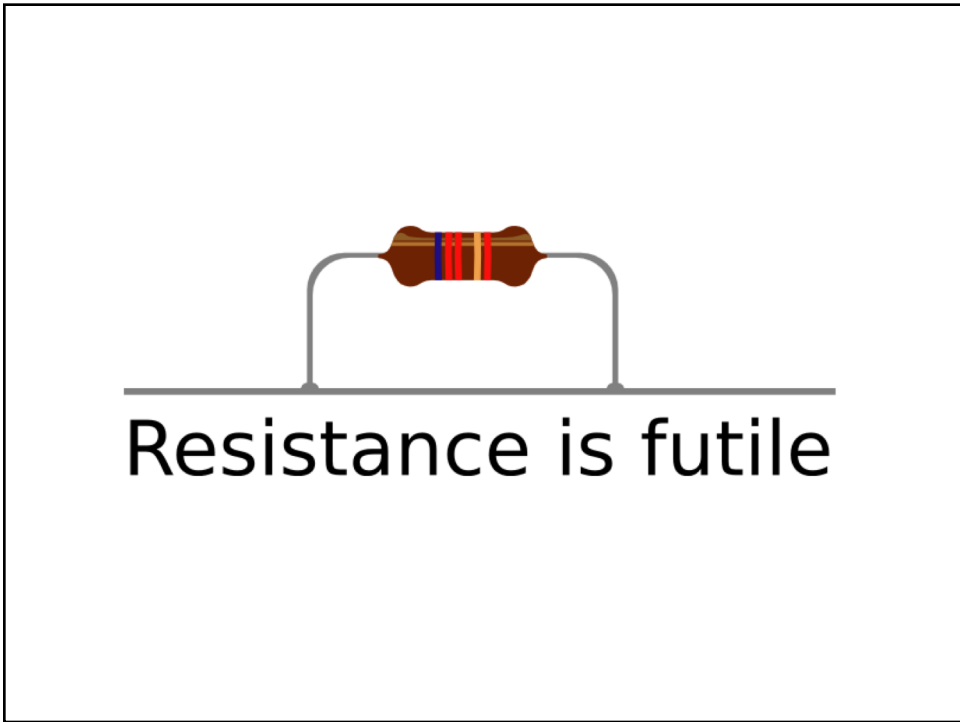

Circuit Analysis

- We need an organized method of applying KVL, KCL, and Ohm's law;
- *Nodal* analysis assigns *voltages* to each node, and then we apply *Kirchhoff's Current Law* to solve for the *node voltages*;
- *Mesh* analysis assigns *currents* to each mesh, and then we apply *Kirchhoff's Voltage Law* to solve for the *mesh currents*.


Review - Nodes, Paths, Loops, Branches

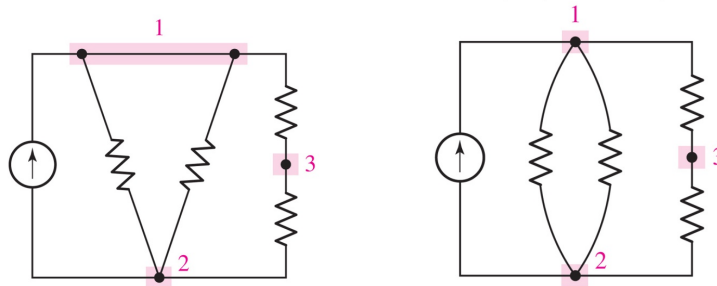

- These two circuits are equivalent.
- There are three *nodes* and five *branches*:
 - *Node*: a point at which two or more elements have a common connection;
 - *Path*: a sequence of nodes;
 - *Branch*: a single path in a circuit composed of one simple element and the node at each end of that element;
 - *Loop*: a closed path.


Node Example

- Node = every point along the same wire

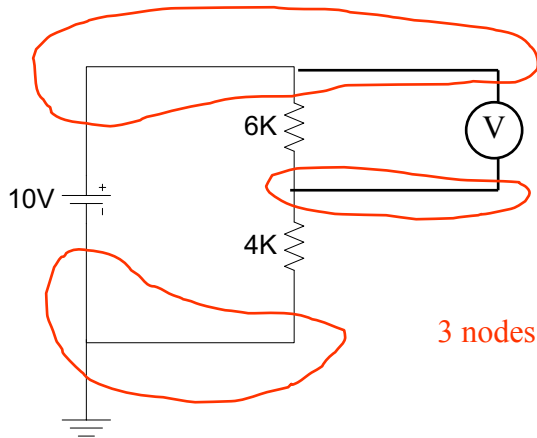

Nodes

- How many nodes in the circuits below?

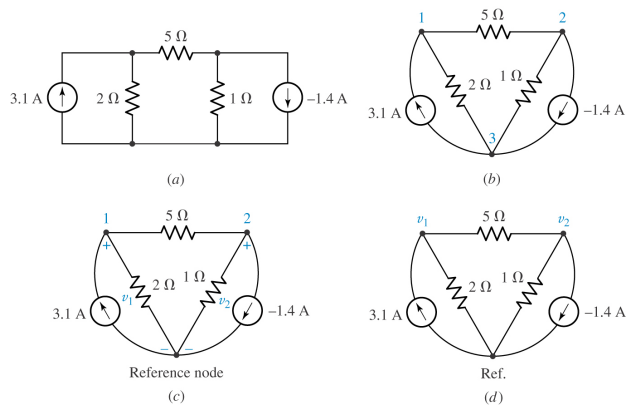

Notes on Writing Nodal Equations


- All terms in the equations are in units of **current**;
- Everyone has their own style of writing nodal equations
 - The important thing is that you remain consistent.
- Probably the easiest method if you are just getting started is to remember that:

$$\text{current entering a node} = \text{current leaving the node}$$

- Current directions can be assigned arbitrarily, unless they are previously specified.


The Nodal Analysis Method

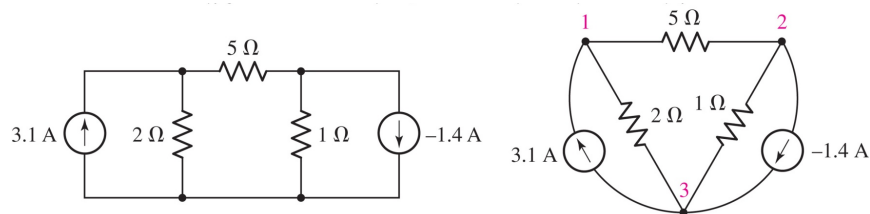- Assign voltages to every node relative to a reference node.




Choosing the Reference Node

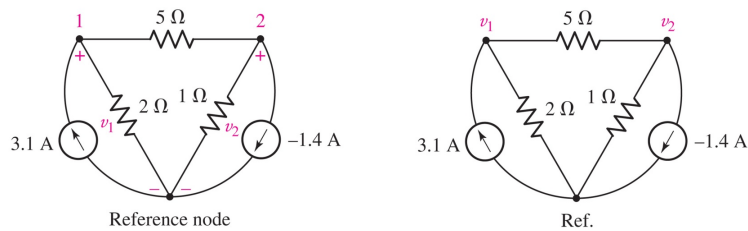- By convention, the bottom node is often the reference node;
- If a ground connection is shown, then that becomes the reference node;
- Otherwise, choose a node with many connections;
- Assign the reference node a value of 0.00 volts.



Apply KCL to Find Voltages

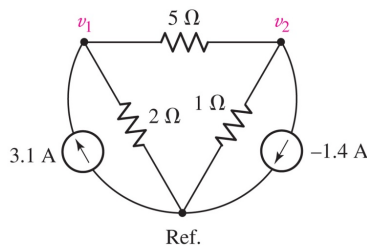
- Assume reference voltage = 0.00 volts;
- Assign current names and directions;
- Apply KCL to node v_1 (Σ out = Σ in);
- Apply Ohm's law to each resistor.



$$\frac{v_1}{2} + \frac{v_1 - v_2}{5} = 3.1$$

Apply KCL to Find Voltages

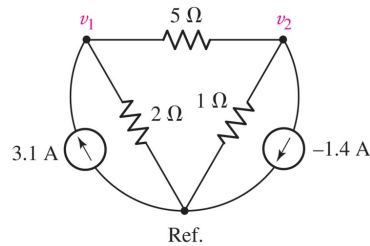- Apply KCL to node v_2 (Σ out = Σ in);
- Apply Ohm's law to each resistor.




$$\frac{v_1 - v_2}{5} = \frac{v_2 - 0}{1} + (-1.4)$$

We now have two equations for the two unknowns v_1 and v_2 and we can solve them simultaneously:

$$v_1 = 5V \text{ and } v_2 = 2V$$

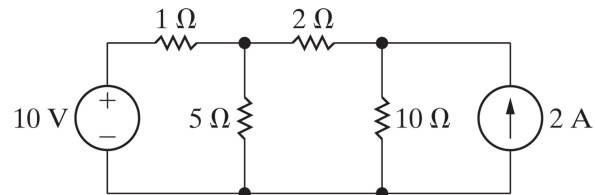Example Problem Page 96 (Nilsson 11th)

Solve for the node voltages in the circuit below.



*Answer: Left node = 9.09 V
Right node = 10.91 V*

Nodal Analysis: Dependent Source Example

Determine the power supplied by the dependent source.


Key step: eliminate i_1 from the equations using $v_1 = 2i_1$

$$15 = \frac{v_1 - v_2}{1} + \frac{v_1 - 0}{2}$$

$$\frac{v_1 - v_2}{1} + 3i_1 = \frac{v_2 - 0}{3}$$


$$i_1 = \frac{v_1 - 0}{2}$$

Answer: 4.5 kW being generated

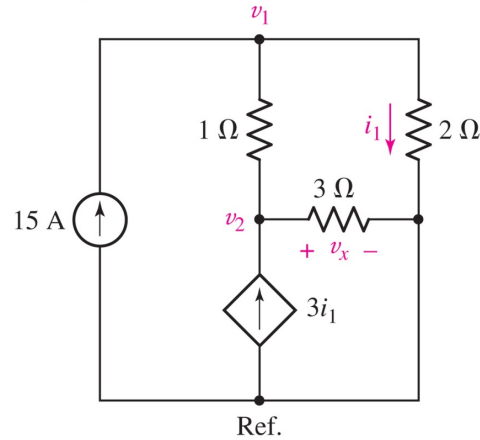


Node Voltage Example

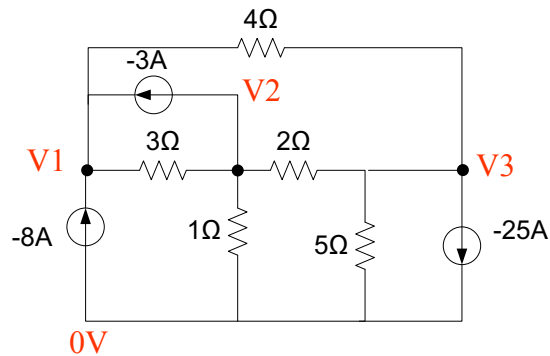- How many nodes are in this circuit?
- How many nodal equations must you write to solve for the unknown voltages?



Node Voltage Example – Node V1

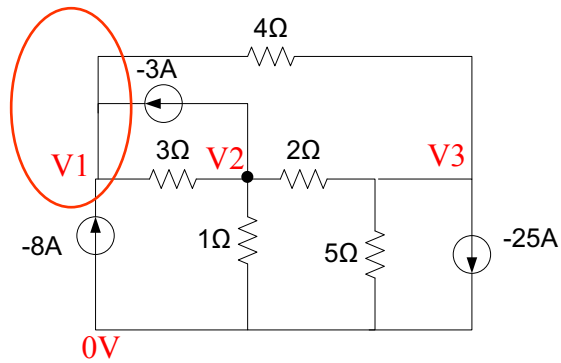


At node V_1

$$8 + \frac{V_1 - V_3}{4} + 3 + \frac{V_1 - V_2}{3} = 0$$

$$96 + 3V_1 - 3V_3 + 36 + 4V_1 - 4V_2 = 0$$

$$7V_1 - 4V_2 - 3V_3 = -132$$

Node Voltage Example – Node V2

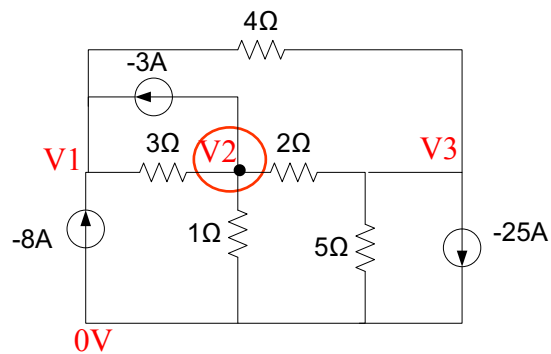


At node V_2

$$\frac{V_2 - V_1}{3} - 3 + \frac{V_2 - V_3}{2} + \frac{V_2 - 0}{1} = 0$$

$$2V_2 - 2V_1 - 18 + 3V_2 - 3V_3 + 6V_2 = 0$$

$$-2V_1 + 11V_2 - 3V_3 = 18$$

Node Voltage Example – Node V3

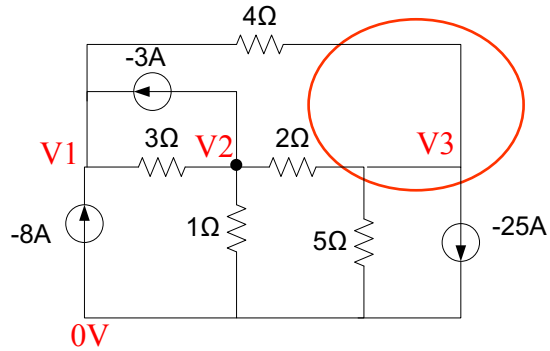

At node V_3

$$\frac{V_3 - V_2}{2} + \frac{V_3 - V_1}{4} - 25 + \frac{V_3 - 0}{5} = 0$$

$$10V_3 - 10V_2 + 5V_3 - 5V_1 - 500 + 4V_3 = 0$$

$$-5V_1 - 10V_2 + 19V_3 = 500$$

Node Voltage Example – Solution

$$7V_1 - 4V_2 - 3V_3 = -132$$

$$-2V_1 + 11V_2 - 3V_3 = 18$$

$$-5V_1 - 10V_2 + 19V_3 = 500$$

Answer:

$$V_1 = 0.956V$$

$$V_2 = 10.576V$$

$$V_3 = 32.132V$$

Section 3.2 Summary

- You learned to apply the node-voltage method to analyze an electric circuit of any configuration, so long as it is linear and planar.