

Chapter 5.5

Response of the RC circuit

Part I


Engr228 - Circuit Analysis
Spring 2020

Dr Curtis Nelson

Section 5.5 Objective

- Learn to:
 - Analyze the transient responses of RC circuits.


Capacitors

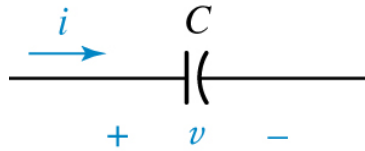

- The unit of capacitance is the Farad (F);
- 1 F = 1 Amp-Second/Volt = 1 Coulomb/Volt;
- The governing voltage and current relationship is:

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

DC Characteristics of a Capacitor

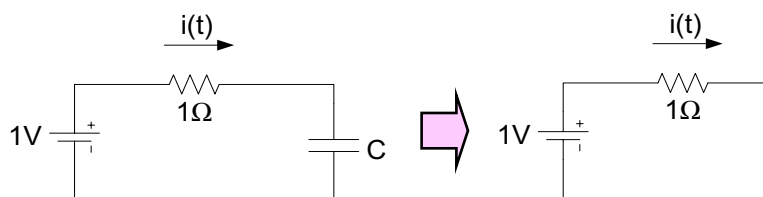


The capacitor acts like an “open circuit” at DC because the time rate of change of voltage is zero so, no current can flow through it.


$$i_C(t) = C \frac{dv_C(t)}{dt}$$

Voltage-Current Relationship in a Capacitor

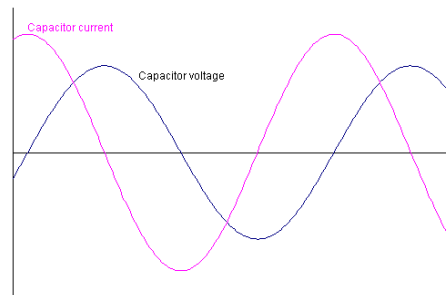Current and voltage in a capacitor are not in phase with each other. **For sinusoidal waves, the voltage across a capacitor lags the current through it by 90°.** (In other words, the current leads the voltage by 90°.) In the diagram below, the tall purple waveform represents the current through a capacitor and the shorter blue waveform represents the voltage across a capacitor.




Inductors

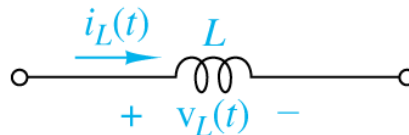

- The inductor is often called a coil because physically coiling a wire greatly increases its inductance, especially if it is coiled around a magnetic material.
- The governing voltage and current relationship is:

$$v_L(t) = L \frac{di(t)}{dt}$$

DC Characteristics of Inductors

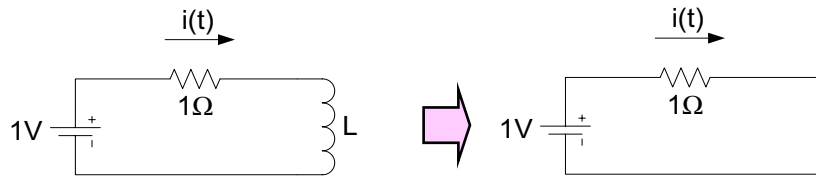


The inductor acts like a “short circuit” at DC because the time rate of current change is equal to zero.

$$v_L(t) = L \frac{di(t)}{dt}$$

Voltage-Current Relationship in an Inductor

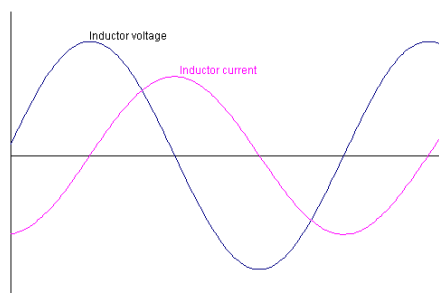Current and voltage in an inductor are not in phase with each other. **For sinusoidal waves, the voltage across an inductor leads the current through it by 90°.** (In other words, the current lags the voltage by 90°.) In the diagram below, the tall blue waveform represents the voltage across an inductor and the shorter purple waveform represents the current through the inductor.




Types of First-Order Responses

- Circuits with one storage device (one capacitor or one inductor), are called **first-order circuits**.
- Their response to source excitations is composed of two parts:
 - Transient response, natural response, homogeneous solution (temporary position change)
 - Fades to zero over time.
 - Forced response, steady-state response, particular solution (permanent position change)
 - Follows the input;
 - Independent of time passed.

Mechanical Analogue

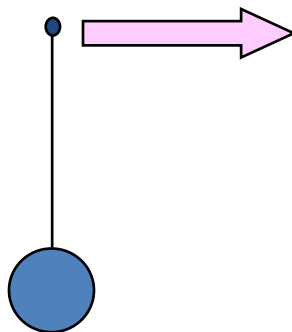
I am holding a ball with a rope attached. What is the movement of the ball if I move my hand to another point?




Two movements:

1. Oscillation
2. Forced position change


Mechanical Analogue

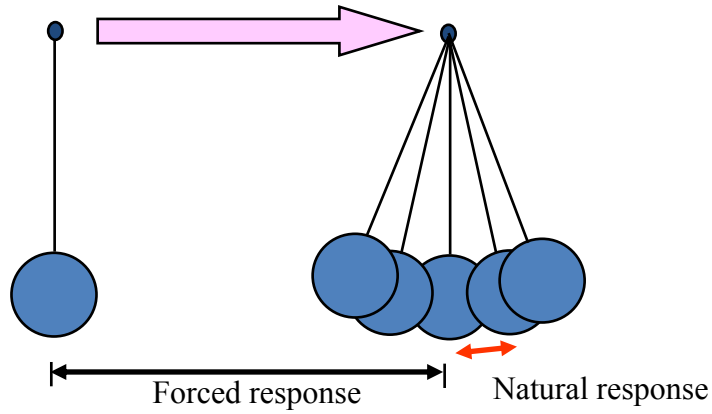

Source-Free RC Circuits

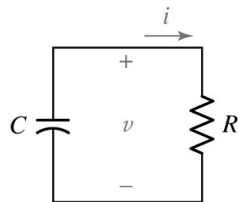

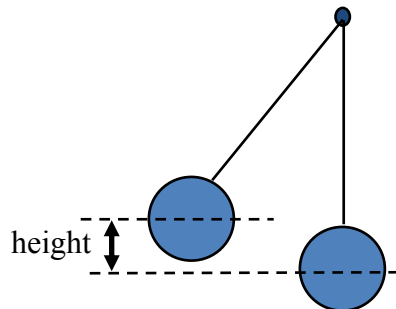Capacitor C has energy stored so initial voltage is V_0 or $V(0^-)$




Similar to a pendulum that is at a height h where the potential energy is nonzero.

Source-Free RC Circuits

- The derivation for the capacitor voltage is a node equation. To be consistent with the direction of assigned voltage:

$$\frac{v(t)}{R} + C \frac{dv(t)}{dt} = 0$$
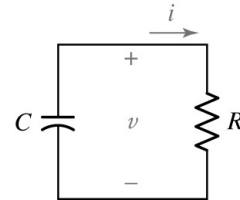
$$\frac{dv(t)}{dt} + \frac{v(t)}{RC} = 0$$



- There are 2 ways to solve this first-order equation:
 - Assume the form of a solution.
 - Direct integration.

Solving Source Free RC Circuits

Assume the solution is of the form $v(t) = Ae^{st}$
where A and s are the constants that need to be solved for.

Substitute $v(t) = Ae^{st}$ into the equation: $\frac{dv(t)}{dt} + \frac{v(t)}{RC} = 0$

$$v_C(t) = V_{C0} e^{-\frac{t}{RC}} = V_{C0} e^{-\frac{t}{\tau}}$$

Time Constant


The term RC is called the **time constant** and is denoted by the symbol τ (*tau*).

$$\tau_c = RC \quad \text{Units: seconds}$$

One time constant is defined as the amount of time required for the output to go from its initial value $V(0)$ to 36.8% of its initial value.

$$e^{-1} = 0.368$$

Time Constant Graph

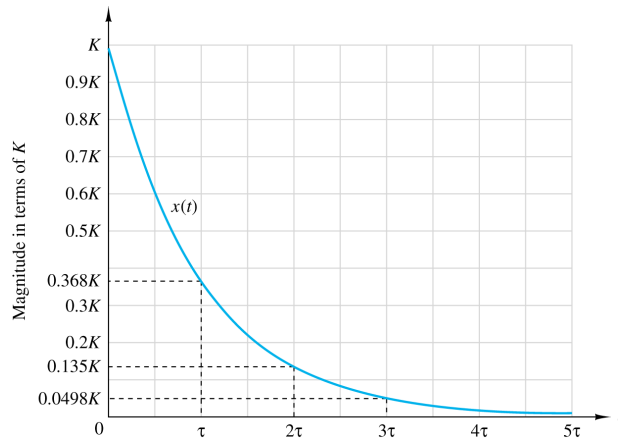


1st Order Response Observations

- The voltage across a capacitor is the same *prior to* and *after* a switch at $t = 0$ seconds because this quantity cannot change instantaneously.
- Resistor voltage (or current) prior to the switch $v(0^-)$ can be different from the voltage (or current) after the switch $v(0^+)$.
- **All** voltages and **all** currents in an RC circuit follow the same natural response $e^{-t/\tau}$.

General RC Circuits

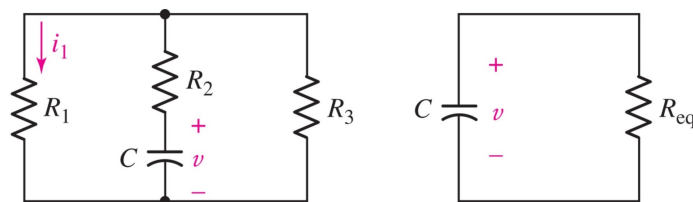
The time constant of a single-capacitor circuit will be $\tau = R_{eq}C$ where R_{eq} is the resistance seen by the capacitor.



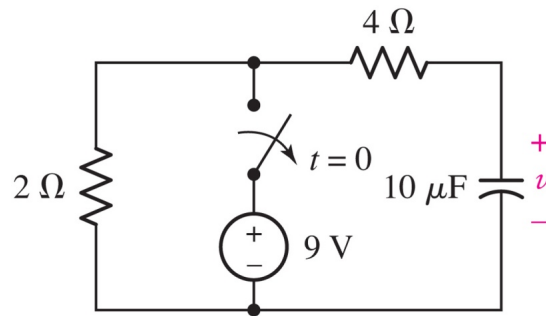Example: $R_{eq} = R_2 + R_1 R_3 / (R_1 + R_3)$

The Source Free RC Circuit


Assume the switch is in the closed position for a long time for $t < 0$. Find the voltage $v(t)$ at $t = 200\mu\text{s}$.



$$v(t) = 321\text{mV at } t = 200\mu\text{s}$$

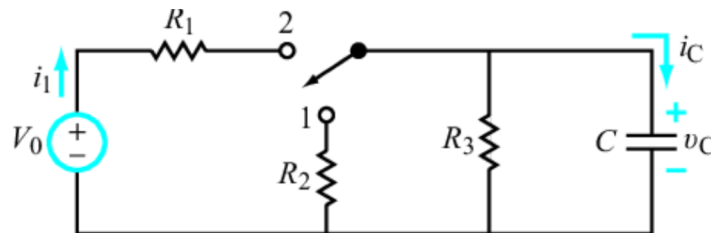Example 5.5.2 Zybooks


After having been in position 2 for a long time, the switch is moved to position 1 at $t = 0$. Given that $V_0 = 12\text{ V}$, $R_1 = 30\text{ k}\Omega$, $R_2 = 120\text{ k}\Omega$, $R_3 = 60\text{ k}\Omega$, and $C = 100\mu\text{F}$, determine $v_C(t)$ for all time.



$$v_C(t) = 8e^{-.25t}$$

Example Problem

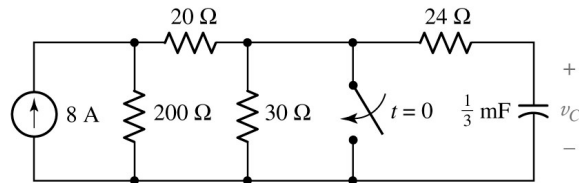- (a) Find $v_C(t)$ for all time in the circuit below.
(b) At what time is $v_C = 0.1v_C(0)$?



$$v_C(0) = 192V \quad v_C(t) = v_C(0)e^{-125t}$$
$$v_C = 0.1v_C(0) \text{ when } t = 18.42mS$$

Section 5.5 Summary

- You learned to:
 - Analyze the transient responses of RC circuits.