

SCORE KEY /30

Rules of engagement:

- This exam is open book:
 - You **may** use all materials at your disposal including the internet, Zybooks, textbooks, lecture notes and videos, example problems and your calculator.
 - You **may not** consult anyone other than yourself about anything related to this test until 5pm on Wednesday, May 27.
- You are allocated a total of 3 hours, **in one sitting**, to work on this exam. You must monitor yourself and stay within this time frame. Once you open the test, you must submit the finished product to the D2L drop box **test2** within 3 hours.
- The drop box will close at 5pm on Wednesday, May 27 and late submissions will not be accepted.
- You may email me your test directly, but only if D2L is not available.
- Students with documented disabilities – I am willing to help you in any way I can, but you are responsible for arranging for your allowed accommodations, including appropriate time extensions.
- I will be generally available, by email only, during the hours you can take the exam, except for 8pm – 6am.
- You will be asked to sign your name below. When you do, I will take this to indicate that you abided by these rules. You must sign your name to get a non-zero grade on the exam.

NAME _____

8 pts First-Order Circuits

The switch in the figure at the right has been in position 1 for a very long time. It is moved to position 2 at $t = 0$ seconds. The component values are:


$$I_1 = 4 \text{ mA}$$

$$I_2 = 6 \text{ mA}$$

$$R_1 = 3 \text{ k}\Omega$$


$$R_2 = 6 \text{ k}\Omega$$

$$C = 0.2 \text{ mF}$$

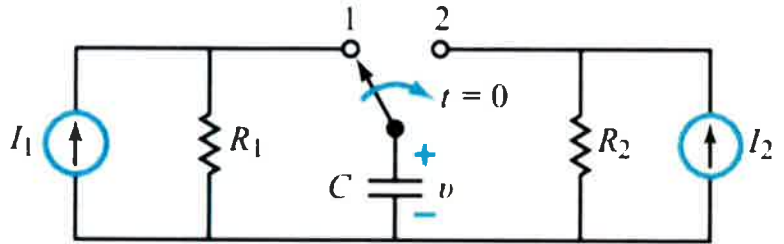

2 pts Find the initial capacitor voltage $V_C(0)$.

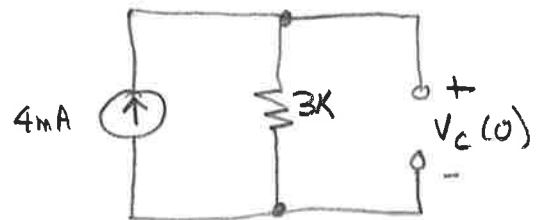
$$V_C(0) = (4 \text{ mA})(3 \text{ k}) = \boxed{12 \text{ V}}$$



2 pts Find the time constant (τ) of this circuit for $t > 0$ seconds.

$$\tau = RC = (0.2 \times 10^{-3})(6 \text{ k})$$

$$= \boxed{1.2 \text{ seconds}}$$

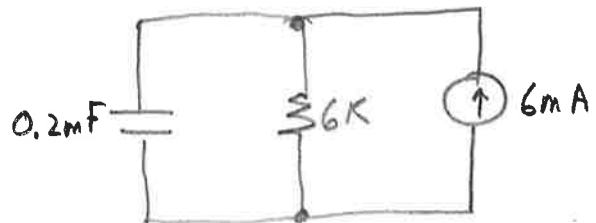

2 pts Find the voltage across the capacitor at time infinity, $V_C(\infty)$.

$$V_C(\infty) = (6 \text{ mA})(6 \text{ k}) = \boxed{36 \text{ V}}$$

2 pts Find an expression for $V_C(t)$ for $t > 0$ seconds.

$$V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)]e^{-t/RC}$$

$$= 36 + [12 - 36]e^{-\frac{5}{6}t}$$

$$= \boxed{36 - 24e^{-\frac{t}{1.2}} \text{ V}}$$



10 pts Second-Order Circuits

The switch in the circuit at the right has been closed since Noah built the ark. It is opened at $t = 0$ seconds.

2 pt Find $V_C(0)$

$$V_C(0) = (1)(4.7k)$$

$$= \boxed{4700V}$$

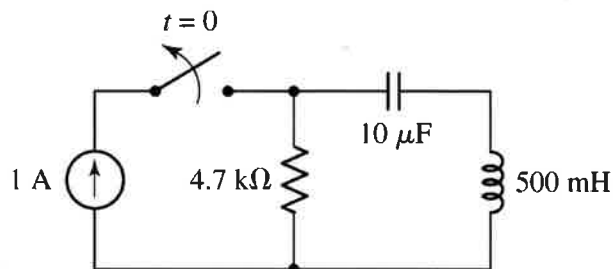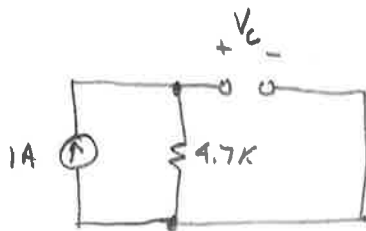
2 pt Find $I_L(0)$

$$I_L(0) = \boxed{0A}$$

1 pt Find $I_L(\infty)$

Because the capacitor is an open circuit,

$$I_L(\infty) = \boxed{0A}$$

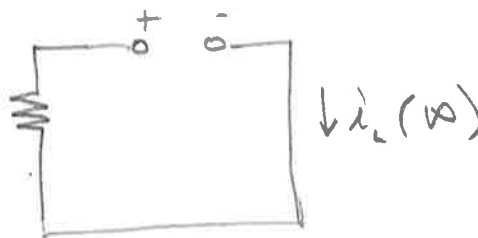2 pts Find α and ω_0

Series RLC circuit

$$\alpha = \frac{R}{2L} = \boxed{4700 \text{ Rad/sec}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \boxed{447.2 \text{ Rad/sec}}$$

1 pt Is this system overdamped, critically damped, or underdamped?

$$\alpha > \omega_0 \text{ so } \boxed{\text{overDamped}}$$

2 pts Find s_1 and s_2 (the roots of the characteristic equation)

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4700 \pm \sqrt{4700^2 - 447.2^2}$$

$$= -4700 \pm 4679$$

$$\boxed{s_{1,2} = -21.3 \text{ and } -9379}$$

8 pts Phasor Circuits

The following four problems are worth **one point each** and refer to the figure at the right. Circle the best answer.

The DC component of the voltage source is:

- a) 0 V
- b) 8 V
- c) 2000π V
- d) Cannot be determined
- e) None of the above

The frequency of the source in Hz is:


- a) 2000π
- b) 1000
- c) 8
- d) Impossible to tell
- e) None of the above

The value of capacitance is:

- a) 0.159 mF
- b) 0.159 F
- c) 0.159 μ F
- d) Impossible to tell
- e) None of the above

The phase difference between the resistor voltage and current ($\theta_v - \theta_i$) is:

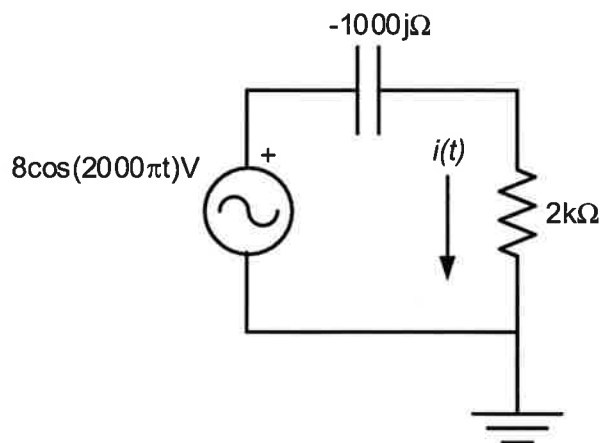- a) 90°
- b) -90°
- c) 180°
- d) 0°
- e) None of the above



4 pts Calculate the voltage across the capacitor and express your answer in *polar, rectangular, and sinusoidal* forms.

using voltage divider,

$$V_C = \frac{V_s Z_{CAP}}{Z_{CAP} + R} = \frac{8 \angle 0 (-1000j)}{-1000j + 2000}$$

$$V_C = 3.578 \angle -63.43^\circ \text{ V}$$

$$= 1.60 - 3.20j \text{ V}$$

$$= 3.578 \cos(2000\pi t - 63.43^\circ) \text{ V}$$

4

6 pts Phasor CircuitsFind the value of ω such that $v_a(t)$ and $i_s(t)$ are in-phase.

Component values are:


$R_1 = 5\Omega$

$R_2 = 3\Omega$

$L = 35 \text{ mH}$

$C = 7 \text{ mF}$

$i_s(t) = 10\cos(100t) \text{ mA}$

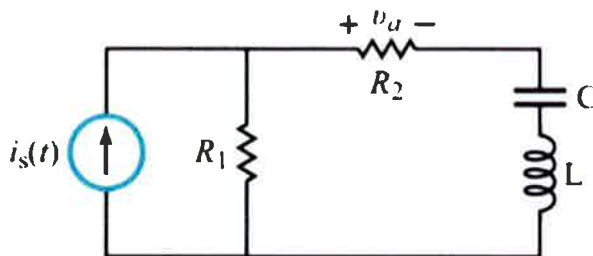

the Quick:

in order for i_s and v_a to be in phase (say 0°), then the phase of the Capacitor has to cancel the phase of the inductor, or $\frac{1}{j\omega C} = j\omega L$

$$\text{Solving, } \omega = \frac{1}{\sqrt{LC}} = \boxed{63.89 \text{ Rad/sec}}$$

the long way:


$$v_a = i_{R_2} R_2 = \frac{i_s (R_1)}{R_1 + R_2 + Z_{cap} + Z_{ind}} \quad (\text{using current divider})$$

$$[R_1 + R_2 + Z_{cap} + Z_{ind}] v_a = R_1 i_s$$

or

$$[R_1 + R_2 + \frac{1}{j\omega C} + j\omega L] v_a \angle \theta_{v_a} = R_1 i_s \angle \theta_{i_s}$$

$$\text{for } \theta_{v_a} = \theta_{i_s}, \quad \angle [R_1 + R_2 + \frac{1}{j\omega C} + j\omega L] = 0$$

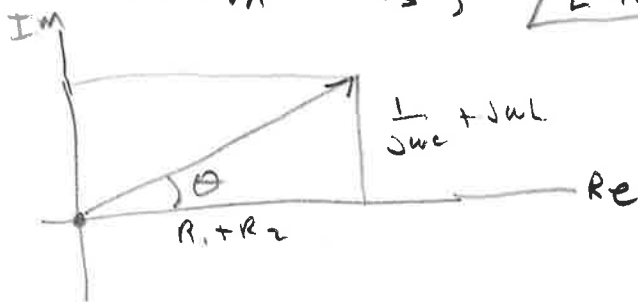For that \angle to be 0° ,

$$\frac{1}{j\omega C} = -j\omega L$$

$$\text{OR } \omega = \frac{1}{\sqrt{LC}} = \boxed{63.89 \text{ Rad/sec}}$$