

Circuits Review

Engr325


Instrumentation

Dr Curtis Nelson


Voltage, Current, and Resistance



Ohm's Law

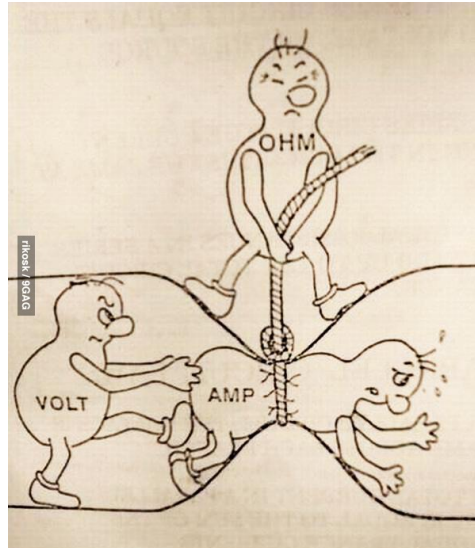


Circuits Pie Chart

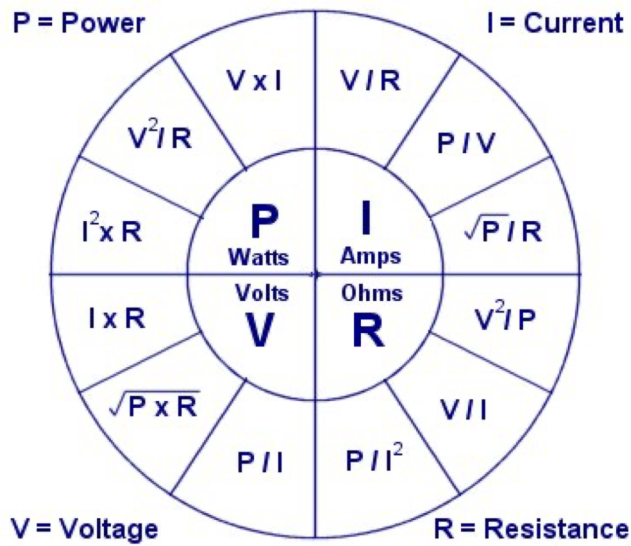

Voltage Division

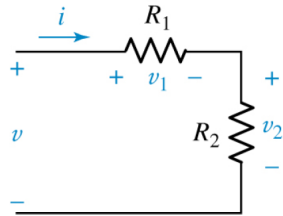Resistors in series “share” the voltage applied to them.



$$i = \frac{v}{R_1 + R_2}$$


$$v_2 = i R_2 = \left(\frac{v}{R_1 + R_2} \right) R_2$$

$$\begin{aligned} v &= v_1 + v_2 \\ &= i(R_1 + R_2) \end{aligned}$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

Voltage Divider Example

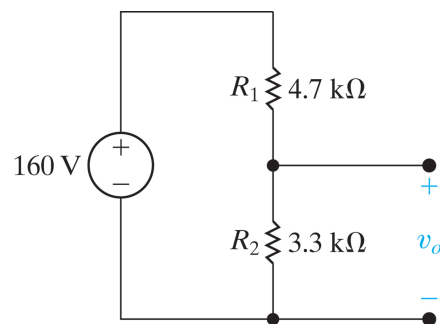
Find the voltage v_o and the power dissipated in both resistors.



$$\begin{aligned} v_o &= 66V \\ P_{R1} &= 1.88W \\ P_{R2} &= 1.32W \end{aligned}$$


Instrument Loading

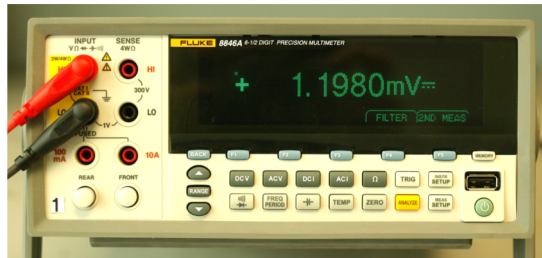- The concepts of Input and Output Impedance (Z_{in} and Z_{out})
- Fluke 8846A Specs:
 - [Fluke 8846A Specifications](#)



Measuring Voltage, Current, and Resistance

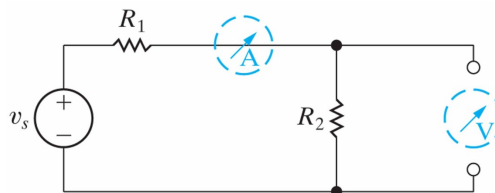
- An ideal meter has no effect on the circuit variable being measured.
- That means when an ideal *ammeter* is *placed in series* to measure the current through an element, it should have an equivalent resistance of 0Ω .
- That means when an ideal *voltmeter* is *placed in parallel* to measure the voltage across an element, it should have an equivalent resistance of $\infty \Omega$.



Instrument Loading - Example

Find v_o if the meter placed in parallel with R_2 has an input resistance of:

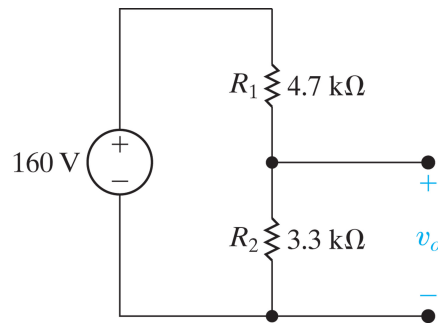- a) $10\text{M}\ \Omega$.
- b) $100\text{k}\ \Omega$.
- c) $1\text{k}\ \Omega$.



$$v_{0a} = 65.87V$$

$$v_{0b} = 64.75V$$

$$v_{0c} = 22.46V$$