

# Digital Logic

# Homework #10

**DUE:** Monday, November 4

## **Objective**

Understand the operation of basic sequential circuit elements.

## **Task**

Wire up your design of the PU latch from Homework #9. Report on your success and at least two things you learned in doing this exercise.

## **Turn In**

**Staple this assignment sheet** to your solutions which are to be done in accordance with the school of engineering homework guidelines posted on the course web page.