

Engr354: Digital Logic Circuits

Chapter 2: Introduction to Logic Circuits

Dr. Curtis Nelson

Chapter 2 Objectives

- Define and illustrate basic logic functions and circuits;
- Present Boolean algebra for dealing with logic functions;
- Illustrate logic gates and synthesis of simple circuits;
- Review CAD tools and the VHDL hardware description language.


Binary Logic Circuits

- Logic circuits perform operations on digital signals;
- These circuits are implemented using electronic components;
- Binary logic circuits can be found in one of two states
 - 0 or 1;
 - off or on;
 - down or up;
 - not asserted or asserted;
 - etc.

Switch Representation




(a) Two states of a switch

 


(b) Symbol for a switch

Switch Example

$$L(x) = x$$

 


(a) Simple connection to a battery

 

(b) Using a ground connection as the return path

Two Basic Functions

 


$$L(x_1, x_2) = x_1 \cdot x_2$$

$$L = 1 \text{ if } x_1 = 1 \text{ and } x_2 = 1$$

$$L = 0 \text{ otherwise}$$

 (a) The logical AND function (series connection)




$$L(x_1, x_2) = x_1 + x_2$$

$$L = 1 \text{ if } x_1 = 1 \text{ or } x_2 = 1$$

$$L = 0 \text{ otherwise}$$

(b) The logical OR function (parallel connection)

A Series-Parallel Example

 

$$L(x_1, x_2, x_3) = (x_1 + x_2) \cdot x_3$$

Truth Tables

- All combinations of inputs on the left;
- Outputs on the right;
- 2-input **AND** and **OR** functions shown below.


| x_1 | x_2 | $x_1 \cdot x_2$ | $x_1 + x_2$ |
|-------|-------|-----------------|-------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

AND OR


3-Input And and Or Functions

| x_1 | x_2 | x_3 | $x_1 \cdot x_2 \cdot x_3$ | $x_1 + x_2 + x_3$ |
|-------|-------|-------|---------------------------|-------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Basic Gates

 

(a) AND gates

 


(b) OR gates




(c) NOT gate

Example Using Basic Gates

 

Sequencing of Inputs

 


Network that implements $f = \bar{x}_1 + x_1 \cdot x_2$

| x_1 | x_2 | $f(x_1, x_2)$ |
|-------|-------|---------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |


Truth table for f

Timing Diagram

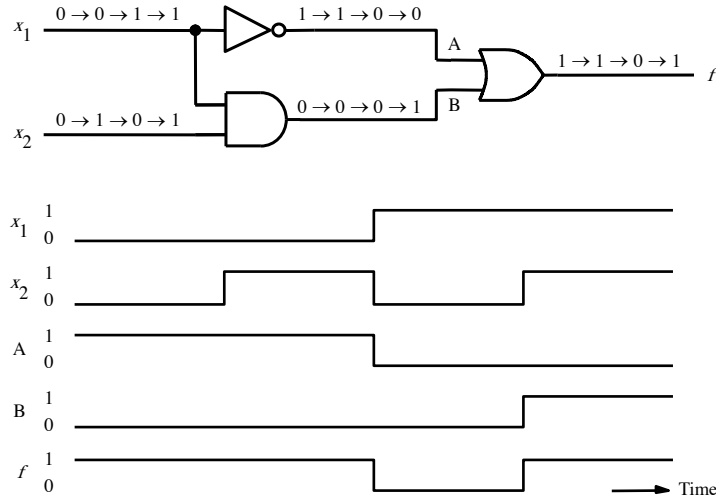

Timing diagram

Example

 

Network that implements $g = \bar{x}_1 + x_2$

- Draw a timing diagram below:

Boolean Algebra

- In 1849, George Boole published a scheme for describing logical thought and reasoning;
- In 1930s, Claude Shannon applied Boolean algebra to describe circuits built with switches;
- Boolean algebra provides the mathematical foundation for digital design.

Notation

- **INVERSION:** $\bar{x} = x' = !x = \text{NOT } x$
 $\overline{f(x_1, x_2)} = \overline{x_1 + x_2} = (x_1 + x_2)' = !(x_1 + x_2)$
 $= \text{NOT}(x_1 + x_2)$
- **AND:** $x_1 \cdot x_2 = x_1 \wedge x_2 = x_1 x_2$
- **OR:** $x_1 + x_2 = x_1 \vee x_2$

Precedence of Operations

- In the absence of parentheses, operations are performed in this order: NOT, AND, OR

$$x_1 x_2 + x_1' x_2' = (x_1 x_2) + ((x_1') (x_2'))$$

Principle of Duality

- On the following pages, axioms and theorems are listed in pairs to show the principle of duality;
- Given a logic expression, its *dual* is found by exchanging + and • operators and 0's and 1's;
- The dual of any true statement is **always** true.

Axioms of Boolean Algebra

- | | |
|----------------------------------|-------------------------------|
| 1. $0 \cdot 0 = 0$ | $1 + 1 = 1$ |
| 2. $1 \cdot 1 = 1$ | $0 + 0 = 0$ |
| 3. $0 \cdot 1 = 1 \cdot 0 = 0$ | $1 + 0 = 0 + 1 = 1$ |
| 4. if $x = 0$ then $\bar{x} = 1$ | if $x = 1$ then $\bar{x} = 0$ |

Single-Variable Theorems

- | | |
|-----------------------------|-------------------|
| 5. $x \cdot 0 = 0$ | $x + 1 = 1$ |
| 6. $x \cdot 1 = x$ | $x + 0 = x$ |
| 7. $x \cdot x = x$ | $x + x = x$ |
| 8. $x \cdot \bar{x} = 0$ | $x + \bar{x} = 1$ |
| 9. $\overline{\bar{x}} = x$ | |

2- and 3-Variable Properties

10a. $x \cdot y = y \cdot x$ Commutative

10b. $x + y = y + x$

11a. $x \cdot (y \cdot z) = (x \cdot y) \cdot z$ Associative

11b. $x + (y + z) = (x + y) + z$

12a. $x \cdot (y + z) = x \cdot y + x \cdot z$ Distributive

12b. $x + y \cdot z = (x + y) \cdot (x + z)$

2- and 3-Variable Properties

13a. $x + x \cdot y = x$ Absorption

13b. $x \cdot (x + y) = x$

14a. $x \cdot y + x \cdot \bar{y} = x$ Combining

14b. $(x + y) \cdot (x + \bar{y}) = x$

15a. $\overline{x \cdot y} = \bar{x} + \bar{y}$ DeMorgan's Thm

15b. $\overline{x + y} = \bar{x} \cdot \bar{y}$

16. $x + \bar{x} \cdot y = x + y$ $x \cdot (\bar{x} + y) = x \cdot y$

Truth Table Proof of DeMorgan's Theorem

15a. $\overline{x \cdot y} = \bar{x} + \bar{y}$ DeMorgan's Theorem

| x | y | $x \cdot y$ | $\overline{x \cdot y}$ | \bar{x} | \bar{y} | $\bar{x} + \bar{y}$ |
|-----|-----|-------------|------------------------|-----------|-----------|---------------------|
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

⏟
⏟

LHS
RHS

Boolean Algebra Examples

1) $(a + b)(a' + b') =$

2) $a'b'c' + a'b'c + ab'c' + ab'c =$

3) $a'b'c' + a'b'c + a'bc' + abc' + ab'c' + ab'c =$

1) $ab' + ba'$

2) b'


3) $b' + c'$

Synthesis


- Synthesis is the process of creating a circuit from a specification, i.e. a truth table, schematic, VHDL code, etc.

| x_1 | x_2 | $f(x_1, x_2)$ |
|-------|-------|---------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Two Implementations of the Function f

 

(a) Sum-of-products form

 

(b) Minimal-cost realization

Minterms and Maxterms

- Minterms
 - For a function of n variables, a product term in which each of the n variables appears once is called a minterm
 - Variables may appear in complemented or uncomplemented form;
 - A given minterm is formed by including x_i if $x_i = 1$ and by including $\text{not}(x_i)$ if $x_i = 0$.
- Maxterms (Principle of duality applies)
 - For a function of n variables, a sum term in which each of the n variables appears once is called a maxterm
 - Variables may appear in complemented or uncomplemented form.
 - A given maxterm is formed by including x_i if $x_i = 0$ and by including $\text{not}(x_i)$ if $x_i = 1$.

Three-Variable Minterm and Maxterm Table

| Row number | x_1 | x_2 | x_3 | Minterm | Maxterm |
|------------|-------|-------|-------|-------------------------------------|---|
| 0 | 0 | 0 | 0 | $m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$ | $M_0 = x_1 + x_2 + x_3$ |
| 1 | 0 | 0 | 1 | $m_1 = \bar{x}_1\bar{x}_2x_3$ | $M_1 = x_1 + x_2 + \bar{x}_3$ |
| 2 | 0 | 1 | 0 | $m_2 = \bar{x}_1x_2\bar{x}_3$ | $M_2 = x_1 + \bar{x}_2 + x_3$ |
| 3 | 0 | 1 | 1 | $m_3 = \bar{x}_1x_2x_3$ | $M_3 = x_1 + \bar{x}_2 + \bar{x}_3$ |
| 4 | 1 | 0 | 0 | $m_4 = x_1\bar{x}_2\bar{x}_3$ | $M_4 = \bar{x}_1 + x_2 + x_3$ |
| 5 | 1 | 0 | 1 | $m_5 = x_1\bar{x}_2x_3$ | $M_5 = \bar{x}_1 + x_2 + \bar{x}_3$ |
| 6 | 1 | 1 | 0 | $m_6 = x_1x_2\bar{x}_3$ | $M_6 = \bar{x}_1 + \bar{x}_2 + x_3$ |
| 7 | 1 | 1 | 1 | $m_7 = x_1x_2x_3$ | $M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$ |

Sum-of-Products (SOP) Form

- A function f can be represented by an expression that is a sum of minterms.
- For example, the function below could be represented as

$$f(x_1, x_2, x_3) = !x_1!x_2x_3 + x_1!x_2!x_3 + x_1!x_2+x_3 + x_1x_2!x_3$$

- Using short hand notation

$$f(x_1, x_2, x_3) = m_1+m_4+m_5+m_6 \text{ or}$$

$$f(x_1, x_2, x_3) = \sum m(1,4,5,6)$$

| Row number | x_1 | x_2 | x_3 | $f(x_1, x_2, x_3)$ |
|------------|-------|-------|-------|--------------------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 1 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 0 |

Product-of-Sums (POS) Form

- The same function f can be represented by an expression that is a product of sums of maxterms (this follows from DeMorgan's laws).
- For example, the function below could also be represented as

$$f(x_1, x_2, x_3) = (x_1+x_2+x_3)(x_1+!x_2+x_3)(x_1+!x_2+!x_3)(!x_1+!x_2+!x_3)$$

- Using short hand notation,

$$f(x_1, x_2, x_3) = M_0M_2M_3M_7 \text{ or}$$

$$f(x_1, x_2, x_3) = \prod M(0,2,3,7)$$

| Row number | x_1 | x_2 | x_3 | $f(x_1, x_2, x_3)$ |
|------------|-------|-------|-------|--------------------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 1 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 0 |

Canonical


- A logic expression is said to be canonical if each term contains all variables, either complemented or uncomplemented.

2-Variable Example


- Synthesize the following function using four different, but equivalent, expressions
 - Minterm form;
 - Maxterm form;
 - Canonical form;
 - Minimum form.

| x_1 | x_2 | $f(x_1, x_2)$ |
|-------|-------|---------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

NAND and NOR Gates

 


(a) NAND gates

 


 (b) NOR gates

DeMorgan's Theorems in Terms of Logic Gates



 
(a) $\overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$




(b) $\overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$

- Function vs. Gate

SOP Implementation Using NAND Gates

 

POS Implementation Using NOR Gates

 


Example

- Synthesize the following function using four different, but equivalent, expressions
 - Minterm form;
 - Maxterm form;
 - Canonical form;
 - Minimum form.


| x_1 | x_2 | x_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Canonical SOP Implementation

 

(a) Sum-of-products realization

Canonical POS Implementation

 

(b) Product-of-sums realization

Minimal Implementation

Textbook Problem 2.28 Brown 3rd Ed.

- Design the simplest circuit that has three inputs, a, b, and c, which produces an output value of 1 whenever two or more of the input variables have the value of 1; otherwise, the output has to be 0.
- Implement the circuit three different ways
 - With minimum *and/or* logic;
 - With *nand* logic gates only;
 - With *nor* logic gates only.

Design Entry

- Truth tables
 - Practical only for small circuits.
- Schematic capture
 - Interconnect symbols in some *library*;
 - Facilitates *hierarchical design*;
 - Good for medium-to-large circuits;
 - Difficult to use for very large circuits.

Design Entry - Continued

- Hardware description languages (HDL's)
 - Similar to a programming language;
 - VHDL and Verilog HDL are IEEE standards;
 - Provide design *portability*;
 - Allow for sharing and design reuse;
 - Support hierarchical design;
 - Can be combined with schematics.


Logic Synthesis

- *Logic synthesis*, or *logic optimization*, is the process of translating a truth table, schematic, or VHDL code into a network of logic gates;
- What makes a circuit good depends on the application – do you want to optimize for speed, area, power?

Simulation

- A *functional simulator* is used to determine if a designed circuit operates correctly from a **logic** perspective.
- **Circuit verification**
 - User provides input values to the circuit;
 - Simulator determines the circuit response;
 - User checks responses against desired outputs.
- A *timing simulator* is used to check correctness by incorporating the **electrical** characteristics of a logic design in addition to the *logical* performance. This simulation requires
 - Technology mapping;
 - Layout synthesis.

A Typical CAD System

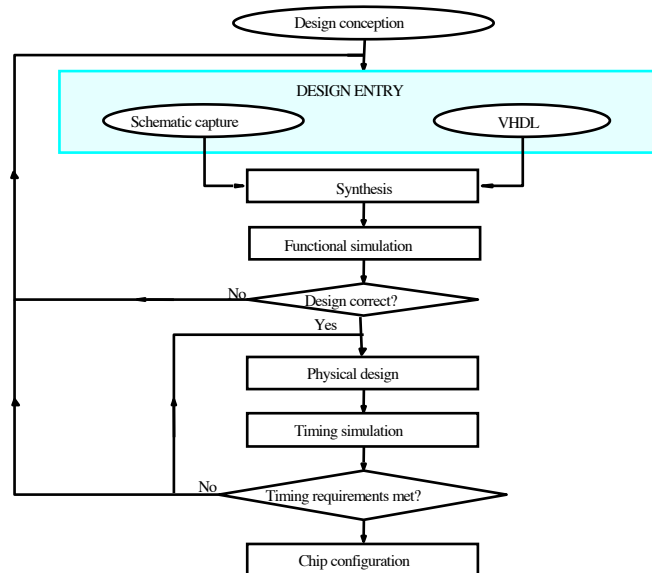


VHDL

- VHDL - Very high speed integrated circuit hardware description language;
- Original IEEE standard adopted in 1987;
- Revised standard in 1993;
- Originally used for documentation and simulation;
- Now, it is also used for synthesis;
- Very complex language, but only a subset is needed to design a wide range of circuits.

Representing Digital Signals in VHDL

- Each logic signal in a circuit is a data object in VHDL code;
- Data objects in VHDL are assigned *types*;
- A simple type is BIT which is used for objects that can take only 2 values: 0 or 1.

A Simple Logic Function Example

 

```
ENTITY example1 IS
    PORT ( x1, x2, x3 : IN BIT ;
          f          : OUT BIT ) ;
END example1 ;

ARCHITECTURE LogicFunc OF example1 IS
BEGIN
    f <= (x1 AND x2) OR (NOT x2 AND x3) ;
END LogicFunc ;
```

Chapter 2 Summary

- Defined and illustrated basic logic functions and circuits;
- Presented Boolean algebra for dealing with logic functions;
- Illustrated logic gates and synthesis of simple circuits;
- Reviewed CAD tools and the VHDL hardware description language.