

Engr354: Digital Logic Circuits

Chapter 7

Sequential Logic Elements

Curtis Nelson

Sequential Logic Elements

In this chapter you will learn about

- Logic circuits that can store information;
- Basic cells, latches, and flip-flops;
- State diagrams;
- Design techniques for circuits that use flip-flops.

Circuit Types

- **Combinational** – output depends only on the input.
- **Sequential** – output depends on input and past behavior
 - Requires use of storage elements;
 - Contents of the storage elements is called *state*;
 - Circuit goes through a sequence of states as a result of changes in inputs.
- **Synchronous** – controlled by a clock.

Clock Signals

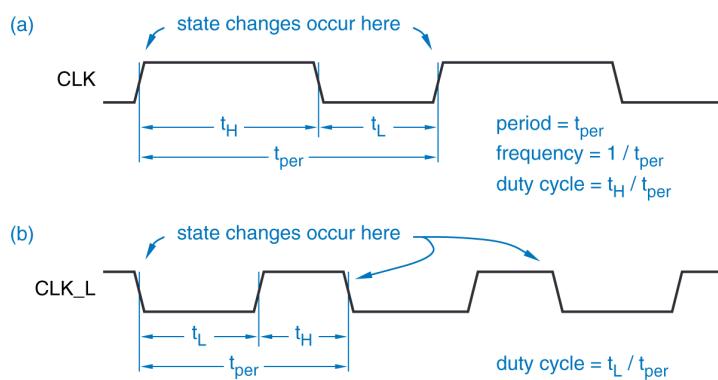


Figure 7-1
Clock signals: (a) active high; (b) active low.

A Bistable Memory Element

- Bistable – possessing two stable states.


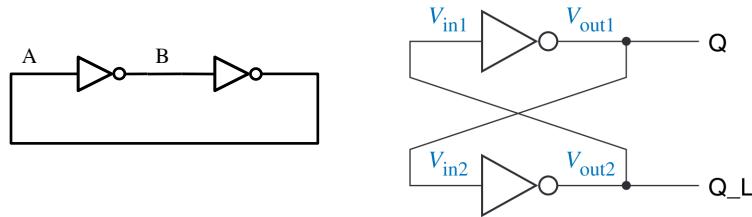


Figure 7-2
A pair of inverters forming a bistable element.



A Set/Reset (SR) Memory Element

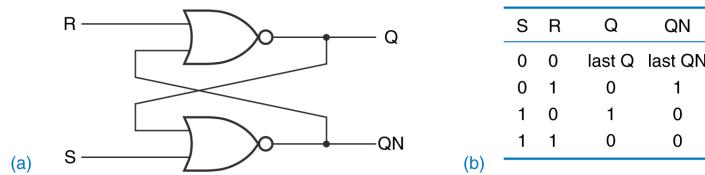- Called a **Basic Cell**;
- NOR centered Basic Cell:
 - Circuit (a), Function table (b).
- Inputs are active when they are **high**;
- Blocking side inputs.




Typical Operation of a *Basic Cell*

- Reset, clear.
- Set, preset.

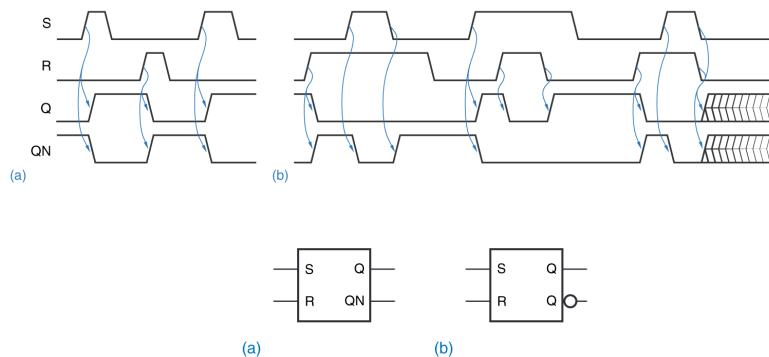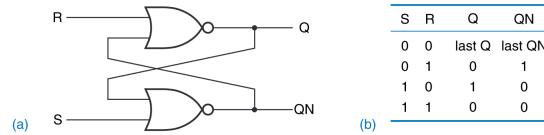

NOR-Centered (Reset Dominant) Basic Cell

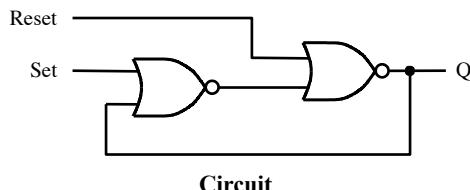


S	R	Action	Q_{n+1}
0	0	hold	Q_n
0	1	reset	0
1	0	set	1
1	1	reset	0

Operation Table

$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
0 → 0	0	ϕ
0 → 1	ϕ	1
1 → 0	1	0
1 → 1	ϕ	1
	ϕ	0


Excitation Table

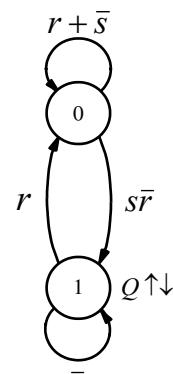

State Diagram

NAND-Centered (Set Dominant) Basic Cell

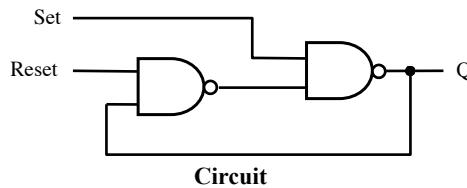- Inputs are active low (when they are *asserted*);
- Operation table indicates assertion, not voltage, levels.




S	R	Action	Q_{N+1}
0	0	hold	Q_N
0	1	reset	0
1	0	set	1
1	1	set	1

Operation Table

$Q_n \rightarrow Q_{n+1}$		Inputs	
		S	R
0	0	0	ϕ
0	1	1	ϕ
1	0	0	1
1	1	1	ϕ
		ϕ	0

Excitation Table

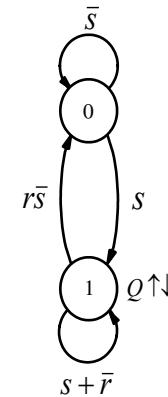

Combined Form of the Basic Cell

$Q_n \rightarrow Q_{n+1}$		Inputs	
		S	R
0	0	0	ϕ
0	1	1	ϕ
1	0	0	1
1	1	1	ϕ
		ϕ	0


**Excitation Table
NAND-centered**

$Q_n \rightarrow Q_{n+1}$		Inputs	
		S	R
0	0	0	ϕ
0	1	1	0
1	0	ϕ	1
1	1	ϕ	0

**Excitation Table
NOR-centered**

$Q_n \rightarrow Q_{n+1}$		Inputs	
		S	R
0	0	0	ϕ
0	1	1	0
1	0	0	1
1	1	ϕ	0

**Excitation Table
Combined Form**

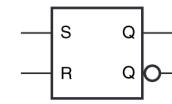


Designing Latches - A Model


- Latch - a logic circuit that transfers the input state to the output state when the *clock* signal is high and latches and holds the input when the *clock* signal goes low.

$Q_0 \rightarrow Q_{n+1}$	Inputs	
	S	R
0 → 0	0	ϕ
0 → 1	1	0
1 → 0	0	1
1 → 1	ϕ	0


Excitation Table
Combined Form

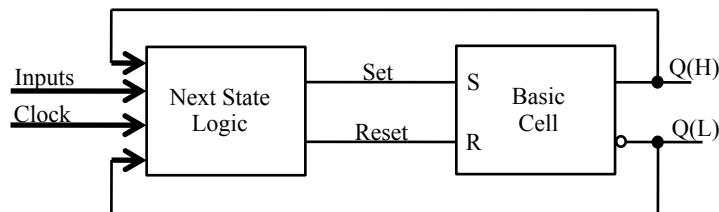


Design of a Clocked D (Data) Latch

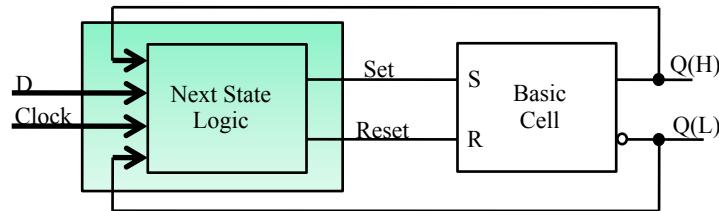

Design of a Clocked D Latch

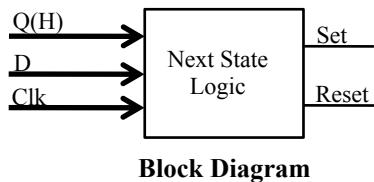

Clk	D	Qn	Qn+1	Set	Reset
0	0	0	0	0	ϕ
0	0	1	1	ϕ	0
0	1	0	0	0	ϕ
0	1	1	1	ϕ	0
1	0	0	0	0	ϕ
1	0	1	0	0	1
1	1	0	1	1	0
1	1	1	1	ϕ	0

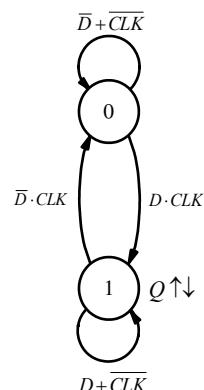

Clk	D	Action	Q_{N+1}
0	x	hold	Q_N
1	0	reset	0
1	1	set	1

Operation Table

$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
0 → 0	0	ϕ
0 → 1	1	0
1 → 0	0	1
1 → 1	ϕ	0

Excitation Table
Basic Cell

Truth Table

$$\text{Set} = \text{clk} \cdot D$$

$$\text{Reset} = \text{clk} \cdot \overline{D}$$


Equations

State Diagram

Excitation Table

Basic Cell

Clocked D Latch

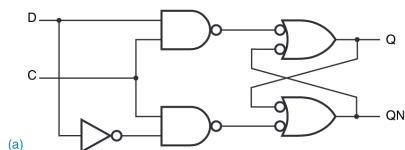

C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

(b)

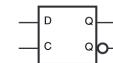


Figure 7-12

D latch: (a) circuit design using NAND gates; (b) function table; (c) logic symbol.


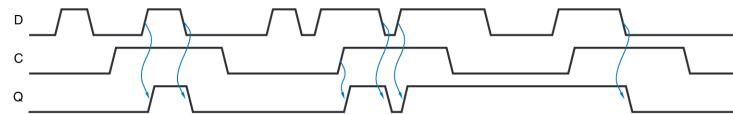


Figure 7-13

Functional behavior of a D latch for various inputs.

Design of a Clocked Toggle (T) Latch

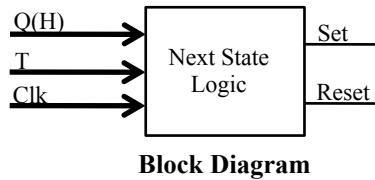

Clk	T	Qn	Qn+1	Set	Reset
0	0	0	0	0	ϕ
0	0	1	1	ϕ	0
0	1	0	0	0	ϕ
0	1	1	1	ϕ	0
1	0	0	0	0	ϕ
1	0	1	1	ϕ	0
1	1	0	1	1	0
1	1	1	0	0	1

Truth Table

Clk	T	Action	Qn+1
0	x	Hold	Qn
1	0	Hold	Qn
1	1	Toggle	\bar{Q}_n

Function Table


Qn \rightarrow Qn+1	Inputs	
	S	R
0 \rightarrow 0	0	ϕ
0 \rightarrow 1	1	0
1 \rightarrow 0	0	1
1 \rightarrow 1	ϕ	0

Excitation Table
Basic Cell


$$\text{Set} = \text{clk} \cdot T \cdot \bar{Q}$$

$$\text{Reset} = \text{clk} \cdot T \cdot Q$$

Equations

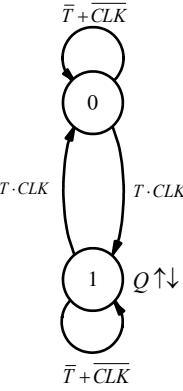

Design of a Clocked JK Latch

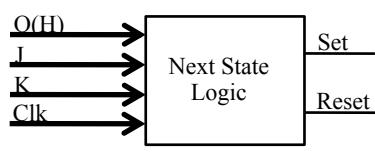

Clk	J	K	Qn	Qn+1	Set	Reset
0	0	0	0	0	0	ϕ
0	0	0	1	1	ϕ	0
0	0	1	0	0	0	ϕ
0	0	1	1	1	ϕ	0
0	1	0	0	0	0	ϕ
0	1	0	1	0	0	ϕ
0	1	1	0	0	0	ϕ
0	1	1	1	1	ϕ	0
1	0	0	0	0	0	ϕ
1	0	0	1	1	ϕ	0
1	0	1	0	0	0	ϕ
1	0	1	1	0	0	1
1	1	0	0	1	1	0
1	1	0	1	1	ϕ	0
1	1	1	0	1	1	0
1	1	1	1	0	0	1

Truth Table

Clk	J	K	Action	Qn+1
0	x	x	Hold	Qn
1	0	0	Hold	Qn
1	0	1	Reset	0
1	1	0	Set	1
1	1	1	Toggle	\bar{Q}_n

Function Table

Qn \rightarrow Qn+1	Inputs	
	S	R
0 \rightarrow 0	0	ϕ
0 \rightarrow 1	1	0
1 \rightarrow 0	0	1
1 \rightarrow 1	ϕ	0


Excitation Table
Basic Cell

$$\text{Set} = \text{clk} \cdot J \cdot \bar{Q}$$

$$\text{Reset} = \text{clk} \cdot K \cdot Q$$


Equations

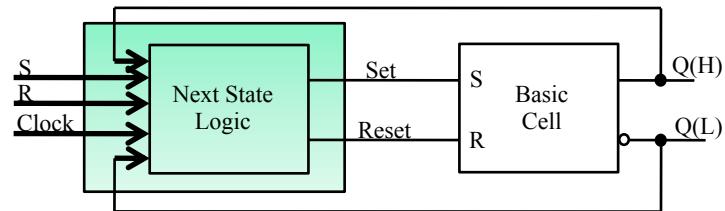Design of a Set-Dominant Clocked SR Latch



- Inputs – S, R, Clock, Q
- Outputs – Set, Reset

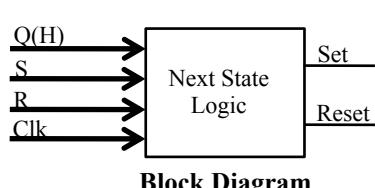Design of a Set-Dominant Clocked SR Latch



S	R	Action	Q_{N+1}
0	0	hold	Q_N
0	1	reset	0
1	0	set	1
1	1	set	1

Operation Table

Inputs		$Q_n \rightarrow Q_{n+1}$
S	R	
0	0	0 \rightarrow 0
0	1	0 \rightarrow 1
1	0	1 \rightarrow 0
1	1	1 \rightarrow 1

Excitation Table

$$\begin{aligned} Set &= clk \cdot S \\ Reset &= clk \cdot R \cdot \bar{S} \end{aligned}$$

Clk	S	R	Q_n	Q_{n+1}	Set	Reset
0	0	0	0	0	0	ϕ
0	0	0	1	1	ϕ	0
0	0	1	0	0	0	ϕ
0	0	1	1	1	ϕ	0
0	1	0	0	0	0	ϕ
0	1	0	1	1	ϕ	0
0	1	1	0	0	0	ϕ
0	1	1	1	1	ϕ	0
1	0	0	0	0	0	ϕ
1	0	0	1	1	ϕ	0
1	0	1	0	0	0	ϕ
1	0	1	1	0	0	1
1	1	0	0	1	1	0
1	1	0	1	1	ϕ	0
1	1	1	0	1	1	0
1	1	1	1	1	ϕ	0

Truth Table

SR Latch with Enable (Clock)

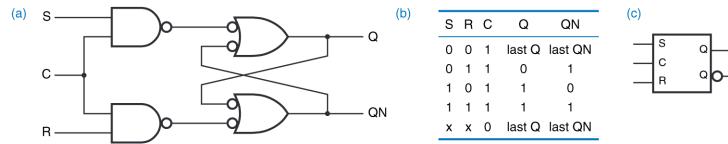


Figure 7-10

S-R latch with enable: (a) circuit using NAND gates; (b) function table; (c) logic symbol.


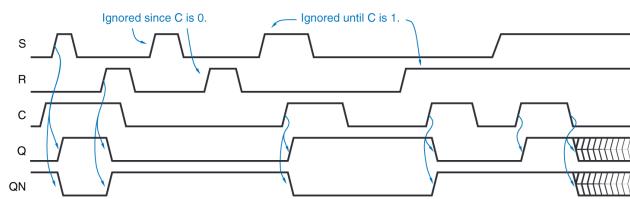


Figure 7-11

Typical operation of an S-R latch with enable.


Design of a Clocked JK Latch – Version II

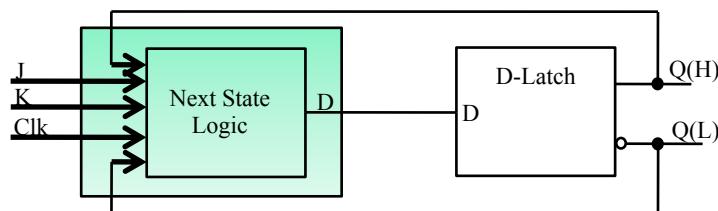- Replace the basic cell with a D-latch as the memory element.



- Inputs – J, K, Clk, Q
- Output – D

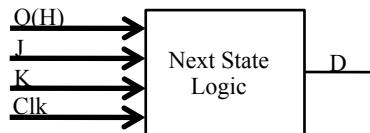Design of a Clocked JK Latch – Version II



Block Diagram

Clk	J	K	Action	Q_{N+1}
0	x	x	Hold	Q_N
1	0	0	Hold	Q_N
1	0	1	Reset	0
1	1	0	Set	1
1	1	1	Toggle	\bar{Q}_N

Function Table

$Q_n \rightarrow Q_{n+1}$	D
0 → 0	0
0 → 1	1
1 → 0	0
1 → 1	1

Excitation Table

Clk	J	K	Q_n	Q_{n+1}	D
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	0	0

Truth Table

$$D = \bar{K} \cdot Q + Q \cdot \bar{clk} + clk \cdot J \cdot \bar{Q}$$


Equation

Terminology

- Latches are often called ***Transparent*** because the output will follow the input as long as the clock signal is high.
- Flip-flops are ***edge-triggered***
 - Positive-edge triggered (PET) is when action occurs on the rising edge of the clock signal;
 - Negative-edge triggered (NET) is when action occurs on the falling edge of the clock signal.
- Types of Flip-flops
 - SR (rarely used);
 - D (very, very common, 74HC74);
 - JK (hardly ever used, 74HC109);
 - Toggle (occasionally used by CAD programs).

Setup and Hold Times

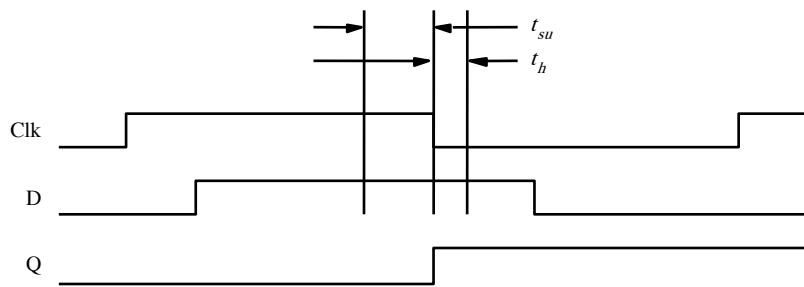- Setup time (t_{SU}) is the time interval preceding the active transition point of the CLK during which all data inputs must remain stable.
- Hold time (t_H) is the time interval following the active transition point of the CLK during which all data inputs must remain stable.
- See data sheet for [74HC74](#)



PET Master-Slave D Flip-Flop

- QM follows the D input whenever CLK is low.
- When CLK goes high, QM is transferred to the output.

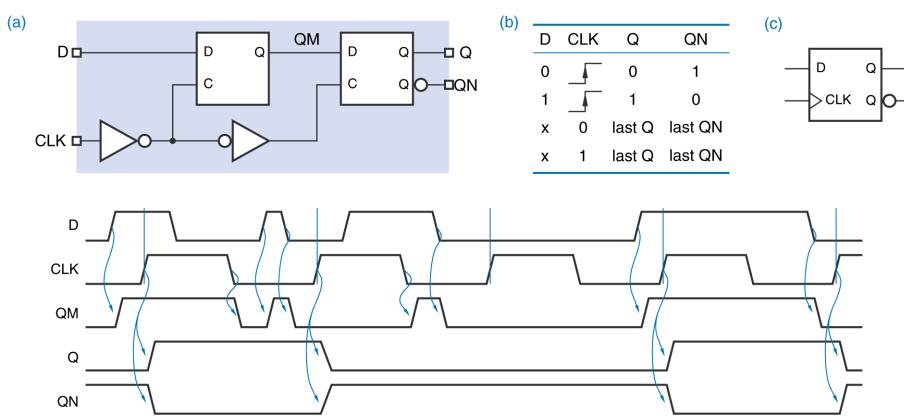


Figure 7-16
Functional behavior of a positive-edge-triggered D flip-flop.

Positive-Edge-Triggered D Flip-Flop

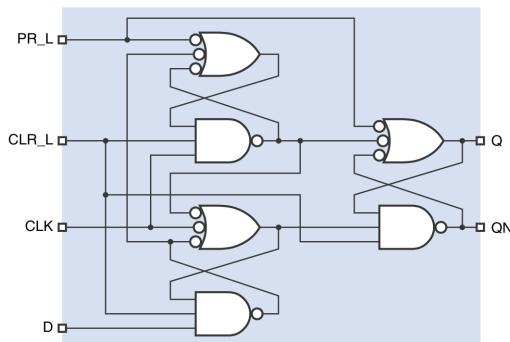


Figure 7-20
Commercial circuit for a positive-edge-triggered D flip-flop such as 74LS74.

PET D Flip-Flop with *Clear* and *Preset*

- Synchronous – transitions or actions occur in relation to the CLK signal;
- Asynchronous – transitions or actions are not related to the CLK signal.


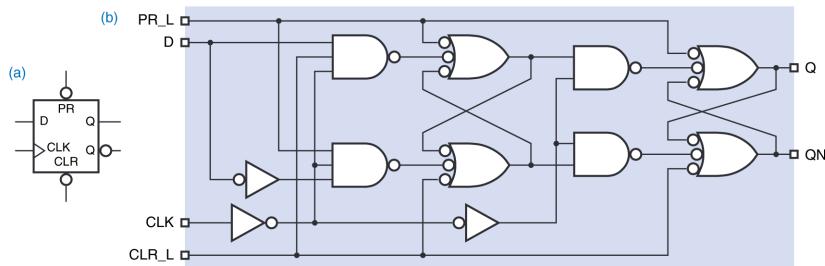


Figure 7-19
Positive-edge-triggered D flip-flop with preset and clear:
(a) logic symbol; (b) circuit design using NAND gates.


Level-Sensitive vs. Edge-Triggered

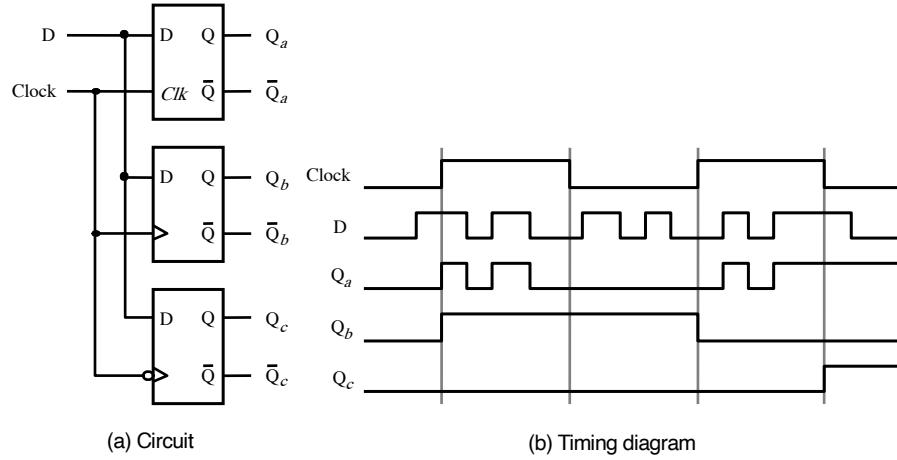- Level-sensitive = latch
- Edge-triggered = flip-flop



Design a T Flip-Flop from a D Flip-Flop

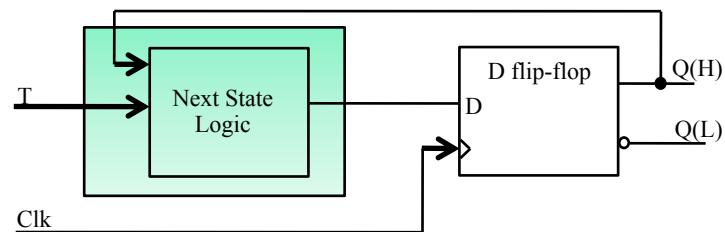- The memory element is now **edge-triggered** meaning the Clk signal is no longer part of the **next-state logic**.



T	$Q(n+1)$
0	$Q(n)$
1	$\bar{Q}(n)$

Function Table


$Q_n \rightarrow Q_{n+1}$	D
0 \rightarrow 0	0
0 \rightarrow 1	1
1 \rightarrow 0	0
1 \rightarrow 1	1

Excitation Table


T	Q_n	Q_{n+1}	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Truth Table

Design a T Flip-Flop from a D Flip-Flop

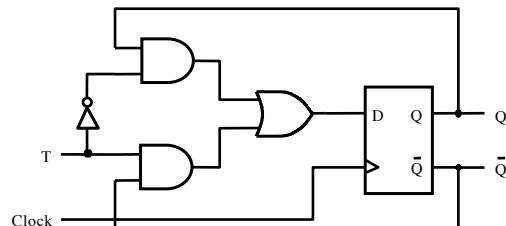


(a) Circuit

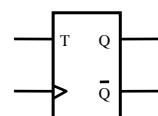

(c) Graphical symbol


Design a JK Flip-Flop from a D Flip-Flop

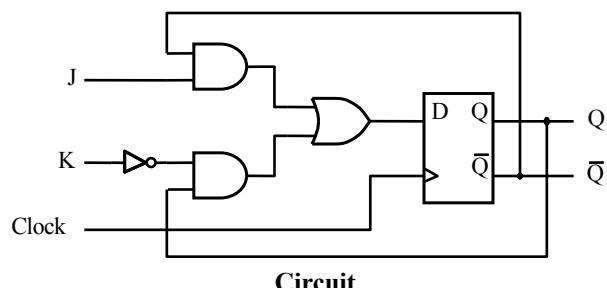

Circuit

J	K	$Q(n+1)$
0	0	$Q(n)$
0	1	0
1	0	1
1	1	$\bar{Q}(n)$

Function Table

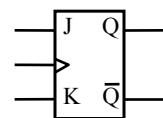

Graphical symbol

Summary of Terminology

- Basic cell – cross-coupled NAND/NOR.
- Gated latch – output changes only when Clk is asserted
 - Gated SR latch;
 - Gated D latch;
 - Gated JK latch.
- Flip-flop – output changes only on Clk edge
 - Master-slave;
 - Edge-triggered;
 - Three main types
 - D (very, very common, 74HC74);
 - JK (hardly ever used, 74HC109);
 - Toggle (occasionally used by CAD programs).

Sequential Logic Elements Summary

In this chapter you learned about

- Logic circuits that can store information;
- Basic cells, latches, and flip-flops;
- State diagrams;
- Design techniques for circuits that use flip-flops.