

Sequential Circuit Design

Name _____

Partner _____

Grade _____/10

Objectives

- Gain sequential logic design experience;
- Gain experience using a logic simulator (Logisim);
- Gain maturity in the construction and debugging of logic circuits.

Circuit Components Required

- Various SSI and MSI IC's.
- Breadboards;
- Wire;
- Instruments as necessary.

Procedure

- Design a 2-bit grey code counter that counts up if the one input **up/down** is asserted, otherwise it counts down. There are two outputs, X and Y. X is asserted when the present state has an odd number of bits asserted. Y is asserted when the present state bits are the same.
 - Use rising edge-triggered D flip-flops as your memory elements.
 - Simulate your design in Logisim.
 - Fully document your design following the 9-step design process presented in class.
 - Find an **absolute minimum number of IC's needed to implement your design.**
- Wire up your circuit using the breadboards in the digital lab. Set $V_{dd} = 3.0$ volts. Have your circuit checked out by the lab assistant before you leave lab. Here is a list of parts available for you to use:

74HC00 Quad 2-Input NAND Gate	74HC74 Dual D Flip-Flop
74HC02 Quad 2-Input NOR Gate	74HC86 Quad 2-Input XOR Gate
74HC04 Hex Inverter	74HC138 3-to-8 Decoder
74HC10 Triple 3-Input NAND Gate	74HC139 Dual 2-to-4 Decoder
74HC20 Dual 4-input NAND Gate	74HC151 8-to-1 Multiplexer (maybe)
74HC27 Triple 3-Input NOR Gate	74HC153 Dual 4-to-1 Multiplexer

To Turn In

- Staple together
 - This handout;
 - A schematic of your circuit. This can be hand written if it is neat;
 - A hard copy of your simulation results. Make sure you have sufficient resolution on all traces;
 - A short write-up explaining your design, procedures, results, conclusions, and lessons learned. **Each person** must turn in a report;
 - This hard-copy information is due by the beginning of class on Wednesday, October 2.