

Chapter 4

Concurrent Signal Assignment Statements

Dr. Curt Nelson
Engr433 – Digital Design

Outline

Combinational versus sequential circuits;
Simple signal assignment statement;
Conditional signal assignment statement;
Selected signal assignment statement;
Conditional vs. selected signal assignment.

Combinational vs. Sequential Circuits


- Combinational circuit
 - No internal state;
 - Output is a function of inputs only;
 - No latches/FFs or closed feedback loop.
- Sequential circuit
 - Contains internal state;
 - Output is a function of inputs and internal state.
- Sequential circuit will be discussed in Chapter 5.

Simple Signal Assignment Statement

- Simple signal assignment is a special case of conditional signal assignment.
- Syntax
 - `signal_name <= value_expression;`
- Example
 - `y <= a + b + 1 after 10 ns;`
- Timing info is ignored in synthesis and δ -delay (tiny delay) is used instead.

Simple Signal Assignment Statement

 - Example
status <= '1';
even <= (p1 **and** p2) **or** (p3 **and** p4);
arith_result <= a + b + c - 1;
- Implementation of example



Signal Assignment Statement With Closed Feedback Loop

- A signal appears in both sides of a concurrent assignment statement.
- Example
q <= ((**not** q) **and** (**not** en)) **or** (d **and** en);
- Syntactically correct.
- Forms a closed feedback loop.
- Should be avoided.

Conditional Signal Assignment Statement

- Simplified syntax

```
signal_name
  <= value_expr_1 when boolean_expr_1 else
    value_expr_2 when boolean_expr_2 else
    value_expr_3 when boolean_expr_3 else
    ...
```

Example: 4-to-1 Mux

```
library ieee;
use ieee.std_logic_1164.all;
entity mux4 is
  port(
    a,b,c,d: in std_logic_vector(7 downto 0);
    s: in std_logic_vector(1 downto 0);
    x: out std_logic_vector(7 downto 0)
  );
end mux4 ;
architecture cond_arch of mux4 is
begin
  x <= a when (s="00") else
    b when (s="01") else
    c when (s="10") else
    d;
end cond_arch;
```

input		output	
s		x	
0	0	0	a
0	1	0	b
1	0	0	c
1	1	0	d

Example: 2-to-2² Binary Decoder

```

library ieee;
use ieee.std_logic_1164.all;
entity decoder4 is
  port(
    s: in  std_logic_vector(1 downto 0);
    x: out std_logic_vector(3 downto 0)
  );
end decoder4 ;
architecture cond_arch of decoder4 is
begin
  x <= "0001" when (s="00") else
       "0010" when (s="01") else
       "0100" when (s="10") else
       "1000";
end cond_arch;

```

input	output
s	x
0 0	0001
0 1	0010
1 0	0100
1 1	1000

Example: 4-to-2 Priority Encoder

```

library ieee;
use ieee.std_logic_1164.all;
entity prio_encoder42 is
  port(
    r: in  std_logic_vector(3 downto 0);
    code: out std_logic_vector(1 downto 0);
    active: out std_logic
  );
end prio_encoder42;
architecture cond_arch of prio_encoder42 is
begin
  code <= "11" when (r(3)='1') else
          "10" when (r(2)='1') else
          "01" when (r(1)='1') else
          "00";
  active <= r(3) or r(2) or r(1) or r(0);
end cond_arch ;

```

input	output	
r	code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

Example: Simple ALU

input	output
ctrl	result
0--	src0 + 1
100	src0 + src1
101	src0 - src1
110	src0 and src1
111	src0 or src1

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity simple_alu is
    port(
        ctrl: in  std_logic_vector(2 downto 0);
        src0, src1: in std_logic_vector(7 downto 0);
        result: out std_logic_vector(7 downto 0)
    );
end simple_alu ;

architecture cond_arch of simple_alu is
    signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
    inc <= std_logic_vector(signed(src0)+1);
    sum <= std_logic_vector(signed(src0)+signed(src1));
    diff <= std_logic_vector(signed(src0)-signed(src1));
    result <= inc  when ctrl(2)='0' else
              sum  when ctrl(1 downto 0)="00" else
              diff when ctrl(1 downto 0)="01" else
              src0 and src1 when ctrl(1 downto 0)="10" else
              src0 or src1;
end cond_arch;

```

Conceptual Implementation

- Syntax

 

```

signal_name
    <= value_expr_1 when boolean_expr_1 else
       value_expr_2 when boolean_expr_2 else
       value_expr_3 when boolean_expr_3 else
       ...
       value_expr_n;

```
- Evaluated in descending order.
- Implicit priority
 - Top value expression has a “higher priority”


2-to-1 Multiplexer

- sel has a data type of *boolean*.
- If sel is true, the input from “T” port is connected to output.
- If sel is false, the input from “F” port is connected to output.



2-to-1 “Abstract” Mux

 
```
signal_name <= value_expr_1 when boolean_expr_1 else  
value_expr_2;
```



4-to-1 “Abstract” Mux

```

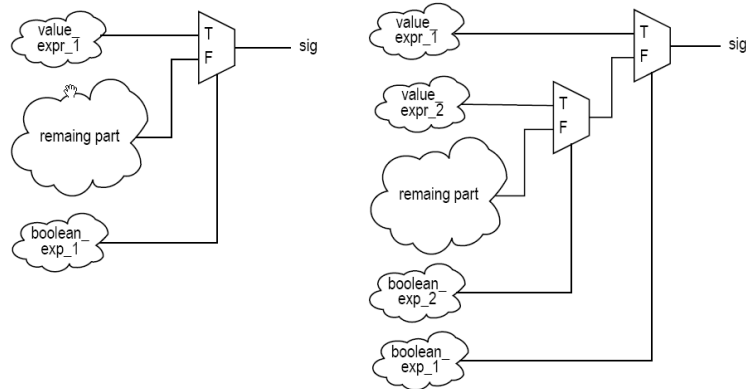signal_name <= value_expr_1 when boolean_expr_1 else
               value_expr_2 when boolean_expr_2 else
               value_expr_3 when boolean_expr_3 else
               value_expr_4;
    
```





Implementation Example #1

```


. . .
signal a,b,y: std_logic;
. . .
y <= '0' when a=b else
      '1';
. . .
    
```

input		output
a	b	a=b
0	0	1
0	1	0
1	0	0
1	1	1

  


Implementation Example #2
 
```
signal a,b,c,x,y,r: std_logic;  
.  
.  
r <= a when x=y else  
    b when x>y else  
    c;
```



Implementation Example #2 Schematic

 


Implementation Example #3

```

. . .
signal a,b,r: unsigned(7 downto 0);
signal x,y: unsigned(3 downto 0);
. . .
r <= a+b when x+y>1 else
    a-b-1 when x>y and y!=0 else
    a+1;
. . .

```

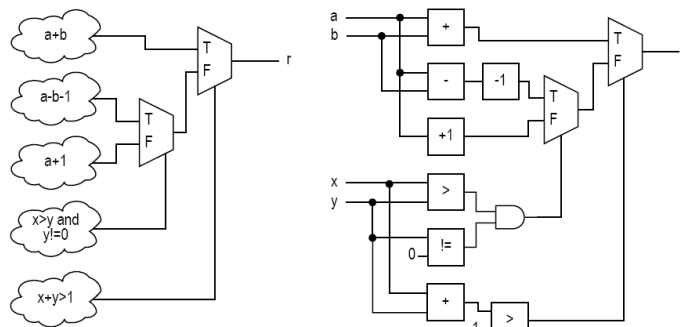

Selected Signal Assignment Statement

- Simplified syntax

with select_expression **select**

signal_name <=

value_expr_1 **when** choice_1,

value_expr_2 **when** choice_2,

value_expr_3 **when** choice_3,

...

value_expr_n **when** choice_n;

- select_expression

- Discrete type or 1-D array

- With finite possible values

- choice_i

- A value of the data type

- Choices must be

- mutually exclusive

- all inclusive

- **others** can be used as last choice_i

Example: 4-to-1 Mux

```
architecture sel_arch of mux4 is
begin
  with s select
    x <= a when "00",
         b when "01",
         c when "10",
         d when others;
end sel_arch ;
```

input s	output x
00	a
01	b
10	c
11	d

Example: 4-to-1 Mux

- Can “11” be used to replace **others**?

```
with s select
  x <= a when "00",
        b when "01",
        c when "10",
        d when "11";
```

Example: 2-to-2² Binary Decoder

```
architecture sel_arch of decoder4 is
begin
  with sel select
    x <= "0001" when "00",
         "0010" when "01",
         "0100" when "10",
         "1000" when others;
end sel_arch;
```

input s	output x
00	0001
01	0010
10	0100
11	1000

Example: 4-to-2 Priority Encoder

```
architecture sel_arch of prio_encoder42 is
begin
  with r select
    code <= "11" when "1000"|"1001"|"1010"|"1011" |
               "1100"|"1101"|"1110"|"1111",
           "10" when "0100"|"0101"|"0110"|"0111",
           "01" when "0010"|"0011",
           "00" when others;
  active <= r(3) or r(2) or r(1) or r(0);
end sel_arch;
```

input r	output code	output active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

Example: 4-to-1 Mux

- Can we use ‘-’?

```
with a select
  x <= "11" when "1---",
       "10" when "01--",
       "01" when "001-",
       "00" when others;
```

- Note implied priority.

Example: Simple ALU

```
architecture sel_arch of simple_alu is
  signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
  inc <= std_logic_vector(signed(src0)+1);
  sum <= std_logic_vector(signed(src0)+signed(src1));
  diff <= std_logic_vector(signed(src0)-signed(src1));
  with ctrl select
    result <= inc          when "000"|"001"|"010"|"011",
               sum         when "100",
               diff        when "101",
               src0 and src1 when "110",
               src0 or src1 when others; -- "111"
end sel_arch;
```


input ctrl	output result
0--	src0 + 1
100	src0 + src1
101	src0 - src1
110	src0 and src1
111	src0 or src1

Example: Truth Table

<pre> library ieee; use ieee.std_logic_1164.all; entity truth_table is port(a,b: in std_logic; y: out std_logic); end truth_table; architecture a of truth_table is signal tmp: std_logic_vector(1 downto 0); begin tmp <= a & b; with tmp select y <= '0' when "00", '1' when "01", '1' when "10", '1' when others; -- "11" end a;</pre>	<table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th style="border-bottom: 1px solid black;">input</th> <th style="border-bottom: 1px solid black;">output</th> </tr> <tr> <th style="border-bottom: 1px solid black;">a b</th> <th style="border-bottom: 1px solid black;">y</th> </tr> </thead> <tbody> <tr> <td>0 0</td> <td>0</td> </tr> <tr> <td>0 1</td> <td>1</td> </tr> <tr> <td>1 0</td> <td>1</td> </tr> <tr> <td style="border-bottom: 1px solid black;">1 1</td> <td style="border-bottom: 1px solid black;">1</td> </tr> </tbody> </table>	input	output	a b	y	0 0	0	0 1	1	1 0	1	1 1	1
input	output												
a b	y												
0 0	0												
0 1	1												
1 0	1												
1 1	1												

Truth Table - Conceptual Implementation

 
- Achieved by a multiplexing circuit.
- Abstract (k+1)-to-1 multiplexer
 - sel is with a data type of (k+1) values:
c0, c1, c2, ..., ck



Conceptual Implementation

- select_expression below is with a data type of 5 values: c0, c1, c2, c3, c4

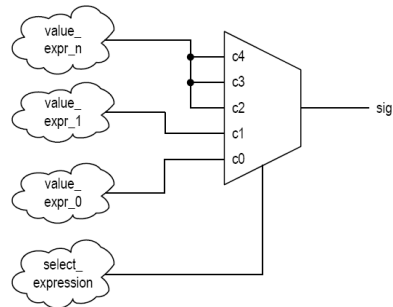
```
with select_expression select
  sig <= value_expr_0 when c0,
        value_expr_1 when c1,
        value_expr_n when others;
```



Detailed Implementation Example

```
signal a,b,r: unsigned(7 downto 0);
signal s: std_logic_vector(1 downto 0);
```
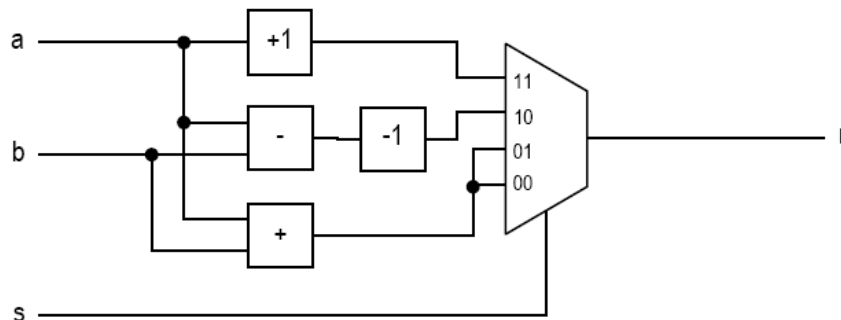
```
...
with s select
  r <= a+1 when "11",
        a-b-1 when "10",
        a+b when others;
```



From Selected Assignment to Conditional Assignment

```
with sel select
  sig <= value_expr_0 when c0,
        value_expr_1 when c1|c3|c5,
        value_expr_2 when c2|c4,
        value_expr_n when others;

sig <=
  value_expr_0 when (sel=c0) else
  value_expr_1 when (sel=c1) or (sel=c3) or (sel=c5) else
  value_expr_2 when (sel=c2) or (sel=c4) else
  value_expr_n;
```

From Conditional Assignment to Selected Assignment

```
sig <= value_expr_0 when bool_exp_0 else
      value_expr_1 when bool_exp_1 else
      value_expr_2 when bool_exp_2 else
      value_expr_n;

sel(2) <= '1' when bool_exp_0 else '0';
sel(1) <= '1' when bool_exp_1 else '0';
sel(0) <= '1' when bool_exp_2 else '0';

with sel select
  sig <= value_expr_0 when "100"|"101"|"110"|"111",
        value_expr_1 when "010"|"011",
        value_expr_2 when "001",
        value_expr_n when others;
```


Comparison

- Selected signal assignment
 - Good match for a circuit described by a functional table;
 - E.g., binary decoder, multiplexer;
 - Less effective when an input pattern is given a preferential treatment.
- Conditional signal assignment:
 - Good match for a circuit that needs to give preferential treatment for certain conditions or to prioritize the operations;
 - E.g., priority encoder;
 - Can handle complicated conditions like this

```
pc_next <=
    pc_reg + offset when (state=jump and a=b) else
    pc_reg + 1 when (state=skip and flag='1') else
    . . .
```