 


Engr433 - Digital Design

VHDL Examples

Dr Curtis Nelson


Adder Circuits – Half Adder




(a) The four possible cases

x	y	Carry c	Sum s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 

(c) Circuit

 

(d) Graphical symbol

Adder Circuits – Full Adder

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table


c_i \ $x_i y_i$	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

c_i \ $x_i y_i$	00	01	11	10
0			1	
1	1	1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 

(c) Circuit

VHDL Code for a Full Adder


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY fulladd IS
    PORT (cin, a, b      : IN    STD_LOGIC ;
          s, cout       : OUT   STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE Behavior OF fulladd IS
BEGIN
    s <= a XOR b XOR cin;
    cout <= (a AND b) OR (a AND cin) OR (b AND cin);
END Behavior ;
    
```

Alternative Full Adder

 

(a) Block diagram

 

(b) Detailed diagram

Class Assignment

- Write **structural** VHDL code for a 4-bit ripple adder using the full adder as a component.
- Teammates for today only
 - Arlt and Ballance
 - Binder and Birge
 - Christensen and Jessop
 - Jurgensen and Llewellyn
 - Marcondes and Palma
 - Pham and Russell
 - Sukachevin and Terrado
 - Ventura and Wilde

VHDL Code for a 4-bit Ripple Adder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY adder4 IS
    PORT (    cin           : IN      STD_LOGIC ;
            x3,x2,x1,x0    : IN      STD_LOGIC ;
            y3,y2,y1,y0    : IN      STD_LOGIC ;
            s3,s2,s1,s0    : IN      STD_LOGIC ;
            x3,x2,x1,x0    : IN      STD_LOGIC ;
            cout          : OUT     STD_LOGIC );
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1,c2,c3 : STD_LOGIC ;
    COMPONENT fulladd
        PORT (    cin, x, y : IN      STD_LOGIC ;
                s, cout  : OUT     STD_LOGIC );
    END COMPONENT ;
BEGIN
    stage0: fulladd PORT MAP (cin, x0, y0, s0, c1 );
    stage1: fulladd PORT MAP (c1, x1, y1, s1, c2 );
    stage2: fulladd PORT MAP (c2, x2, y2, s2, c3 );
    stage3: fulladd PORT MAP (
        cin => c3, cout => cout, x=> x3, y=> y3, s=> s3 );
END Structure ;
```

VHDL Code for a 2-to-1 Mux

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT (    w0, w1, s : IN      STD_LOGIC ;
            f           : OUT     STD_LOGIC );
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN '0',
           w1 WHEN OTHERS ;
END Behavior ;
```

VHDL Using Conditional Signal Assignments

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN    STD_LOGIC ;
          f         : OUT   STD_LOGIC );
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END Behavior ;
```

VHDL Code for a 4-to-1 Mux

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3 : IN    STD_LOGIC ;
          s               : IN    STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          f               : OUT   STD_LOGIC );
END mux4to1 ;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
          w1 WHEN "01",
          w2 WHEN "10",
          w3 WHEN OTHERS ;
END Behavior ;
```

Component Declaration for 4-to-1 Mux

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
PACKAGE mux4to1_package IS
  COMPONENT mux4to1
    PORT ( w0, w1, w2, w3      : IN      STD_LOGIC ;
          s                    : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          f                    : OUT     STD_LOGIC ) ;
  END COMPONENT ;
END mux4to1_package ;
```

Hierarchical Code for a 16-to-1 Mux

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY work ;
USE work.mux4to1_package.all ;

ENTITY mux16to1 IS
  PORT ( w      : IN      STD_LOGIC_VECTOR(0 TO 15) ;
        s      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
        f      : OUT     STD_LOGIC ) ;
END mux16to1 ;

ARCHITECTURE Structure OF mux16to1 IS
  SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
BEGIN
  Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNTO 0), m(0) ) ;
  Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNTO 0), m(1) ) ;
  Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNTO 0), m(2) ) ;
  Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNTO 0), m(3) ) ;
  Mux5: mux4to1 PORT MAP
    ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;
END Structure ;
```

Code for a 2-to-4 Decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w : IN      STD_LOGIC_VECTOR(1 DOWNT0 0) ;
           En : IN      STD_LOGIC ;
           y : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNT0 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "1000" WHEN "100",
             "0100" WHEN "101",
             "0010" WHEN "110",
             "0001" WHEN "111",
             "0000" WHEN OTHERS ;
END Behavior ;
```

Hierarchical Code for a 4-to-16 Decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec4to16 IS
    PORT ( w : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           En : IN      STD_LOGIC ;
           y : OUT     STD_LOGIC_VECTOR(0 TO 15) ) ;
END dec4to16 ;

ARCHITECTURE Structure OF dec4to16 IS
    COMPONENT dec2to4
        PORT ( w : IN      STD_LOGIC_VECTOR(1 DOWNT0 0) ;
              En : IN      STD_LOGIC ;
              y : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
    END COMPONENT ;
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
BEGIN
    G1: FOR i IN 0 TO 3 GENERATE
        Dec_ri: dec2to4 PORT MAP ( w(1 DOWNT0 0), m(i), y(4*i TO 4*i+3) ) ;
    G2: IF i=3 GENERATE
        Dec_left: dec2to4 PORT MAP ( w(i DOWNT0 i-1), En, m ) ;
    END GENERATE ;
    END GENERATE ;
END Structure ;
```

VHDL Code for a Priority Encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT   STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT   STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    y <=  "11" WHEN w(3) = '1' ELSE
          "10" WHEN w(2) = '1' ELSE
          "01" WHEN w(1) = '1' ELSE
          "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;
```

Less Efficient Code for a Priority Encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT   STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT   STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    WITH w SELECT
        y <= "00" WHEN "0001",
            "01" WHEN "0010",
            "01" WHEN "0011",
            "10" WHEN "0100",
            "10" WHEN "0101",
            "10" WHEN "0110",
            "10" WHEN "0111",
            "11" WHEN OTHERS ;
    WITH w SELECT
        z <= '0' WHEN "0000",
            '1' WHEN OTHERS ;
END Behavior ;
```


A BCD-to-7-segment Decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY seg7 IS
    PORT (    bcd    : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           leds    : OUT     STD_LOGIC_VECTOR(1 TO 7) );
END seg7 ;
ARCHITECTURE Behavior OF seg7 IS
BEGIN
    PROCESS ( bcd )
    BEGIN
        CASE bcd IS --
            WHEN "0000" => leds <= "1111110" ;
            WHEN "0001" => leds <= "0110000" ;
            WHEN "0010" => leds <= "1101101" ;
            WHEN "0011" => leds <= "1111001" ;
            WHEN "0100" => leds <= "0110011" ;
            WHEN "0101" => leds <= "1011011" ;
            WHEN "0110" => leds <= "1011111" ;
            WHEN "0111" => leds <= "1110000" ;
            WHEN "1000" => leds <= "1111111" ;
            WHEN "1001" => leds <= "1110011" ;
            WHEN OTHERS => leds <= "-----" ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

Code for a 4-bit Magnitude Comparator

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY compare IS
    PORT (    A, B      : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           AeqB, AgtB, AltB : OUT     STD_LOGIC );
END compare ;

ARCHITECTURE Behavior OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END Behavior ;
```

4-bit Comparator using Signed Numbers

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all ;

ENTITY compare IS
    PORT ( A, B          : IN    SIGNED(3 DOWNTO 0);
          AeqB, AgtB, AltB : OUT  STD_LOGIC );
END compare ;

ARCHITECTURE Behavior OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END Behavior ;
```

Code that Represents the Functionality of the 74381 ALU

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY alu IS
    PORT ( s      : IN    STD_LOGIC_VECTOR(2 DOWNTO 0);
          A, B    : IN    STD_LOGIC_VECTOR(3 DOWNTO 0);
          F      : OUT  STD_LOGIC_VECTOR(3 DOWNTO 0));
END alu ;

ARCHITECTURE Behavior OF alu IS
BEGIN
    PROCESS ( s, A, B )
    BEGIN
        CASE s IS
            WHEN "000" => F <= "0000" ;
            WHEN "001" => F <= B - A ;
            WHEN "010" => F <= A - B ;
            WHEN "011" => F <= A + B ;
            WHEN "100" => F <= A XOR B ;
            WHEN "101" => F <= A OR B ;
            WHEN "110" => F <= A AND B ;
            WHEN OTHERS =>
                F <= "1111" ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

Concurrent vs. Sequential VHDL Code

- All previous VHDL statements shown are called *concurrent assignment statements* because order does not matter;
- When order matters, the statements are called *sequential assignment statements*;
- All sequential assignment statements are placed within a *process statement*.

Process Statement

- Begins with PROCESS keyword followed by a *sensitivity list*;
- For a combinational circuit, sensitivity list includes all input signals used in the process;
- Process executed whenever there is a change on a signal in the sensitivity list;
- Statements executed in sequential order;
- No assignments are visible until all statements in the process have been executed;
- If multiple assignments, only last one has an effect.

2-to-1 Mux using an if-then-else Statement

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN    STD_LOGIC ;
          f          : OUT   STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        IF s = '0' THEN
            f <= w0 ;
        ELSE
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Alternative Code for a 2-to-1 Mux

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN    STD_LOGIC ;
          f          : OUT   STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        f <= w0 ;
        IF s = '1' THEN
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Priority Encoder Using if-then-else

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY priority IS
    PORT ( w : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT     STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT     STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    PROCESS ( w )
    BEGIN
        IF w(3) = '1' THEN
            y <= "11" ;
        ELSIF w(2) = '1' THEN
            y <= "10" ;
        ELSIF w(1) = '1' THEN
            y <= "01" ;
        ELSE
            y <= "00" ;
        END IF ;
    END PROCESS ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;
```

Alternative Code for the Priority Encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT     STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT     STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    PROCESS ( w )
    BEGIN
        y <= "00" ;
        IF w(1) = '1' THEN y <= "01" ; END IF ;
        IF w(2) = '1' THEN y <= "10" ; END IF ;
        IF w(3) = '1' THEN y <= "11" ; END IF ;

        z <= '1' ;
        IF w = "0000" THEN z <= '0' ; END IF ;
    END PROCESS ;
END Behavior ;
```

Code for a 1-bit Equality Comparator

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY compare1 IS
    PORT ( A, B      : IN      STD_LOGIC ;
          AeqB      : OUT     STD_LOGIC );
END compare1 ;

ARCHITECTURE Behavior OF compare1 IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        AeqB <= '0' ;
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

CASE statement for a 2-to-1 Mux

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN      STD_LOGIC ;
          f          : OUT     STD_LOGIC );
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        CASE s IS
            WHEN '0' =>
                f <= w0 ;
            WHEN OTHERS =>
                f <= w1 ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

Case Statement for a 2-to-4 Binary Decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En      : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
    PROCESS ( w, En )
    BEGIN
        IF En = '1' THEN
            CASE w IS
                WHEN "00" => y <= "1000" ;
                WHEN "01" => y <= "0100" ;
                WHEN "10" => y <= "0010" ;
                WHEN OTHERS => y <= "0001" ;
            END CASE ;
        ELSE
            y <= "0000" ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Implied Memory

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT ( A, B      : IN      STD_LOGIC ;
          AeqB      : OUT     STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Code for a Gated D Latch

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, Clk : IN    STD_LOGIC ;
          Q      : OUT   STD_LOGIC);
END latch ;

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Code for a D Flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q      : OUT   STD_LOGIC);
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```


Code for a D Flip-flop Using WAIT UNTIL

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY flipflop IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q          : OUT  STD_LOGIC );
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        Q <= D ;
    END PROCESS ;
END Behavior ;
```

D Flip-flop with Asynchronous Reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN    STD_LOGIC ;
          Q                  : OUT  STD_LOGIC );
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

D Flip-flop with Synchronous Reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN    STD_LOGIC ;
          Q                  : OUT  STD_LOGIC);
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSE
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```