

Sequential Logic Elements

Latches

Circuit Types

- ***Combinational*** – output depends only on the input.
- ***Sequential*** – output depends on input and past behavior
 - Requires use of storage elements;
 - Contents of the storage elements is called *state*;
 - Circuit goes through a sequence of states as a result of changes in inputs.
- ***Synchronous*** – controlled by a clock.

Clock Signals

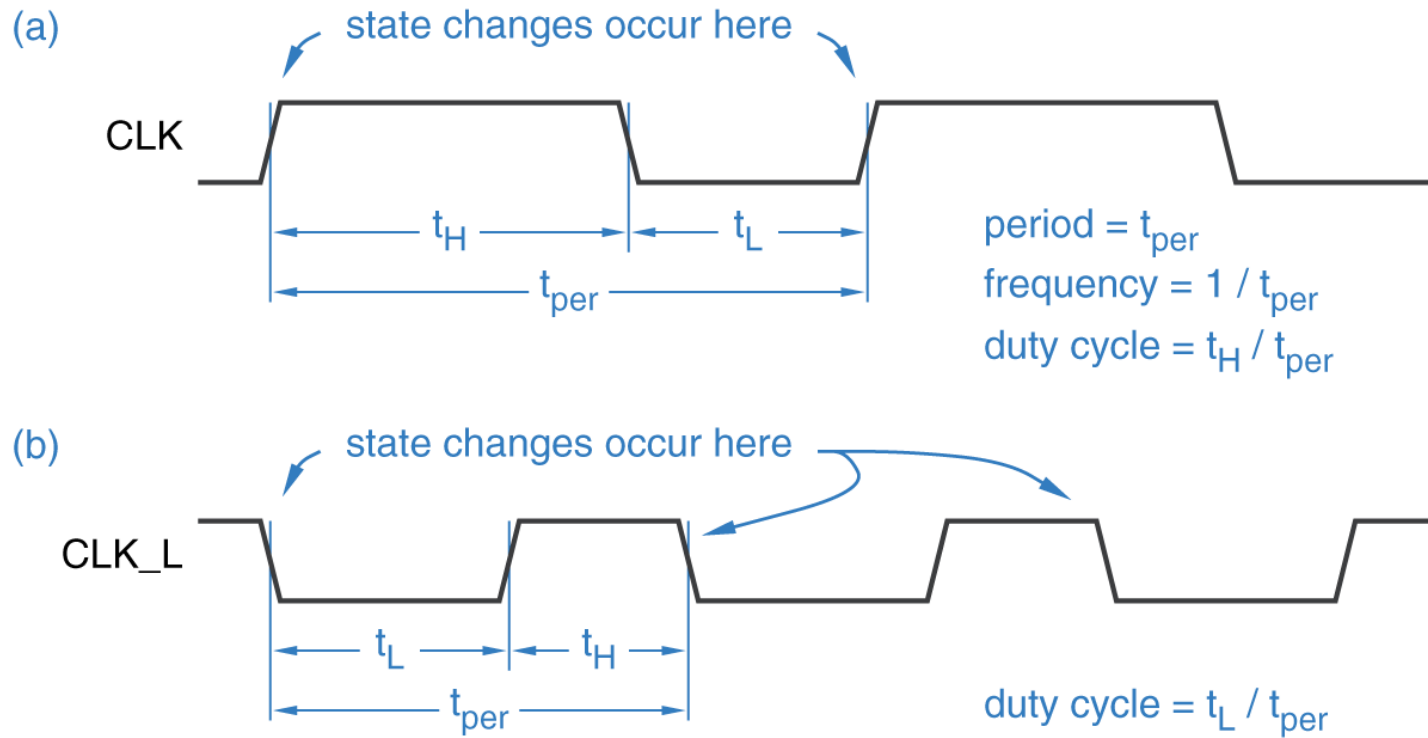


Figure 7-1

Clock signals: (a) active high; (b) active low.

A Bistable Memory Element

- Bistable – possessing two stable states.


 
 


Figure 7-2

A pair of inverters forming a bistable element.

A Set/Reset (SR) Memory Element

 - Called a *Basic Cell*;
- NOR centered Basic Cell:
 - Circuit (a), Function table (b).
- Inputs are active when they are *high*;
- Blocking side inputs.




(b)





| S | R | Q | QN |
|---|---|--------|---------|
| 0 | 0 | last Q | last QN |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

Typical Operation of a *Basic Cell*

- Reset, clear.
- Set, preset.

 


| S | R | Q | QN |
|---|---|--------|---------|
| 0 | 0 | last Q | last QN |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

   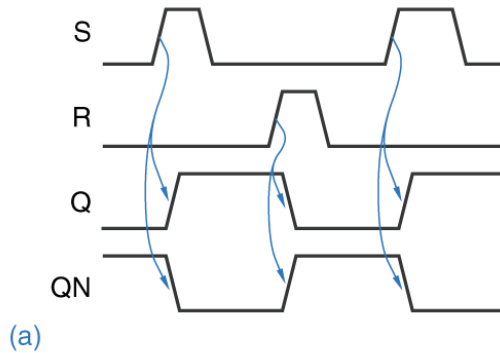

(a)

(b)

NOR-Centered (Reset Dominant) Basic Cell

 


Circuit

| S | R | Action | Q_{n+1} |
|---|---|--------|-----------|
| 0 | 0 | hold | Q_n |
| 0 | 1 | reset | 0 |
| 1 | 0 | set | 1 |
| 1 | 1 | reset | 0 |

Operation Table

| $Q_n \rightarrow Q_{n+1}$ | Inputs | |
|---------------------------|--------|--------|
| | S | R |
| $0 \rightarrow 0$ | 0 | ϕ |
| $0 \rightarrow 1$ | 1 | 0 |
| $1 \rightarrow 0$ | ϕ | 1 |
| $1 \rightarrow 1$ | ϕ | 0 |


Excitation Table

 

State Diagram

NAND-Centered (Set Dominant) Basic Cell

 - Inputs are active low (when they are *asserted*);
- Operation table indicates assertion, not voltage, levels.




Circuit

| S | R | Action | Q_{N+1} |
|---|---|--------|-----------|
| 0 | 0 | hold | Q_N |
| 0 | 1 | reset | 0 |
| 1 | 0 | set | 1 |
| 1 | 1 | set | 1 |

Operation Table

| $Q_n \rightarrow Q_{n+1}$ | Inputs | |
|---------------------------|--------|--------|
| | S | R |
| $0 \rightarrow 0$ | 0 | ϕ |
| $0 \rightarrow 1$ | 1 | ϕ |
| $1 \rightarrow 0$ | 0 | 1 |
| $1 \rightarrow 1$ | 1 | ϕ |
| | ϕ | 0 |

Excitation Table

 

**State
Diagram**

Combined Form of the Basic Cell

| $Q_n \rightarrow Q_{n+1}$ | Inputs | |
|---------------------------|--------|--------|
| | S | R |
| 0 \rightarrow 0 | 0 | ϕ |
| 0 \rightarrow 1 | 1 | ϕ |
| 1 \rightarrow 0 | 0 | 1 |
| 1 \rightarrow 1 | 1 | ϕ |
| | ϕ | 0 |


**Excitation Table
NAND-centered**

| $Q_n \rightarrow Q_{n+1}$ | Inputs | |
|---------------------------|--------|--------|
| | S | R |
| 0 \rightarrow 0 | 0 | ϕ |
| | ϕ | 1 |
| 0 \rightarrow 1 | 1 | 0 |
| 1 \rightarrow 0 | ϕ | 1 |
| 1 \rightarrow 1 | ϕ | 0 |

**Excitation Table
NOR-centered**

| $Q_n \rightarrow Q_{n+1}$ | Inputs | |
|---------------------------|--------|--------|
| | S | R |
| 0 \rightarrow 0 | 0 | ϕ |
| 0 \rightarrow 1 | 1 | 0 |
| 1 \rightarrow 0 | 0 | 1 |
| 1 \rightarrow 1 | ϕ | 0 |

**Excitation Table
Combined Form**

 


Basic Cell

Designing Latches - A Model


- Latch - a logic circuit that transfers the input state to the output state when the *clock* signal is high and latches and holds the input when the *clock* signal goes low.

| $Q_n \rightarrow Q_{n+1}$ | Inputs | |
|---------------------------|--------|--------|
| | S | R |
| $0 \rightarrow 0$ | 0 | ϕ |
| $0 \rightarrow 1$ | 1 | 0 |
| $1 \rightarrow 0$ | 0 | 1 |
| $1 \rightarrow 1$ | ϕ | 0 |


**Excitation Table
Combined Form**

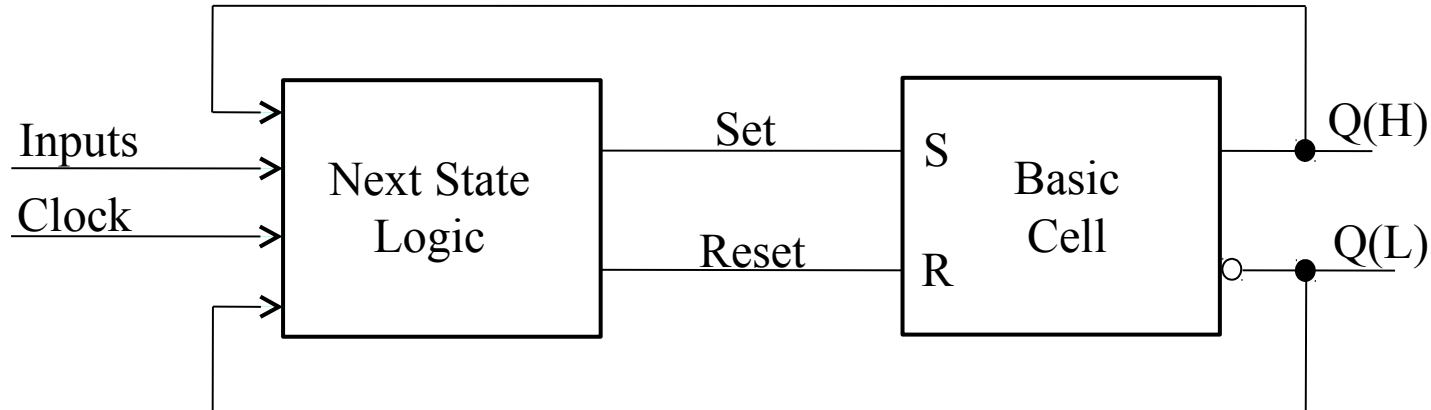

Design of a Clocked D (Data) Latch

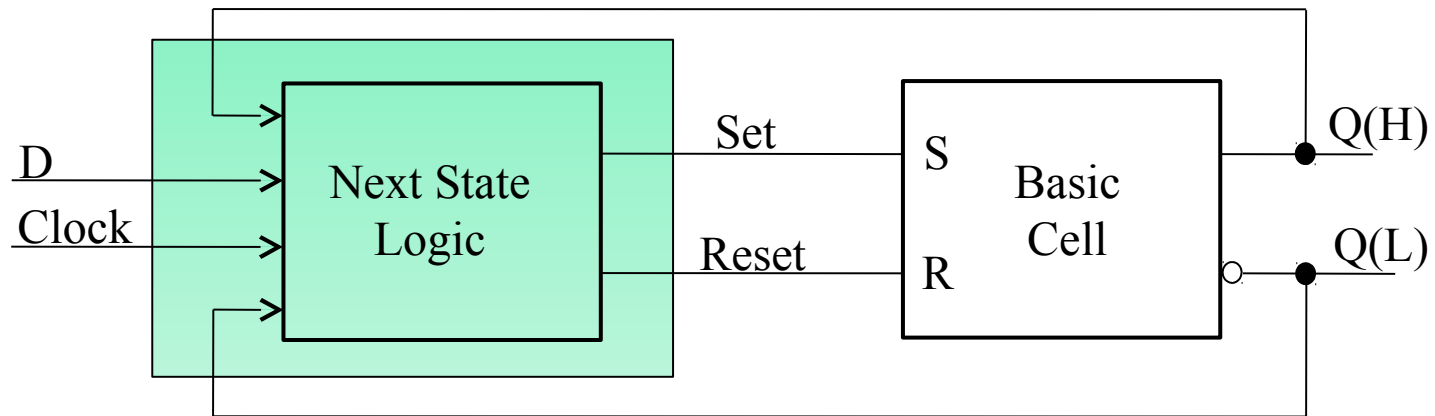

Design of a Clocked D Latch

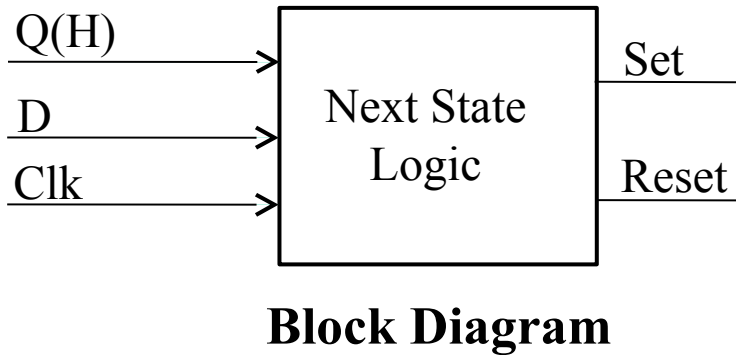

| Clk | D | Q _n | Q _{n+1} | Set | Reset |
|-----|---|----------------|------------------|-----|-------|
| 0 | 0 | 0 | 0 | 0 | φ |
| 0 | 0 | 1 | 1 | φ | 0 |
| 0 | 1 | 0 | 0 | 0 | φ |
| 0 | 1 | 1 | 1 | φ | 0 |
| 1 | 0 | 0 | 0 | 0 | φ |
| 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | φ | 0 |

Truth Table

| Clk | D | Action | Q _{N+1} |
|-----|---|--------|------------------|
| 0 | x | hold | Q _N |
| 1 | 0 | reset | 0 |
| 1 | 1 | set | 1 |

Operation Table


| Q _n → Q _{n+1} | Inputs | |
|-----------------------------------|--------|---|
| | S | R |
| 0 → 0 | 0 | φ |
| 0 → 1 | 1 | 0 |
| 1 → 0 | 0 | 1 |
| 1 → 1 | φ | 0 |

**Excitation Table
Basic Cell**

$$Set = clk \cdot D$$

$$Reset = clk \cdot \bar{D}$$

Equations

 

State Diagram

Clocked D Latch

 


Figure 7-12

D latch: (a) circuit design using NAND gates; (b) function table; (c) logic symbol.


 


Figure 7-13

Functional behavior of a D latch for various inputs.

Design of a Clocked Toggle (T) Latch

 

Block Diagram

| Clk | T | Q _n | Q _{n+1} | Set | Reset |
|-----|---|----------------|------------------|-----|-------|
| 0 | 0 | 0 | 0 | 0 | φ |
| 0 | 0 | 1 | 1 | φ | 0 |
| 0 | 1 | 0 | 0 | 0 | φ |
| 0 | 1 | 1 | 1 | φ | 0 |
| 1 | 0 | 0 | 0 | 0 | φ |
| 1 | 0 | 1 | 1 | φ | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 |

Truth Table

| Clk | T | Action | Q _{N+1} |
|-----|---|--------|------------------|
| 0 | x | Hold | Q _N |
| 1 | 0 | Hold | Q _N |
| 1 | 1 | Toggle | \overline{Q}_N |

Function Table


| Q _n → Q _{n+1} | Inputs | |
|-----------------------------------|--------|---|
| | S | R |
| 0 → 0 | 0 | φ |
| 0 → 1 | 1 | 0 |
| 1 → 0 | 0 | 1 |
| 1 → 1 | φ | 0 |

Excitation Table
Basic Cell

$$Set = clk \cdot T \cdot \overline{Q}$$


$$Reset = clk \cdot T \cdot Q$$

Equations

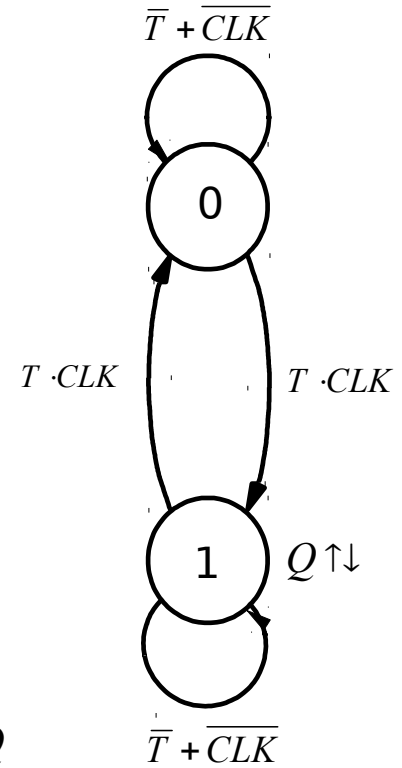

State Diagram

Design of a Clocked JK Latch

 

Block Diagram

| Clk | J | K | Qn | Qn+1 | Set | Reset |
|-----|---|---|----|------|-----|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | ϕ |
| 0 | 0 | 0 | 1 | 1 | ϕ | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | ϕ |
| 0 | 0 | 1 | 1 | 1 | ϕ | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | ϕ |
| 0 | 1 | 0 | 1 | 1 | ϕ | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | ϕ |
| 0 | 1 | 1 | 1 | 1 | ϕ | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | ϕ |
| 1 | 0 | 0 | 1 | 1 | ϕ | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | ϕ |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | ϕ | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 |

Truth Table

| Clk | J | K | Action | Q _{N+1} |
|-----|---|---|--------|------------------|
| 0 | x | x | Hold | Q _N |
| 1 | 0 | 0 | Hold | Q _N |
| 1 | 0 | 1 | Reset | 0 |
| 1 | 1 | 0 | Set | 1 |
| 1 | 1 | 1 | Toggle | \bar{Q}_N |

Function Table

| Q _n → Q _{n+1} | Inputs | |
|-----------------------------------|--------|---|
| | S | R |
| 0 → 0 | 0 | ϕ |
| 0 → 1 | 1 | 0 |
| 1 → 0 | 0 | 1 |
| 1 → 1 | ϕ | 0 |


**Excitation Table
Basic Cell**

$$Set = clk \cdot J \cdot \bar{Q}$$

$$Reset = clk \cdot K \cdot Q$$


Equations

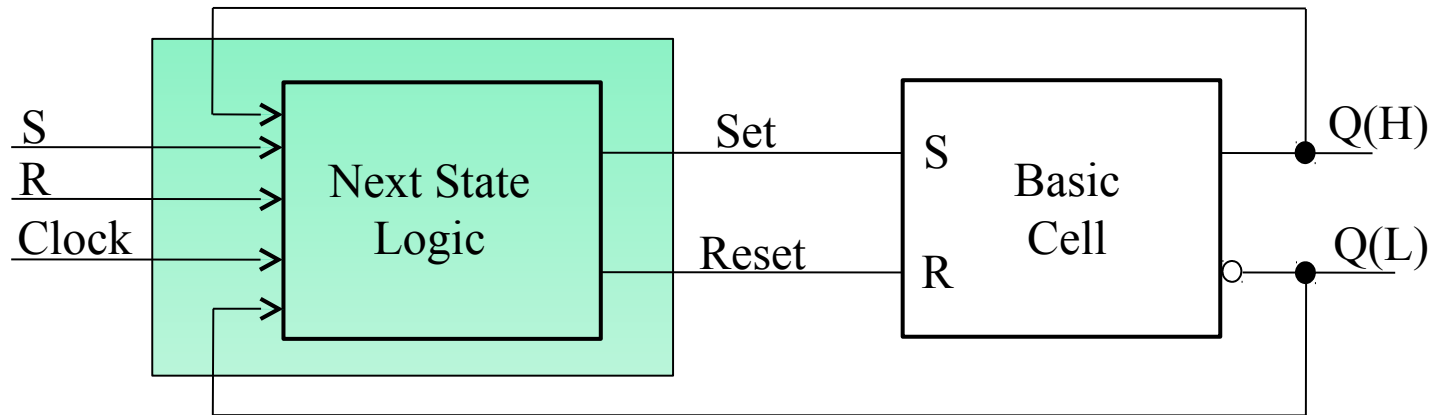Design of a Set-Dominant Clocked SR Latch



- Inputs – S, R, Clock, Q
- Outputs – Set, Reset

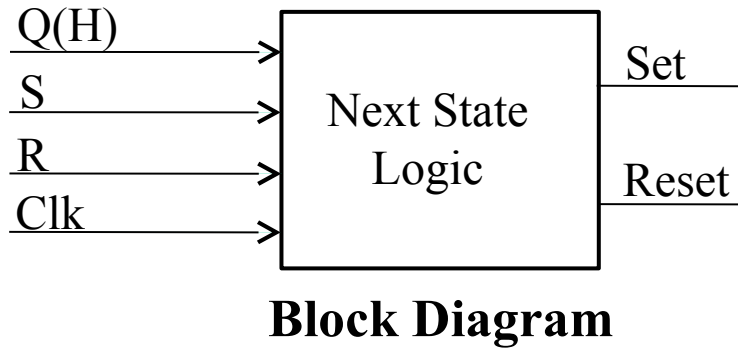Design of a Set-Dominant Clocked SR Latch



| S | R | Action | Q_{N+1} |
|---|---|--------|-----------|
| 0 | 0 | hold | Q_N |
| 0 | 1 | reset | 0 |
| 1 | 0 | set | 1 |
| 1 | 1 | set | 1 |

Operation Table

| $Q_n \rightarrow Q_{n+1}$ | Inputs | |
|---------------------------|--------|--------|
| | S | R |
| $0 \rightarrow 0$ | 0 | ϕ |
| $0 \rightarrow 1$ | 1 | 0 |
| $1 \rightarrow 0$ | 0 | 1 |
| $1 \rightarrow 1$ | ϕ | 0 |

**Excitation Table
Basic Cell**

$$Set = clk \cdot S$$

$$Reset = clk \cdot R \cdot \bar{S}$$

Equations

| Clk | S | R | Q_n | Q_{n+1} | Set | Reset |
|-----|---|---|-------|-----------|--------|--------|
| 0 | 0 | 0 | 0 | 0 | 0 | ϕ |
| 0 | 0 | 0 | 1 | 1 | ϕ | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | ϕ |
| 0 | 0 | 1 | 1 | 1 | ϕ | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | ϕ |
| 0 | 1 | 0 | 1 | 1 | ϕ | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | ϕ |
| 0 | 1 | 1 | 1 | 1 | ϕ | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | ϕ |
| 1 | 0 | 0 | 1 | 1 | ϕ | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | ϕ |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | ϕ | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | ϕ | 0 |

Truth Table

SR Latch with Enable (Clock)

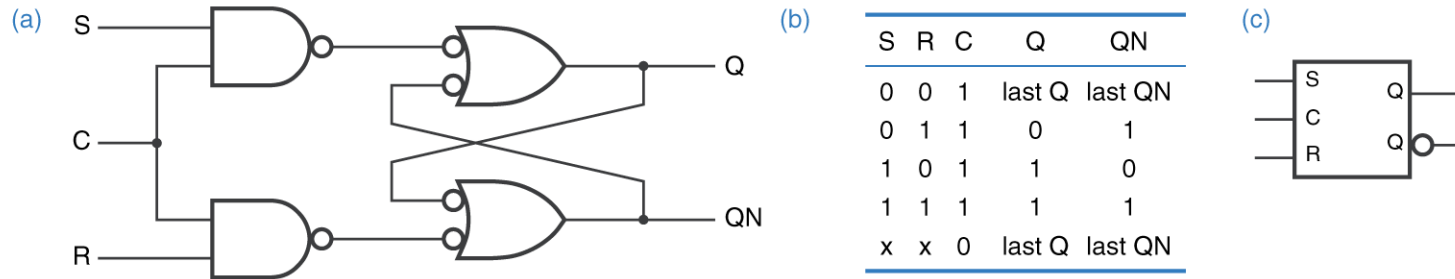


Figure 7-10

S-R latch with enable: (a) circuit using NAND gates; (b) function table; (c) logic symbol.


 


Figure 7-11

Typical operation of an S-R latch with enable.


Design of a Clocked JK Latch – Version II

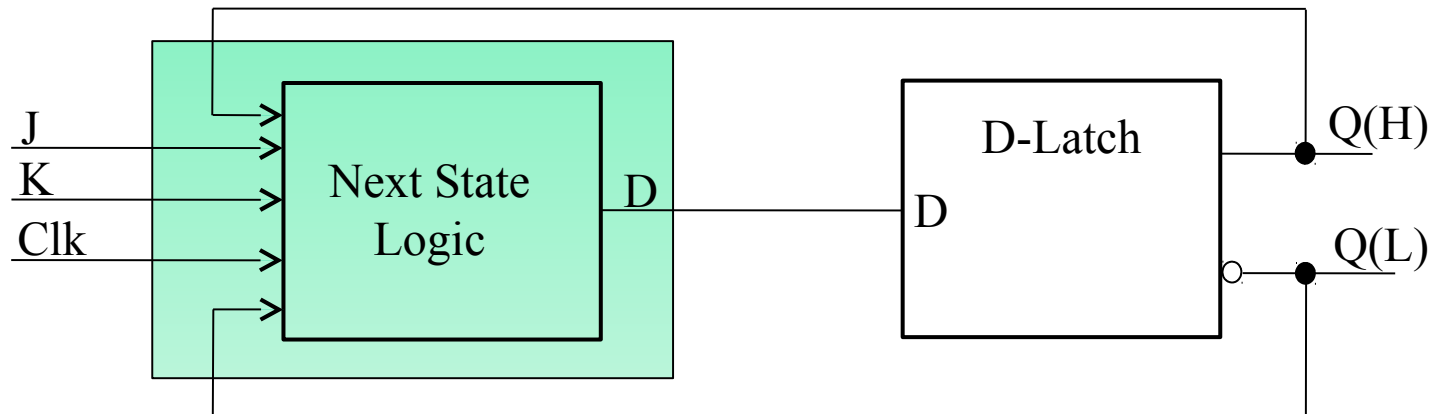- Replace the basic cell with a D-latch as the memory element.



- Inputs – J, K, Clk, Q
- Output – D

 Design of a Clocked JK Latch – Version II



Block Diagram

| Clk | J | K | Q _n | Q _{n+1} | D |
|-----|---|---|----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 |

Truth Table

| Clk | J | K | Action | Q _{N+1} |
|-----|---|---|--------|------------------|
| 0 | x | x | Hold | Q _N |
| 1 | 0 | 0 | Hold | Q _N |
| 1 | 0 | 1 | Reset | 0 |
| 1 | 1 | 0 | Set | 1 |
| 1 | 1 | 1 | Toggle | \bar{Q}_N |

Function Table

| Q _n → Q _{n+1} | D |
|-----------------------------------|---|
| 0 → 0 | 0 |
| 0 → 1 | 1 |
| 1 → 0 | 0 |
| 1 → 1 | 1 |

Excitation Table

$$D = \bar{K} \cdot Q + Q \cdot \bar{clk} + clk \cdot J \cdot \bar{Q}$$

Equation

Terminology

- Latches are often called *Transparent* because the output will follow the input as long as the clock signal is high.
- Flip-flops are *edge-triggered*
 - Positive-edge triggered (PET) is when action occurs on the rising edge of the clock signal;
 - Negative-edge triggered (NET) is when action occurs on the falling edge of the clock signal.
- Types of Flip-flops
 - SR (rarely used);
 - D (very, very common, 74HC74);
 - JK (hardly ever used, 74HC109);
 - Toggle (occasionally used by CAD programs).