
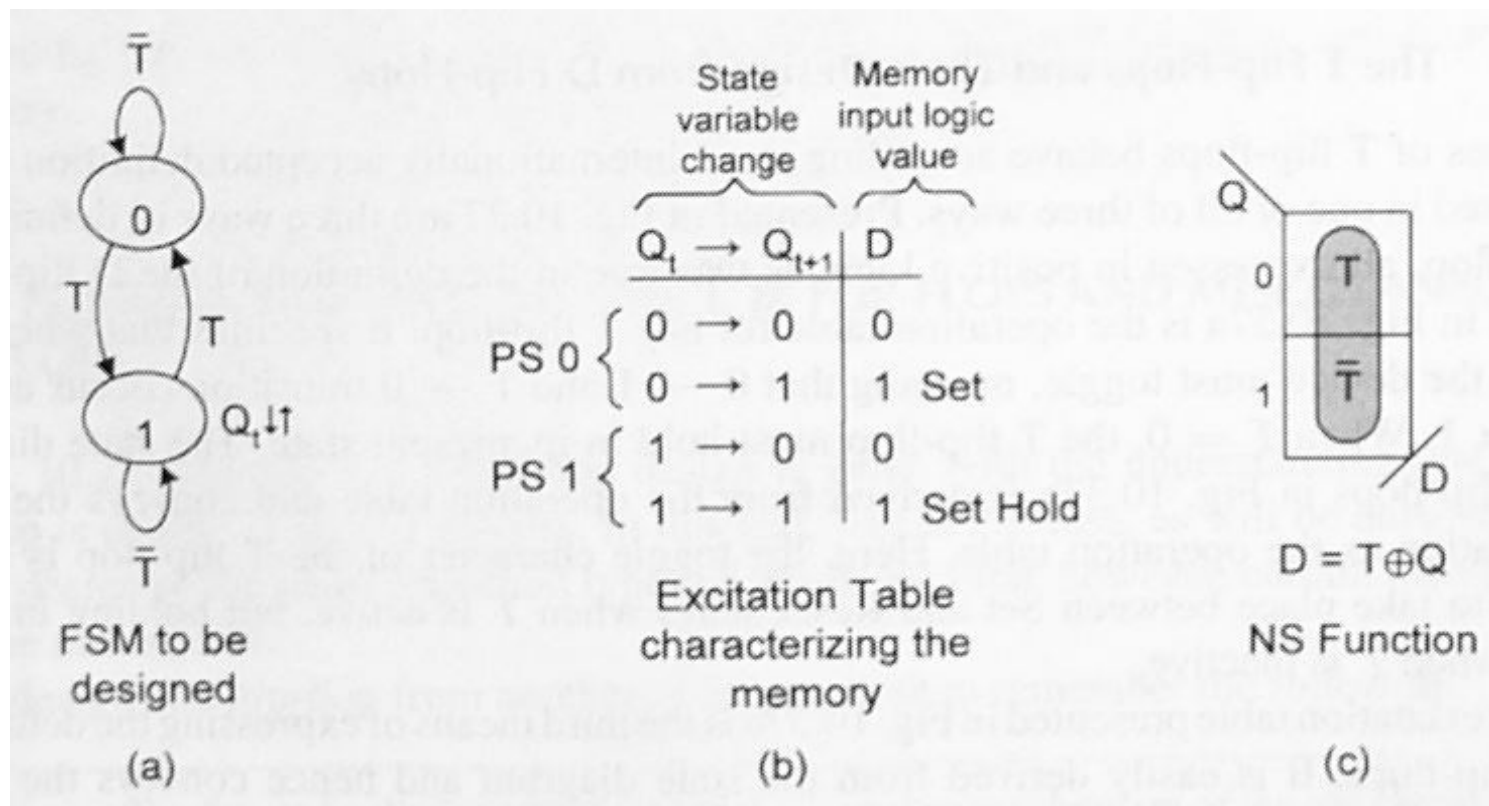




Further Consideration of State Machine Operation

Three topics today

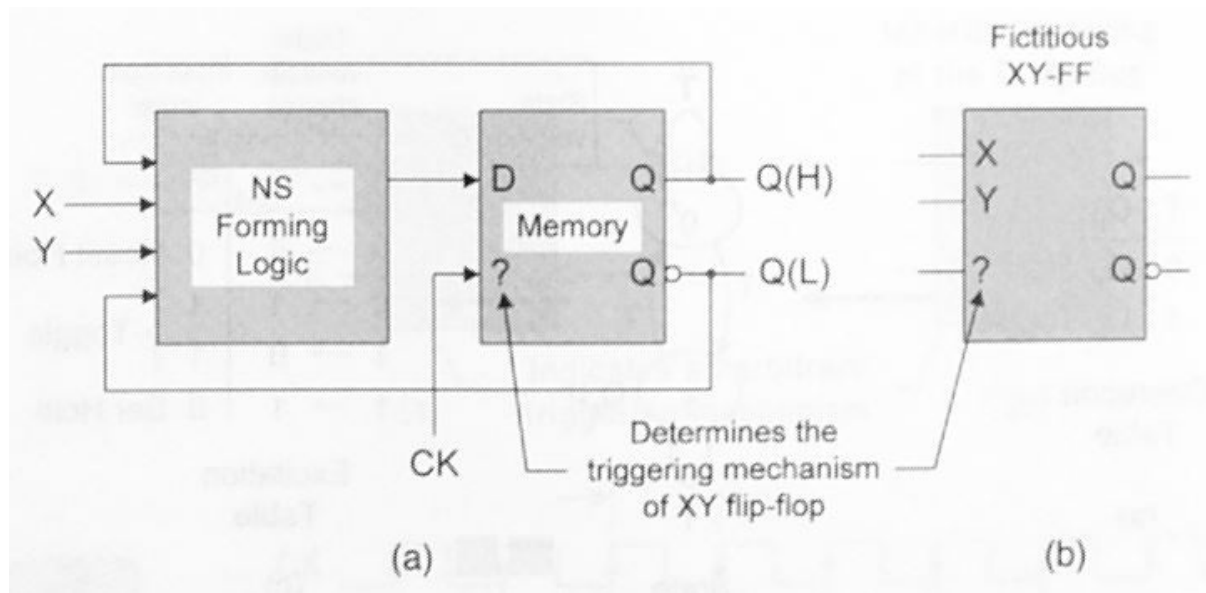- More detail about basic flip-flops
- State machine next state logic design
- State machine timing




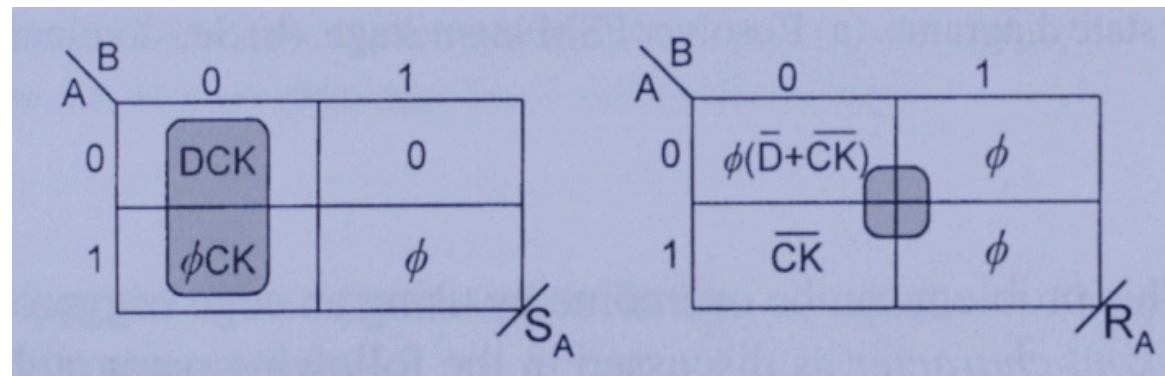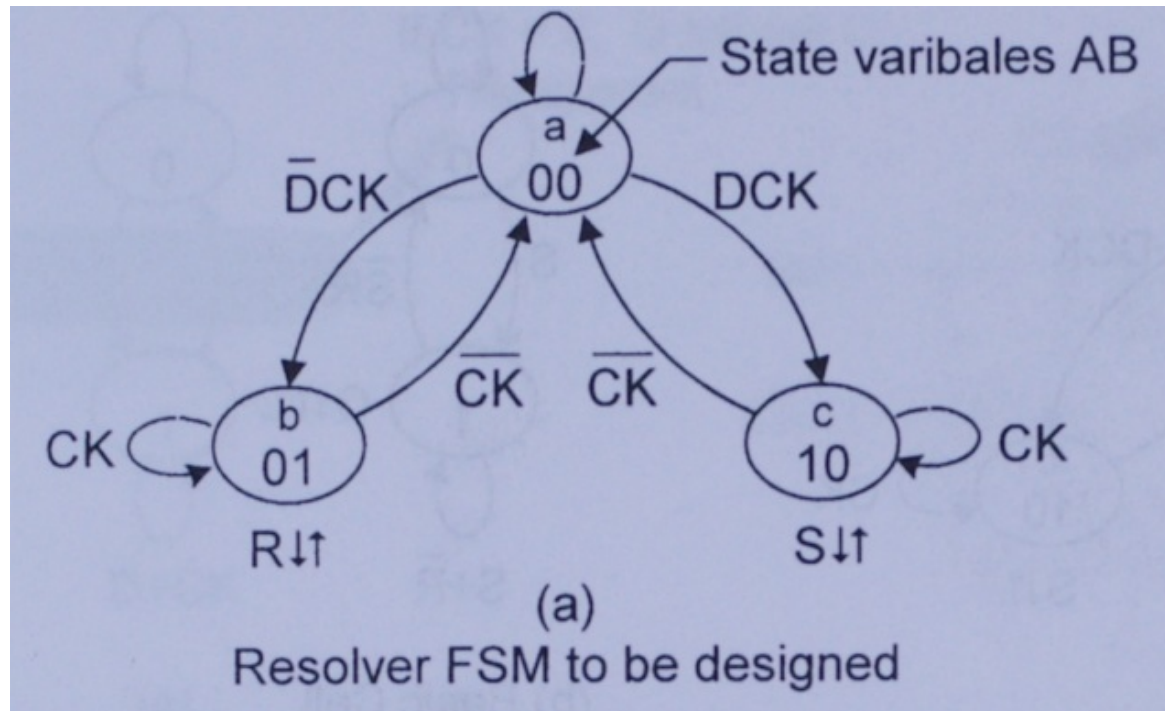Recall the resolver circuit for creating an edge triggered F/F and creation of the next state logic where the state number is binary encoded:




Next state logic design using one-hot encoding

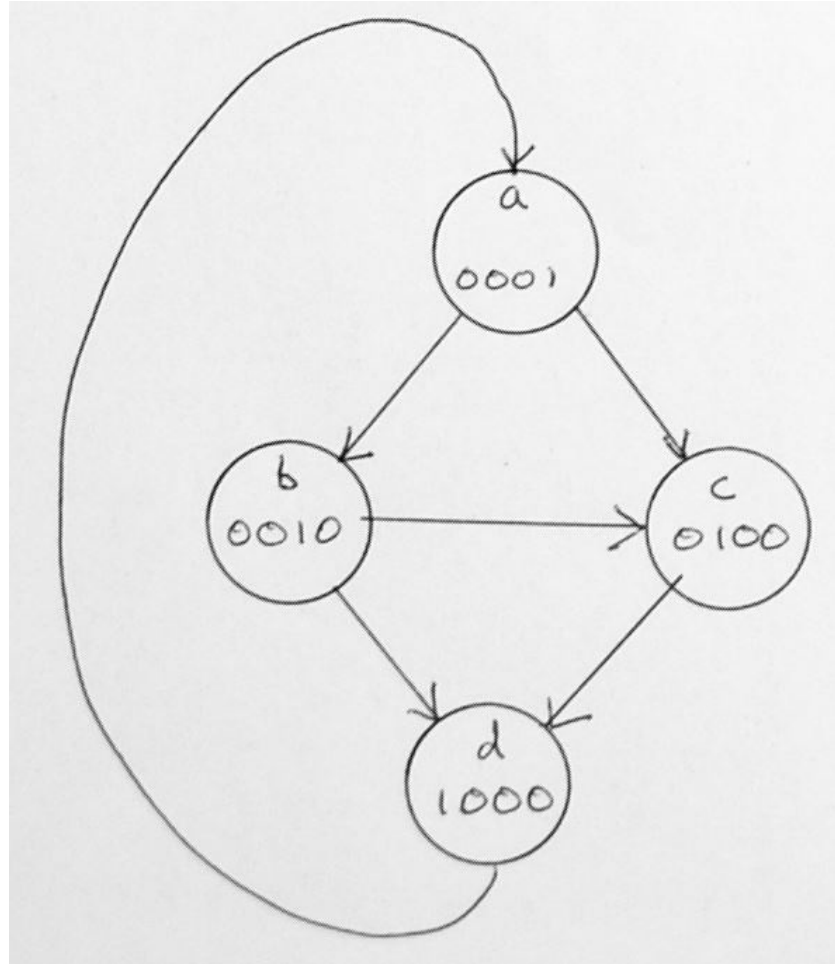
The state number, in binary, is all zeros except one digit is a one



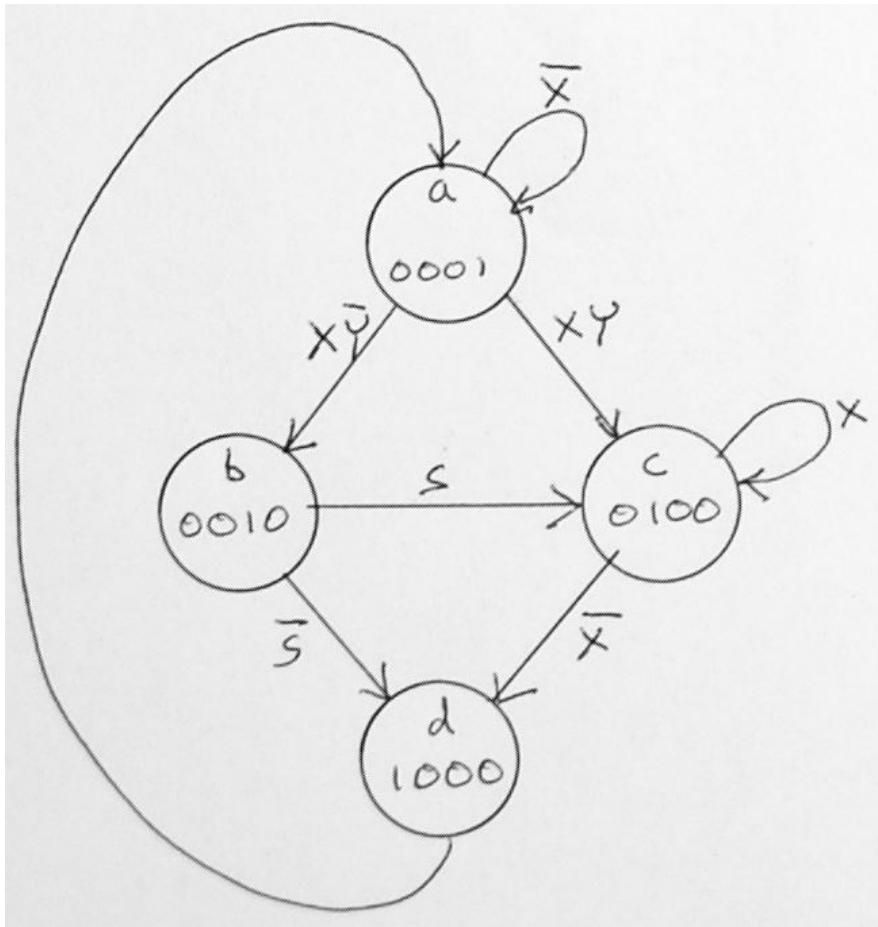Here is the same state diagram with branching conditions added



Formal definition of one-hot encoding

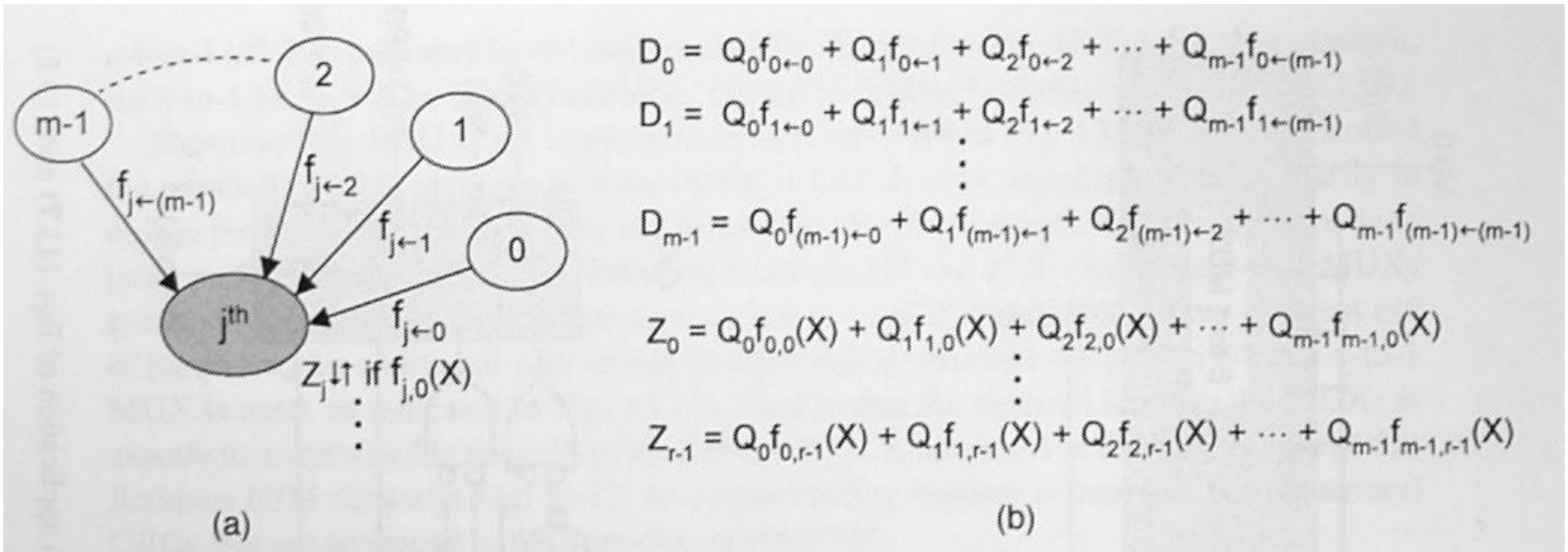


$$\begin{aligned}
 D_0 &= Q_0 f_{0←0} + Q_1 f_{0←1} + Q_2 f_{0←2} + \dots + Q_{m-1} f_{0←(m-1)} \\
 D_1 &= Q_0 f_{1←0} + Q_1 f_{1←1} + Q_2 f_{1←2} + \dots + Q_{m-1} f_{1←(m-1)} \\
 &\vdots \\
 D_{m-1} &= Q_0 f_{(m-1)←0} + Q_1 f_{(m-1)←1} + Q_2 f_{(m-1)←2} + \dots + Q_{m-1} f_{(m-1)←(m-1)} \\
 \\
 Z_0 &= Q_0 f_{0,0}(X) + Q_1 f_{1,0}(X) + Q_2 f_{2,0}(X) + \dots + Q_{m-1} f_{m-1,0}(X) \\
 &\vdots \\
 Z_{r-1} &= Q_0 f_{0,r-1}(X) + Q_1 f_{1,r-1}(X) + Q_2 f_{2,r-1}(X) + \dots + Q_{m-1} f_{m-1,r-1}(X)
 \end{aligned}$$

(b)



Below are equations that summarize next state logic D and output logic Z

$$D_j = \sum_{k=0}^{m-1} Q_k \cdot f_{j←k} \quad \text{and} \quad Z_l = \sum_{j=0}^{m-1} Q_j \cdot f_{j,l}(X)$$

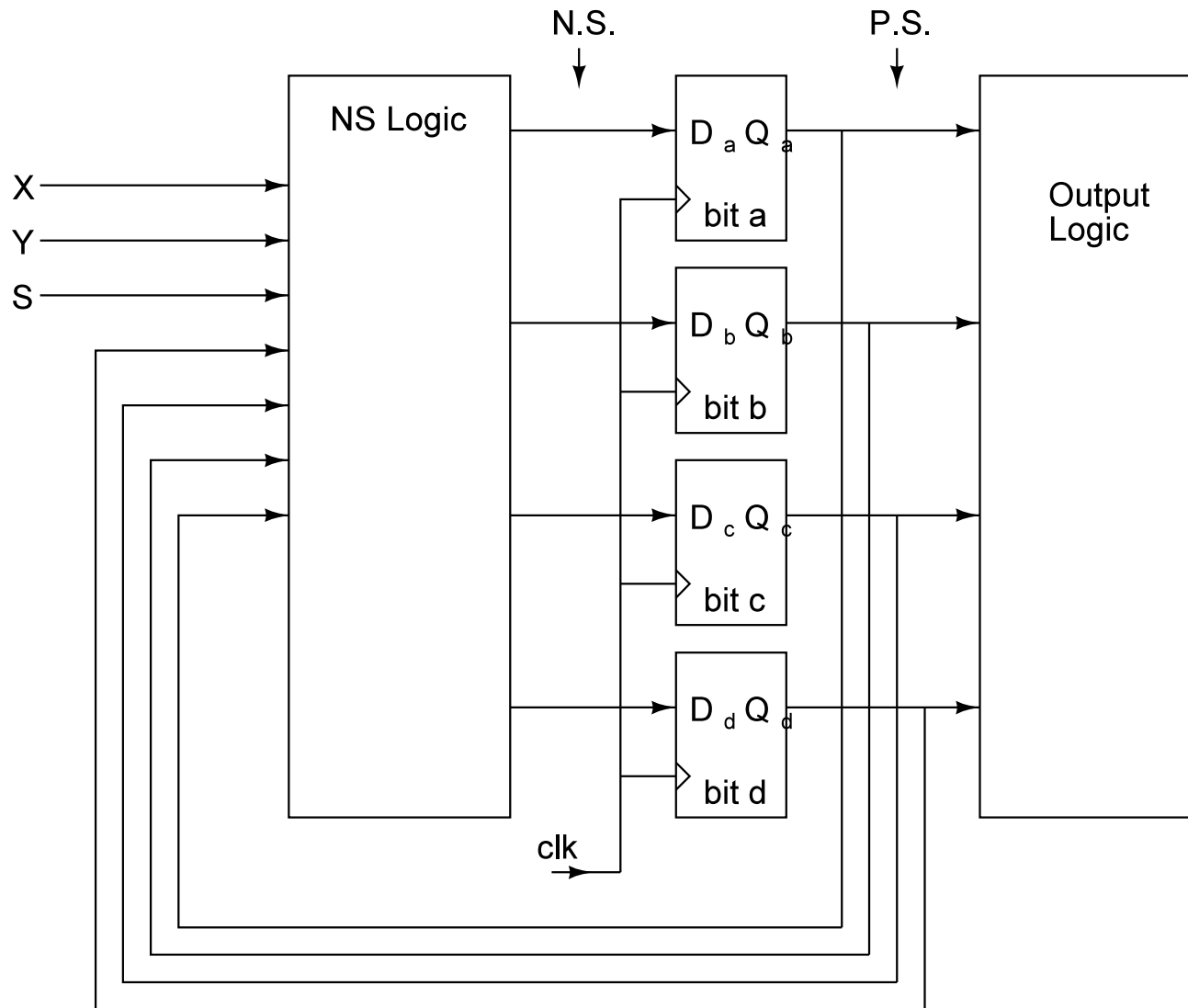For the four-state example, here is the circuit:



Here is the logic for each state bit.

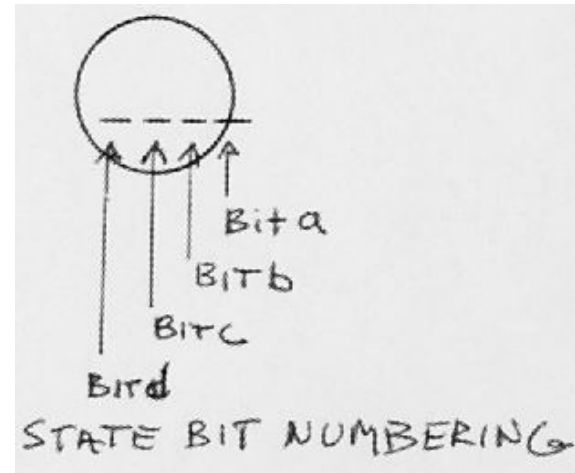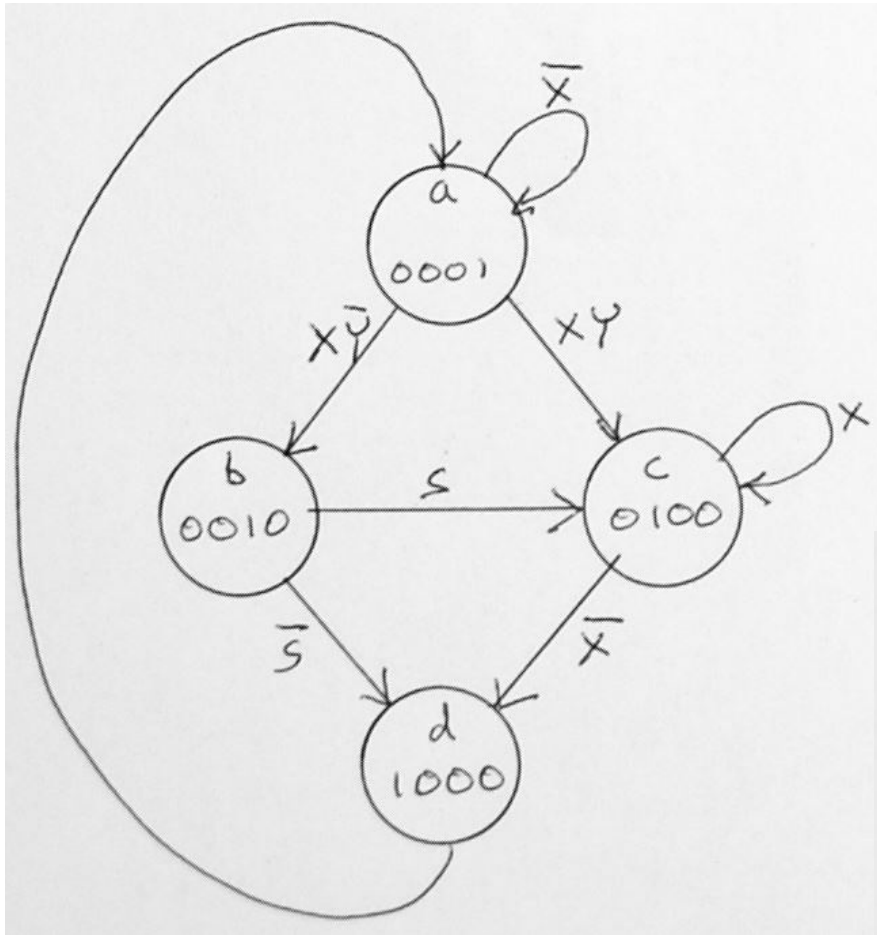

NEXT STATE LOGIC


$$D_a = \overline{X}Q_a + Q_d$$

$$D_b = X\overline{Y}Q_a$$

$$D_c = XYQ_a + SQ_b + XQ_c$$

$$D_d = \overline{S}Q_b + \overline{X}Q_c$$

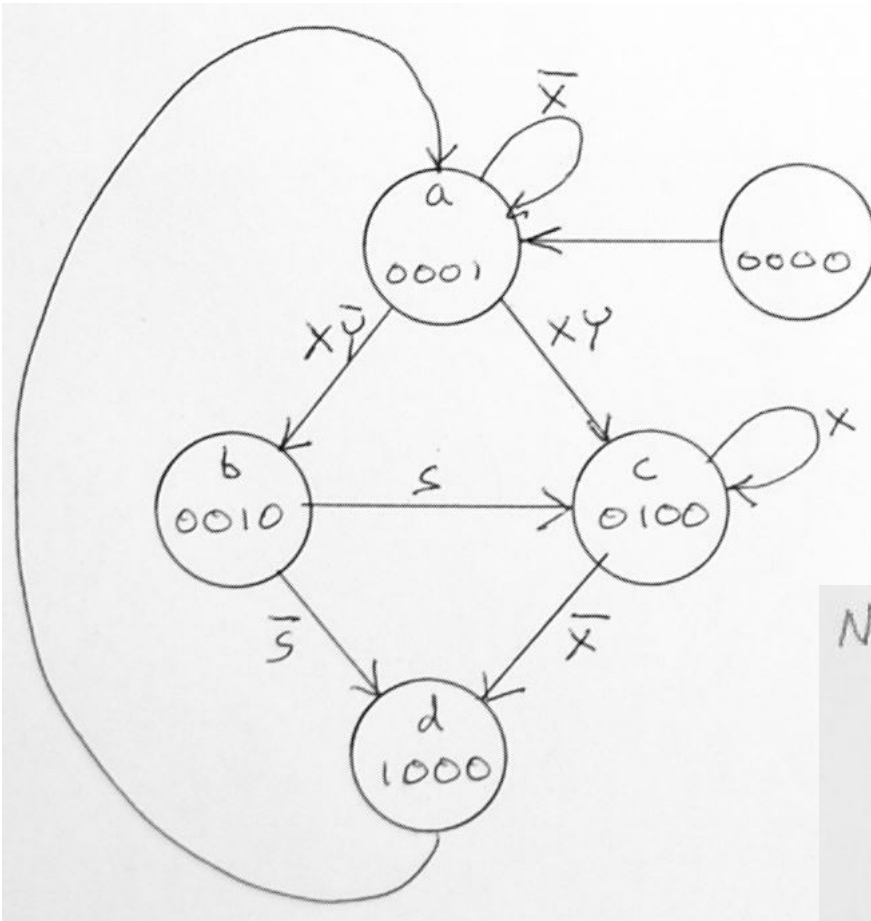One-hot plus one state coding: Adds an initial state to force transition to a desired state at system start-up.



NEXT STATE LOGIC

$$D_a = \bar{X}Q_a + Q_d + \underbrace{\bar{Q}_d\bar{Q}_c\bar{Q}_b\bar{Q}_a}_{\text{TRANSITION FROM 0000}}$$

$$D_b = X\bar{Y}Q_a$$

$$D_c = XYQ_a + SQ_b + XQ_c$$

$$D_d = \bar{S}Q_b + \bar{X}Q_c$$

A more complex example.

